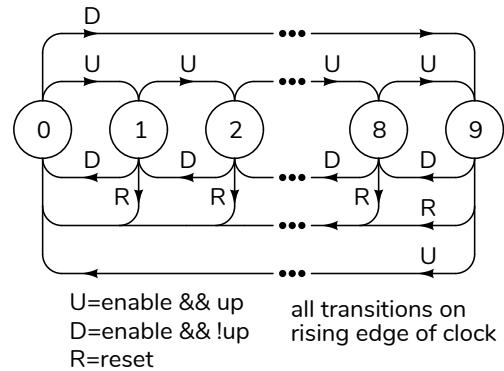


BCD Counters

Introduction

Counters that count in base 10 rather than binary are useful when the count must be displayed as decimal digits. Each digit is represented by a 4-bit counter that counts from 0 to 9. This is known as binary-coded decimal (BCD). Multi-digit BCD counters can be built from single-digit BCD counters as described below.

In this lab you will design a single-digit BCD counter. A test module provided by the instructor will use four instances of your module to create a four-digit up/down counter whose digits will be displayed on the multiplexed LED display used in the previous lab.




carry is a combinational logic output that is asserted when **count** is equal to 9 and **enable** and **up** are asserted. **carry** is also asserted when **count** is equal to 0, **enable** is asserted and **up** is not ¹:

count	enable	up	carry
9	1	1	1
0	1	0	1
others			0

BCD Counter Specifications

 
Your BCD up/down counter must have **clock**, **enable** and **reset** inputs. An **up** input controls the count direction: up when asserted, down otherwise. The counter has a 4-bit BCD **count** output and a one-bit **carry** output:



The counter is synchronous. This means the count value changes only on the rising edge of the clock. As shown in the following state transition diagram, **count** is:

- set to zero when **reset** is asserted,
- incremented when **enable** and **up** are asserted,
- decremented when **enable** is asserted and **up** is not asserted:

 The **carry** output allows BCD counters to be combined into a multi-digit counter by connecting the **carry** output of one digit to the **enable** input of the next-most-significant digit:



In such a multi-digit counter the **clock**, **reset** and **up** inputs are connected together.

Note that, unlike some other counter designs, **count** does not necessarily change in each clock cycle and the **enable** signal is not a clock.

Components

You will need the same components as in the previous lab plus two pushbutton switches (use the

¹When counting down carry means “borrow.”

normally-closed contacts as shown in the schematic below).

Procedure

Design a BCD counter that meets the specifications above.

Download the `lab5.qar` project archive file from the course web site. This project archive includes a complete project except for the Verilog code in the file `bcdcount.sv`.

Open the archive file with Quartus and restore it to a convenient folder. Add your BCD counter code to `bcdcount.sv`. Do not rename the signals in the `bcdcount` module declaration. Change the pin assignments, if necessary, to match your circuit layout. Compile your design, program the CPLD and test it.

The project contains an `.sdc` file that defines the clock frequency (50 MHz) and the I/O signals as asynchronous. This allows Quartus to verify that your design operates at that clock frequency.

The project also includes a `.srf` file to suppress spurious error messages. These files should allow your project to compile without warnings:


● 293000 Quartus Prime Full Compilation was successful. 0 errors, 0 warnings

The archive was created using Quartus version 20.1. Opening it with Quartus II version 13.0sp1 will display errors but you can open the `.qpf` project file after restoring the archive.

The test circuit instantiates four of your BCD counters as shown above and displays the count on the 4-digit LED display. The `up_in` pushbutton increments the count at 1 kHz while the `down_in` button decrements it at 100 Hz. Pushing both buttons resets the counters.

CPLD I/O

 
The connections to the CPLD are shown in the following diagram:




The pin assignments for the LED in the supplied project are the same as in the previous lab. The two pushbutton switch inputs have pull-up resistors configured. The pin assignments are shown below:

To	Assignment Name	Value
out a	Location	PIN_33
out b	Location	PIN_44
out c	Location	PIN_38
out d	Location	PIN_34
out e	Location	PIN_30
out f	Location	PIN_52
out g	Location	PIN_40
out dp	Location	PIN_36
out en[0]	Location	PIN_42
out en[1]	Location	PIN_48
out en[2]	Location	PIN_50
out en[3]	Location	PIN_35
in clock	Location	PIN_12
in up_in	Location	PIN_99
in up_in	Weak Pull-Up Resistor	On
in down_in	Location	PIN_97
in down_in	Weak Pull-Up Resistor	On

 The wiring to the 7-segment LED is shown below:



and the connections to the CPLD pin headers are:

 

 


Figure 1: Example RTL Schematic for Lab 5.

Submission

To get credit for completing this lab, submit the following to the Assignment folder for this lab on the course website:

1. A PDF document containing:
 - Your name, BCIT ID, course number and lab number.
 - A listing of your `bcdcount00` block to expand it, and then `File > Export...`. The file should look similar to Figure 1.
2. The PDF file containing the schematic created by `Tools > Netlist Viewers > RTL Viewer`, clicking on

the + button on the `bcdcount00` block to expand it, and then `File > Export...`. The file should look similar to Figure 1.

Note that this is the schematic of one of your BCD counters, not of the complete design.

3. a video of your breadboard distinctly showing:
 - the count being reset when both buttons are pushed
 - the count reaching more than 1000 when the `up_in` button is pushed (about 1 second)
 - the count being reset again when both buttons are pushed
 - the count reaching less than 9900 when the `down_in` button is pushed (about 1 second)

Flow Summary	
Flow Status	Successful - Sun Oct 18 12:31:38 2020
Quartus Prime Version	20.1.0 Build 711 06/05/2020 SJ Lite Edition
Revision Name	lab5
Top-level Entity Name	lab5
Family	MAX II
Device	EPM240T100C5
Timing Models	Final
Total logic elements	124 / 240 (52 %)
Total pins	15 / 80 (19 %)
Total virtual pins	0
UFM blocks	0 / 1 (0 %)

2. The PDF file containing the schematic created by `Tools > Netlist Viewers > RTL Viewer`, clicking on