 


## Introduction to Digital Design with Verilog HDL


**Exercise 1:** What changes would result in a 3-input OR gate?

```
// AND gate in Verilog  
module ex1 ( input logic a, b, c,  
             output logic y ) ;  
  
    assign y = a | b | c ;  
  
endmodule
```

**Exercise 2:** What schematic would you expect if the statement was `assign y = ( a ^ b ) | c ;`?






 **Exercise 3:** If the signal `i` is declared as `logic [2:0] i;`, what is the 'width' of `i`? If `i` has the value 6 (decimal), what is the value of `i[2]`? Of `i[0]`?



$i[2] = 1$   
 $i[1] = 1$   
 $i[0] = 0$

packed array models a bus:

   


**Exercise 4:** What changes might result in a 4-bit 4-to-1 multiplexer controlled by a 2-bit sel input?

```

1 module ex3 (input logic [1:0] sel,
2             input logic [3:0] a, b, c, d,
3             output logic [3:0] y) ;
4
5     always_comb begin
6         if (sel[1] == 0)
7             if (sel[0] == 0)
8                 y = a ;
9             else
10                y = b ;
11        else
12            if (sel[0] == 0)
13                y = c ;
14            else
15                y = d ;
16    end
17
18 endmodule

```

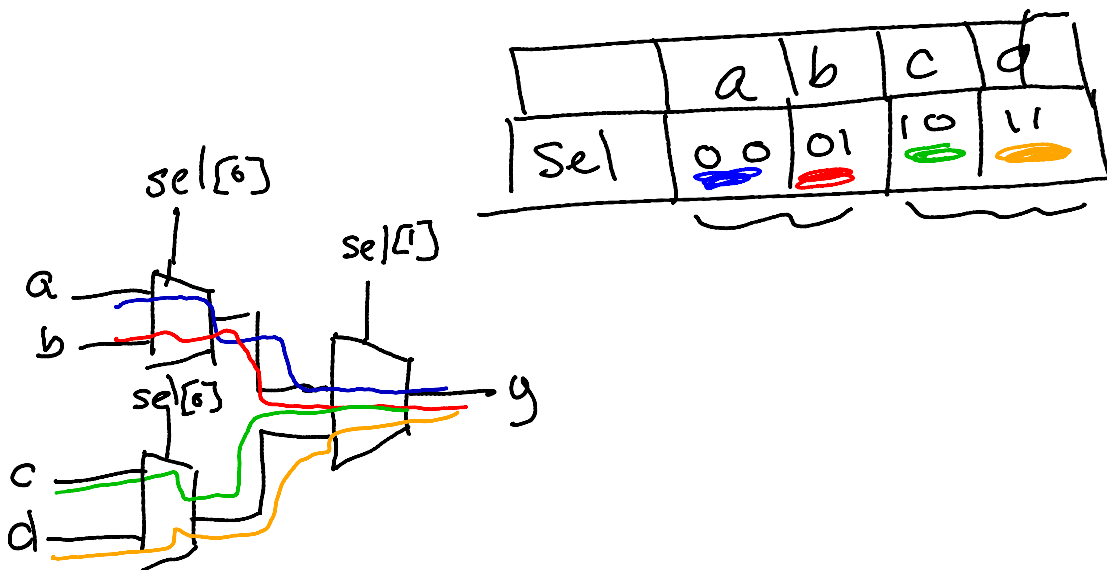

**Exercise 5:** What is the output in binary when the input is `a=2'b10`

$2'b10 = 10$   
d) would be set to 'ha4  
32-bit value (only L.S. 8 bits used)  
 $hA4 = \underline{1010\_0100}$

**Exercise 6:** What are the values in decimal of the constants in the code above?

`0'hc0` ,  $\rightarrow 1100\_0000 = 192$   
`8'b1111_1001` ;  $\rightarrow$   
`'ha4` ;  
`t: d = 176` ;  $\cdot 176$