 


Implementation of Digital Logic Circuits

Exercise 1: If \overline{D} is a data bus and $\overline{D_0}$ is low, is the value on the data bus an even or odd number?

$\overline{D_0}$ is the least-significant bit and low = 1
 . it's an odd number.

Exercise 2: Which transistors are on when the output is high? When it is low? In which direction does the output current flow in each case?




Exercise 3: Which of these specifications does the manufacturer guarantee? Which are requirements?

V_{OH}
 V_{OL} } guaranteed

V_{IL}
 V_{IH} } required


were not defined
 for voltage levels

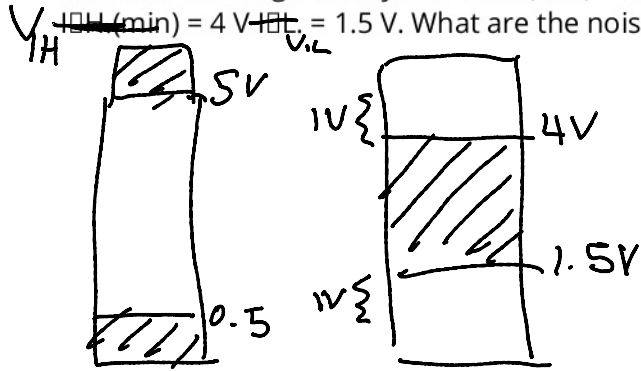Exercise 4: A logic family has $V_{OH}(\min) = 5\text{ V}$, $V_{OL}(\max) = 0.5\text{ V}$, $V_{IH}(\min) = 4\text{ V}$, $V_{IL}(\max) = 1.5\text{ V}$. What are the noise margins?



$$\text{noise margin (H)} = 5 - 4 = 1\text{ V}$$
 
$$\text{noise margin (L)} = 1.5 - 0.5\text{ V}$$



} typically quote as positive number.


Exercise 5: All else being equal, by how much would we expect to decrease power consumption when reducing logic levels from 5 V to 3.3 V? What would be the effect on power consumption in reducing the clock frequency from 50 MHz to 1 MHz?

$$\text{power} \propto c f v^2$$


$$\frac{P_{3.3} = c \cdot f \cdot (3.3)^2}{P_5 = c \cdot f \cdot 5^2} = \frac{11}{25} < \frac{1}{2}$$

$$\frac{P_1 = c \cdot 1 \cdot v^2}{P_{50} = c \cdot 50 \cdot v^2} = 2\%$$

= g. battery powered watch
32,768 Hz

 

 Exercise 6: What are the active-state current and the RC time constant for a wired-or interrupt-request line using a 10kΩ resistor pulling up a circuit with 50 pF capacitance to 3.3 V?



0	H	L	H
②	H	L	L
9P	L	H	Z

$$R = 10k$$

$$C = 50 pF$$

$$V_{dd} = 3.3V$$

$$i = \frac{V}{R} = \frac{3.3}{10k} = \underline{\underline{0.3 mA}}$$

$$RC = 10 \times 10^3 \cdot 50 \times 10^{-12}$$

$$= 500 \times 10^{-9}$$

$$= 0.5 \times 10^{-6}$$

