

Interfaces

Exercise 1: How could you modify the circuit so that the bits are transmitted in order from the most-significant to the least-significant bit?

