

- Power consumption at 2.5V is 100mW, what would be the estimated power consumption at 5V?

power $\propto V^2$ $\frac{P_2}{P_1} = \frac{V_2^2}{V_1^2} = \left(\frac{V_2}{V_1}\right)^2 = \left(\frac{5}{2.5}\right)^2 = 2^2 = 4$ $\left(\begin{array}{l} \times 100\text{mW} = \\ \underline{\underline{400\text{mW}}} \end{array}\right)$


- Power consumption at 32 kHz is 0.1mW, what would be estimated power consumption at 32 MHz?

power $\propto f$ $\frac{P_2}{P_1} = \frac{f_2}{f_1} = \frac{32 \times 10^6}{32 \times 10^3} = 1000$

$P_2 = P_1 \cdot 1000 = 0.1\text{mW} \cdot 1000 = \underline{\underline{100\text{mW}}}$

- The pull-up resistor results in a steady-state current when the OC bus is pulled low

- What is this current?

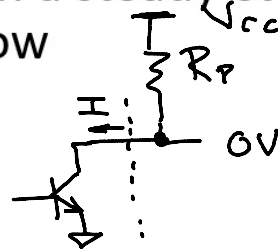

$I = \frac{V}{R} = \frac{V_{CC}}{R_P}$

e.g. $V_{CC} = 5\text{V}$
 $R_P = 1\text{k}\Omega$

$I = \frac{5}{1000} = 5\text{mA}$

- If there is a capacitance between the bus and ground, it will take time to charge. What is the time constant?

$\tau = RC = R_P \cdot C$

e.g. $R_P = 1\text{k}\Omega$

$C = 20\text{pF}$

$RC = 1 \times 10^3 \times 20 \times 10^{-12} \text{ s}$
 $= 20 \times 10^{-9} = \underline{\underline{20\text{ns}}}$