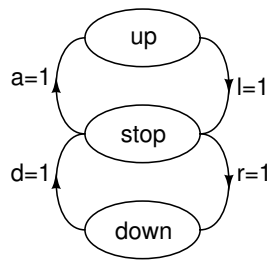


Practice Lab Exam 1

State Transition Diagram



Outputs

up 1100
stop 0000
down 0011

Marking

l	r	a	d	output	check
0	0	1	1	1100	<input type="checkbox"/>
0	0	0	0	1100	<input type="checkbox"/>
1	0	0	0	0000	<input type="checkbox"/>
0	0	0	0	0000	<input type="checkbox"/>
0	1	0	0	0011	<input type="checkbox"/>
0	0	0	0	0011	<input type="checkbox"/>
0	0	0	1	0000	<input type="checkbox"/>
0	0	1	0	1100	<input type="checkbox"/>