 


Solutions to Midterm Exam


Midterm 1

Question 1

There were two timing diagrams, one for a J-K flip-flop:



and one for an SR flip-flop:

 

and two truth tables, one for a T flip-flop:


T	$\overline{\text{CLR}}$	clk	Q	\overline{Q}
x	0	x	0	1
0	1	↑	Q_0	$\overline{Q_0}$
1	1	↑	$\overline{Q_0}$	Q_0
0	1	↑	Q_0	$\overline{Q_0}$

and one for a J-K flip-flop:

J	K	$\overline{\text{CLR}}$	clk	Q	\overline{Q}
x	x	0	↑	0	1
0	1	1	↑	0	1
1	0	1	↑	1	0
1	1	1	↑	$\overline{Q_0}$	Q_0

 Question 2

There were two timing diagrams with different labels. Only one is shown here:



On this device the clock signal is an output from the microcontroller. It is also an input to the flip-flops in the peripheral device and in the microcontroller. These flip-flops store the data transmitted over the interface¹.

The **clock out** signal is specified as an output so timing specifications between two points on the clock (A, B, C, G and F above) will be guaranteed specifications.

The **data in** signal is an input so timing specifications for this signal (D, E) relative to a clock edge will be requirements.

letter	name	var.	R/G
A	period	T	G
$\frac{C}{B+C}$	duty cycle	t_{DC}	G
D	setup time	t_{SU}	R
E	hold time	t_H	R
F	rise time	t_R	G
G	fall time	t_F	G

Question 3

There were two versions of the question with different values. In each case the minimum clock period is $T_{\min} = t_{CO} + t_{PD} + t_{SU}$ and the maximum clock period is $f_{\max} = 1/T_{\min}$.

¹Since we had not covered this situation before, specification D will also be marked correct if specified as a propagation delay. Specification E cannot be a propagation delay because the change in the output happens before the change in the input.

- for $t_{CO} = 3$ ns, $t_{SU} = 5$ ns and $t_{PD} = 8$ ns, $T_{min} = 3+8+5 = 16$ ns and $f_{max} = 1/16$ GHz = 62.5 MHz
- for $t_{CO} = 5$ ns, $t_{SU} = 2$ ns and $t_{PD} = 3$ ns, $T_{min} = 5+3+2 = 10$ ns and $f_{max} = 1/10$ GHz = 100 MHz

Question 4

The figure shows a circuit that adds 1 to Q if Q is less than 3, otherwise the value is unchanged. Thus if the value of Q is less than 3 it increases by 1 each clock edge until it reaches the value 3. There were two versions of the question, with initial values of 1 and 0.


If the initial value is 1 then the next values in the sequence will be 2, 3, 3 and 3. If the initial value is 0, the subsequent values will be 1, 2, 3, 3.

Midterm 2

 Question 1

There were two versions of this question, one turning on the warning after two faults, the other three. The three-fault version simply has one more state and is shown below.


- The hint says to use the number of faults since the most recent reset as the state. We'll name them **S0**, **S1**, **S2** and (optionally) **S3**.
- The state transition diagram simply moves from one state to the next higher count when **fault** is asserted and to **S0** when **reset** is asserted:




- In this case the output is only high in state **S3** so the expression, in VHDL format, for the output could be: `warn <= '1' when state = S3 else '0' ;`.

 Question 2


There were two versions of this question, differing only in the order.




`a <= b nand c ;`

 
 
`y <= x when a = '1' or b = '1' else x"ff" ;`



 
`y_next <= y+1 when a = '1' else
y-1 when b = '1' else
x"00" when a = '1' and b = '1' else
y ;`




`y <= y_next when rising_edge(d) ;`

 Question 3


There were two version of this question differing only in the order of the block diagrams. The VHDL for each diagram is shown below:



 
```
c <= a nor b ;
-- or
c <= not ( a or b ) ;
```



 
```
y_next <= x when c = '1' else y ;
```


 
```
c <= a when not ( b = '1' ) else 'Z' ;
```



```
y <= x when rising_edge(a) ;
```

 

```
-- the simplest solution is to negate the control
-- input of the highest-priority multiplexer
-- the condition could be:
--   y /= z           -- best
--   not ( y = z )   -- OK
--   ( y = z ) = false -- should work
```

```
y_next <=
  y - 1 when y /= z else
  z when a = '1' else
  y - x ;
```

-- an alternate solution is to use logic that
-- ensures the y=z condition has priority

```
y_next <=
  z   when y = z and a = '1' else
  y-x when y = z and a = '0' else
  y-1 ; -- if y /= z
```

-- another solution that was accepted because it
-- was not explicitly disallowed is to use an
-- intermediate variable:

```
tmp <= z when a = '1' else y-x ;
y_next <= tmp when y = z else y-1 ;
```