 


Introduction to Digital Design with Verilog HDL

Exercise 1: What changes would result in a 3-input OR gate?


```
// AND gate in Verilog  
  
module ex1 ( input logic a, b, c,  
             output logic y ) ;  
  
] assign y = a | b | c ;  
  
endmodule
```

Exercise 2: What schematic would you expect if the statement was `assign y = (a ^ b) | c ;`?



Exercise 3: Write two assign statements that produce the same result. Does their order in the module matter?

```
// AND gate in Verilog  
  
module ex3 ( input logic a, b, c,  
             output logic y ) ;  
  
] logic z ;  
] assign y = z | c ;  
] assign z = a ^ b ;  
  
endmodule
```

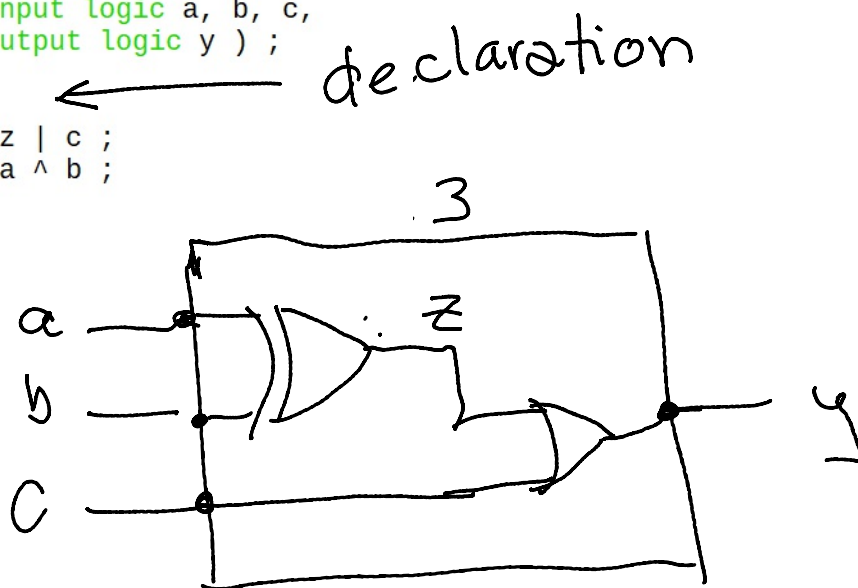

Exercise 4: What is the value of the expression $3 \ ? \ 10 \ : \ 20$? Of the expression $x \ ? \ 1 \ : \ 0$ if x has the value 0? If x has the value -1?

$$3 \ ? \ 10 \ : \ 20 \ \Rightarrow \ 10$$

$$x \ ? \ 1 \ : \ 0 \ \Rightarrow \ \begin{array}{l} \text{if } x=0 \Rightarrow 0 \\ \text{if } x=-1 \Rightarrow 1 \end{array}$$

Exercise 5: If the signal i is declared as `logic [2:0] i;`, what is the 'width' of i ? If i has the value 6 (decimal), what is the value of $i[2]$? Of $i[0]$?

width : 3 bits

$$6_{10} = 110_2$$



$\begin{array}{ccc} & \nearrow & \nearrow \\ i[2] & & i[0] \\ & \nwarrow & \nwarrow \\ & i[1] & \end{array}$

$$i[2] = 1$$


$$i[0] = 0$$

Exercise 6: Write the truth table and Verilog description of a 3-bit 4-to-1 multiplexer controlled by a 2-bit sel input? Label the inputs a (for sel=00) through d (for sel=11).

inputs		outputs
sel		y
0	0	a
0	1	b
1	0	c
1	1	d

  

There are (at least) two solutions:

 

Multiplexers are implemented with the conditional operator.

```

/*
Exercise 6: Write the truth table and Verilog description of a 3-bit
4-to-1 multiplexer controlled by a 2-bit sel input? Label the inputs
a (for sel=00) through d (for sel=11).
*/
module ex6 (
input logic [1:0] sel,
input logic [2:0] a, b, c, d,
output logic [2:0] y );

assign y = !sel[1] ? ( sel[0] ? b : a ) : (sel[0] ? d : c ) ;



/*
assign y = sel == 2'b00 ? a :
( sel == 2'b01 ? b :
( sel == 2'b10 ? c :
d ) );
*/
endmodule

```

Note Correction (Jan. 19)

	sel[1]	sel[0]
a	0	0
b	0	1
c	1	0
d	1	1

  Note that Quartus combined the two 3-bit muxes into one 6-bit mux.



/*

Exercise 6: Write the truth table and Verilog description of a 3-bit 4-to-1 multiplexer controlled by a 2-bit sel input? Label the inputs a (for sel=00) through d (for sel=11).

```




*/
module ex6 ( input logic [1:0] sel,
             input logic [2:0] a, b, c, d,
             output logic [2:0] y );

//[] assign y = sel[1] ? ( sel[0] ? b : a ) : ( sel[0] ? d : c ) ;

    assign y = sel == 2'b00 ? a :
        ( sel == 2'b01 ? b :
          ( sel == 2'b10 ? c :
            d ) );

endmodule

```

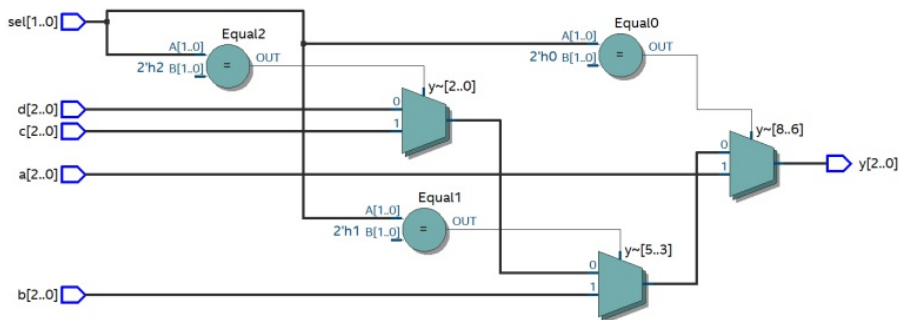  

Exercise 7: What are the values, in decimal, of the constants in the code above?

```

module ex37 (input logic [1:0] a,
             output logic [3:0] d) ;

    logic [3:0] lut [4] =
        '{ 4'b1000, 4'd1, 4'ha, 3 } ;

    assign d = lut[a] ;

```


$$4'b1000 = 8$$

$$4'd1 = 1$$

$$4'ha = 10$$

$$\underbrace{[3:0]}_{[d]} 3 = 3$$

 Exercise 8: What is the output, in binary, when the input is $a=2'b10$ →



output will be 1010_2 10_{10} .

Exercise 9: Write a Verilog module with a two-bit input i and a two-bit output n that uses an unpacked array to output the number of bits in the input that are "1". Start by writing the truth table.

i	n
00	00
01	01
10	01
11	10

```

module ex9 (input logic [1:0] i,
            output logic [1:0] n );

    logic [1:0] nbits [4] = '{ 2'b00, 2'd1, 2'h1, 2 }; // for fun
    assign n = nbits[i];

endmodule

```

