

Common Circuits

Exercise 1: Draw the block diagram for the Verilog above.

```
// resetable clock divider
```

```
assign count_next
```

```
= reset ? period-1 :
```

```
count ? count - 1'b1 : period-1 ;
```

```
always_ff @(posedge clk) count = count_next ;
```

```
// latch a '1 first time count reaches zero
```

```
assign timeout_next
```

```
= reset ? '0 :
```

```
count ? timeout : '1 ;
```



```
always_ff @(posedge clk) timeout = timeout_next ;
```

```
// periodic signal
```


```
assign enable_next
```

```
= count_next ? '0 : '1 ;
```





```
always_ff @(posedge clk) enable = enable_next ;
```

 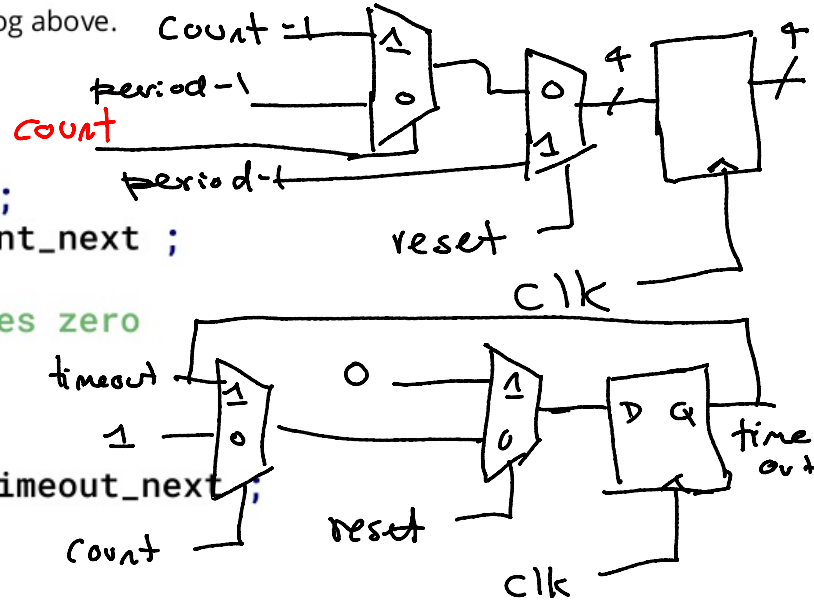


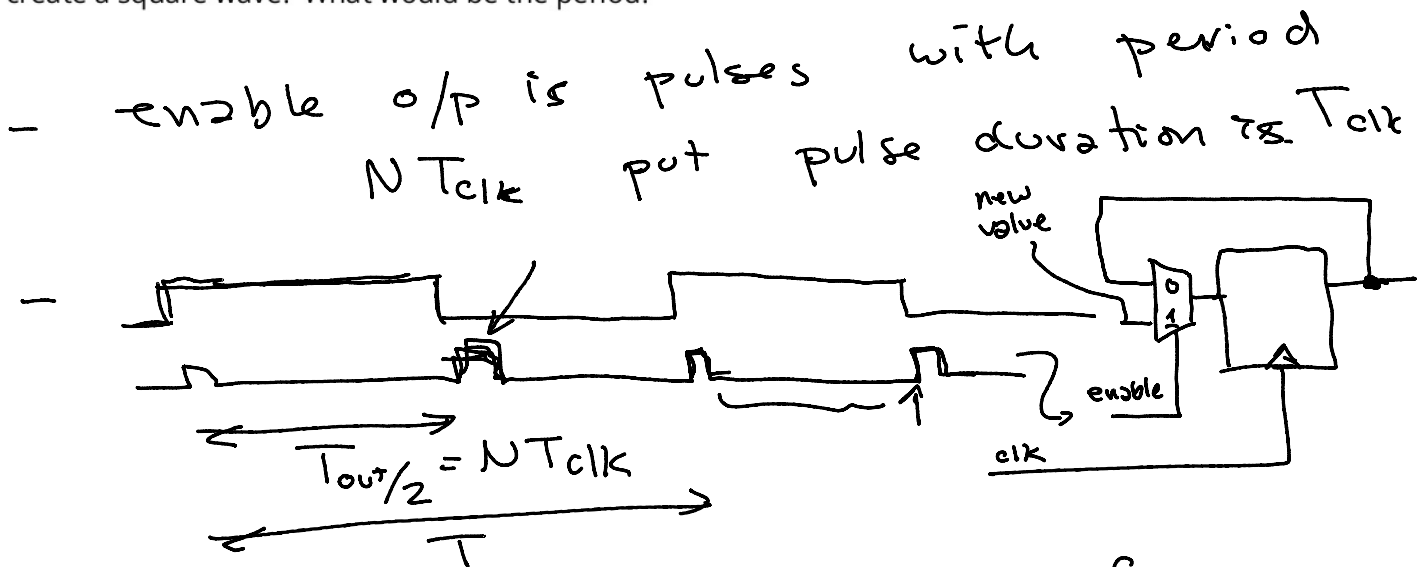
Exercise 2: Is the enable output a square wave? How could you create a square wave? What would be the period?



    
- period would be $2 N T_{clock}$ if toggle o/p on each enable



enable

  
 
$$\frac{1}{100 \text{ Hz}} = 10 \text{ ms}$$



$$20 \text{ ns} = \frac{1}{50 \text{ MHz}}$$

$$\begin{aligned} \frac{10 \text{ ms}}{20 \text{ ns}} &= \\ \frac{10 \times 10^{-3}}{20 \times 10^{-9}} &= \\ &= 0.5 \times 10^6 \\ &= 500,000 \end{aligned}$$



Exercise 3: How would the output differ if enable_next was based on count rather than count_next?

it would be delayed by 1 clock period

Exercise 4: What is the duration of the sig_rising output?

1 clock period.

Exercise 5: How would you detect a falling edge?

  

Exercise 6: Draw the schematic of a synchronizer.



Exercise 7: What is the bounce duration in the waveform above?
What value of N would achieve a delay of ten times this with a 50 MHz clock?

≈ 1 ms.

10 ms with 20 ns clock period.

$$\frac{10 \text{ ms}}{20 \text{ ns}} = \frac{10 \times 10^{-3}}{20 \times 10^{-9}} = 0.5 \times 10^6$$

N = 500,000 clock cycles.