
## Solutions to Review Lecture II

## **State Machines**

The inputs are from two pushbuttons (start and stop) and from the timer circuit (time). The outputs to control the motor are run and slow and the output to control the timer is reset. The controller can be in three states: OFF, SLOW and FAST and the output values for each state are:

State	run	slow	reset
OFF	0	0	0
SLOW	1	1	1
RUN	1	0	0

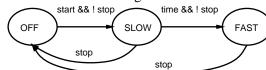The state transition diagram is as follows:



and it can be summarized in tabular form as:

Starting	Input			Next
State	stop	start	time	State
OFF	0	0	X	OFF
OFF	0	1	X	SLOW
OFF	1	X	X	OFF
SLOW	0	X	0	SLOW
SLOW	0	X	1	FAST
SLOW	1	X	X	OFF
FAST	0	X	X	FAST
FAST	1	X	X	OFF

## **C Programming**