 


## HDL Synthesis Idioms

**Exercise 1:** Using the schematic symbols shown below, convert each of the following System Verilog expressions into a schematic.


$$y = a \wedge b ;$$




$$y = a < b ;$$



$$y = y+1 ;$$

 



$$y = a[3] ;$$

 

$$y = a[3] ? 4 : a[2] ? 3 : a[1] ? 2 : a[0] ? 1 : 0;$$



$$y = \text{table}[x] ;$$

  



$$\text{if } (y < b)$$

$$y = y+1 ;$$

else


$$y = y-1 ;$$

$$y = oe ? d : 16'hzzzz ;$$

 
 


**Exercise 2:** Using the schematic symbols shown above, convert each of the following System Verilog expressions into a schematic.


always@(posedge clk)  
y <= a ;

 

  
always@(posedge clk)  
y[7:0] <= {y[6:0], a} ;



 
always@(posedge clk)  
if ( e )  
y <= a ;  
else  
y <= y ;



 
always@(posedge clk)  
if ( r )  
y <= '0 ;  
else  
if ( e )  
y <= y+1'b1 ;  
else  
y <= y ;



```
next = ( reset || done ) ? '0 : cnt+'b1 ;
```

 

 
```
always@(posedge clk)
  if ( falling )
    mosi <= sr[31] ;
```





```
always@(posedge clk)
```

```
  cnt <= cnt_next ;
```

 


```
// logic [31:0] mem [15:0]
```

  
```
always_ff@(posedge clk) begin
  mem[p] <= din ;
```



 
```
p_next = (valid && rdg) ? p + 1'b1 : p ;
```



 
```
// i, j are logic[4:0]; w, sclk are logic
nxt = w ? 5'd7 : ( j==N && sclk ) ? i-1 : i ;
```



 
```
readdata = {31'b0,csn} ; // csn is logic
```



 
```
crc = ~ (g&sr) ; // g and sr are logic[31:0]
```



```
nxt = ~d[8] ;
```

 

 **Exercise 3:** Write System Verilog that would generate each of the following schematics. Include any required signal declarations (using logic).




```

logic [2:0] x, y;
logic [2:0] z;

z = x != y;

if (x != y)
    z = '1;
else
    z = '0;


```

 

```

logic [2:0] c;
d = {1'b0, c} + 1'b1;
d = c + 4'b1;

```

 

always @ (posedge clk)


$$c \leftarrow \text{rom}[s]$$

```

assign r = c[0];
" h = c[1];
" g = c[2];



```

$r \leftarrow \text{rom}[s][0]$

 


$$\{a, b, c, d\} = 4'b1 \ll x;$$


$$ab = \text{oen} ? 16'bz : \sim a;$$

  

 always @ (posedge clk)  
 $q \leftarrow d;$



(see below)

 


logic [7:0] q, d;

always\_comb  
if ( $q < 125$ )  
 $d = q + 1;$   
else  
 $d = 0;$

always\_ff @ (posedge clk)

$q \leftarrow d;$

 

always\_comb


$d = h ? q[i] : (1 ? p[i] : q[i]);$

always\_ff @ (posedge clk)

$q \leftarrow d;$

FF with Synchronous set/reset inputs:

logic [3:0] q, q-n, s, d, r;

 


always-comb  
for (int i=0; i<4; i++)  
if (s[i]) //set has priority  
q-next[i] = 1;  
else if (r[i])  
q-next[i] = 0;  
else  
q-next[i] = d[i];

always\_ff @ (posedge clk) begin  
q <- q-next;  
q-n <- ~q-next;  
end;

asynchronous set / reset (not recommended):

always @ (s, r, clk)

 for (int i=0; i<4; i++)  
if (s[i] && !r[i]) q[i] = 1;  
else if (r[i] && !s[i]) q[i] = 0;  
else if (posedge clk) q[i] = d[i];



always-comb

```
if (c > 12)
    d = 0;
```

else


```
if (c < 4)
    d = 1;
```

else

```
d = ud;
```


always ff @ (posedge clk)

```
ud <= d;
```

 

always-comb

```
d = ud ? c+1 : c-1
```

 

always ff @ (posedge clk)

```
c <= d;
```

always-comb begin

```
for (int i=0 ; i<N-1 ; i++)
    d[i+1] = q[i];
```

```
d[0] = sin;
```

end;

always ff @ (posedge clk)

```
q <= d;
```

assign sout = q[N-1];