

ELEX 7660 : Digital System Design  
Term 201810

MIDTERM EXAMINATION - PART 2  
12:30 AM – 1:20 PM  
February 23, 2018

*This exam has two (2) questions on four (4) pages. The marks for each question are as indicated. There are a total of 14 marks. Answer all questions. Write your answers and all rough work in this paper and nowhere else. Show your work. Books and notes are allowed. No electronic devices other than calculators are allowed.*

This exam paper is for:

Exam 1 A00123456

Each exam is equally difficult.  
Answer your own exam.

Do not start until you are told to do so.

Name: \_\_\_\_\_


BCIT ID: \_\_\_\_\_

Signature: \_\_\_\_\_

Question	Mark	Max.
1		9
2		5
Total		16

 **Question 1 (9 marks)**


Write a System Verilog module that models the schematic shown below on the facing page. Use logic signal types throughout. Include all code from module to endmodule. Where the order of declarations or statements is not significant you may use any order.





Question 2 ( 9 marks)

Using the following symbols:

 

draw a schematic for the following Verilog module on the facing page. Label the inputs and outputs. Indicate the bus width if it's more than 1 bit.

```
module fract
  ( input logic [7:0] d, thr,
    output logic limit,
    input logic reset, clk ) ;

  logic [15:0] cnt, cnt_next ;

  always_comb begin
    if ( reset )
      cnt_next = '0 ;
    else
      if ( d > thr )
        cnt_next = cnt + 1 ;
      else
        cnt_next = cnt ;
  end

  always@(posedge clk)
    cnt <= cnt_next ;

  assign limit = cnt >= 16'h1000 ;

endmodule
```



- This page intentionally left blank. -

ELEX 7660 : Digital System Design  
Term 201810

MIDTERM EXAMINATION - PART 2  
12:30 AM – 1:20 PM  
February 23, 2018

*This exam has two (2) questions on four (4) pages. The marks for each question are as indicated. There are a total of 14 marks. Answer all questions. Write your answers and all rough work in this paper and nowhere else. Show your work. Books and notes are allowed. No electronic devices other than calculators are allowed.*

This exam paper is for:

Exam 2 A00123456

Each exam is equally difficult.  
Answer your own exam.

Do not start until you are told to do so.

Name: \_\_\_\_\_


BCIT ID: \_\_\_\_\_

Signature: \_\_\_\_\_

Question	Mark	Max.
1		9
2		5
Total		16

 **Question 1** (9 marks)

Write a System Verilog module that models the schematic shown below on the facing page. Use logic signal types throughout. Include all code from module to endmodule. Where the order of declarations or statements is not significant you may use any order.








Question 2 ( 9 marks)

Using the following symbols:

 

draw a schematic for the following Verilog module on the facing page. Label the inputs and outputs. Indicate the bus width if it's more than 1 bit.

```
module accum
  ( input logic [7:0] d,
    output logic limit,
    input logic reset, clk ) ;

  logic [7:0] sum, sum_next ;

  always_comb begin
    if ( reset )
      sum_next = '0 ;
    else
      if ( d > 7'd127 && sum < 200)
        sum_next = sum + 1 ;
      else
        sum_next = sum ;
    end

  always@(posedge clk)
    sum <= sum_next ;

  assign limit = sum >= 200 ;

endmodule
```



- This page intentionally left blank. -