EECE251 Circuit Analysis Set 2: Methods of Circuit Analysis

Shahriar Mirabbasi Department of Electrical and Computer Engineering University of British Columbia shahriar@ece.ubc.ca

1

Reading Material

- Chapter 3 of the textbook
 - Section 3.1: Nodal analysis
 - Section 3.2: Loop analysis (and mesh analysis which is a special case of loop analysis)

Methods of Circuit Analysis

- Two popular and powerful techniques for analyzing circuits are:
 - Nodal analysis: a general procedure to find all the node voltages in a circuit. It is based on KCL and Ohm's Law.
 - Mesh analysis: another general approach to find mesh currents which circulate around closed paths in the circuit. It is based on KVL and Ohm's Law.
- Yet there is another more general! and powerful! technique which we call:
 - Modified Nodal Analysis (MNA)
 - Though more powerful it is not as popular of the first two (Almost all books don't even have it!)

Definitions (Recall)

- These are standard textbook definitions (for node the definition is slightly different from what we saw in slide set 1!)
 - Node: A point of connection of two or more circuit elements.
 A node can be spread out with perfect conductors (wires)
 - Branch: A portion of the circuit containing only a single element and the nodes at each end of the element (not that we are assuming that the elements have two terminals!)
 - Loop: Any closed path through the circuit in which no node is encountered more than once.

More Terminology

- **Reference node or ground:** a node that is assumed to have a zero potential.
 - If the reference node is not explicitly indicated on the circuit one can arbitrarily choose any node as the ground. We will soon see how to choose a good ground node.

• **Node voltage** is the voltage difference/drop from a given node to the reference node.

Regular Nodal Analysis

- Steps to determine the node voltages for a circuit with <u>no</u> <u>floating voltage source</u>:
- 1. Select a reference node. A floating voltage source is a voltage source that neither of its terminals is connected to the reference node.
- 2. Assign voltages to other nodes. These node voltages are referenced to the reference node.
- 3. Write KCL for all <u>unknown</u> non-reference nodes. When possible use Ohm's law to relate the branch currents to node voltages
- 4. Solve the resulting system of equations for unknown node voltages.

Nodal Analysis Example

• Let's analyze the following circuit using nodal analysis:



7

Nodal Analysis

• Consider node a:



$$G_1 V_a + G_2 (V_a - V_b) + G_5 (V_a - V_{in}) - I_s = 0$$

 $(G_1 + G_2 + G_5) V_a - G_2 V_b = I_s + G_5 V_{in}$

• Consider node b:

$$V_{a} \underbrace{\bigvee_{V_{b}} G_{4}(V_{b} - V_{in})}_{G_{2}(V_{b} - V_{a})} \underbrace{\bigvee_{V_{b}} G_{4}(V_{b} - V_{in})}_{G_{2}(V_{b} - V_{a})} = 0$$

$$G_{2}(V_{b} - V_{a}) \underbrace{\bigvee_{V_{b}} G_{3}V_{b}}_{G_{3}V_{b}} -G_{2}V_{a} + (G_{2} + G_{3} + G_{4})V_{b} = G_{4}V_{in}$$

$$\begin{bmatrix}G_{1} + G_{2} + G_{5} & -G_{2} \\ -G_{2} & G_{2} + G_{3} + G_{4}\end{bmatrix} \begin{bmatrix}V_{a} \\ V_{b}\end{bmatrix} = \begin{bmatrix}I_{s} + G_{5}V_{in} \\ G_{4}V_{in}\end{bmatrix}$$

• Write the nodal analysis equations that lead to solve the following circuit.



Floating Voltage Sources

• Problem: The current through the floating voltage source cannot be written as function of its two terminal voltages!



• Solution: Form a supernode which is formed by enclosing the floating voltage source (independent or dependent) and any elements in parallel with it in a closed boundary.

Floating Voltage Sources

- Since there are two nodes (two terminals of the floating voltage source) are enclosed in the supernode, two equations are needed for each supernode:
 - KCL at supernode gives one equation
 - The other equation is the relationship between the voltages of the two nodes enclosed in the supernode
- For example for the supernode in the previous slide we can write the following two equations:

$$-3 + 0.15(V_b - V_a) + 0.05V_b + 0.25V_c - 25 + 0.2(V_c - V_a) = 0$$

 $-V_b + V_c = 440$

Nodal Analysis Example



• KCL at Node a:

 $8 + 0.15(V_a - V_b) + 3 + 0.2(V_a - V_c) = 0$

• For the supernode we have:

$$-3 + 0.15(V_b - V_a) + 0.05V_b + 0.25V_c - 25 + 0.2(V_c - V_a) = 0$$

 $-V_b + V_c = 440$



Loop and Mesh Analysis

- Mesh analysis is a special case of a more general technique called loop analysis.
- A mesh is a loop that does not contain any other loops within it.
- Mesh analysis is not quite as general as nodal analysis since it can only be applied to planar circuits
- A planar circuit is a circuit that can be drawn in a plane with no branches crossing one another.
- Example of non-planar circuits:



Note

- Number of linearly independent loops:
 - In a circuit with B branches and N nodes there are B-N+1 linearly independent loops!
 - Number of linearly independent loops is equal to the number of meshes!
- Find the number of linearly independent loops in the following circuit: 4Ω 3V



Mesh (Loop) Analysis

- Steps to calculate mesh (loop) currents for a given circuit in which no current source is shared between two meshes:
- 1. Assign mesh (loop) currents to each mesh (loop)
- 2. Write KVL for each of the meshes (loops) and use Ohm's law to express the voltages of the elements in the mesh (loop) in terms of mesh (loop) currents
- 3. Solve the resulting systems of linear equations for unknown mesh (loop) currents

Mesh Analysis Example



• For mesh 1:

 $28 = I_1 + 4(I_1 - I_2) + 12 + (I_1 - 8) = 6I_1 - 4I_2 + 4 \quad \text{or} \quad 6I_1 - 4I_2 = 24$

• For mesh 2:

 $0 = 4(I_2 - I_1) + 2I_2 + 2(I_2 - 8) = -4I_1 + 8I_2 - 16 \quad \text{or} \ -4I_1 + 8I_2 = 16$

• Mesh 3? $\begin{bmatrix} 6 & -4 \\ -4 & 8 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 24 \\ 16 \end{bmatrix}$

17

• In the following circuit, use mesh analysis to find I_o :



• In the following circuit, find I_o.



Mesh Analysis

- Steps to calculate mesh (loop) currents for a given circuit in which some current sources are shared between two meshes:
- 1. Assign mesh currents to every mesh in the circuit.
- 2. Define a supermesh when two (or more) meshes have a (dependent or independent) current source(s) in common.
- 3. Write KVL for each regular mesh.
- 4. Apply both KVL and KCL to suppermeshes.
- 5. Solve the resulting system of equations.

• In the following circuit, find the mesh currents:



• Write the mesh equations for the following circuit:



Notes

 In the following circuit, find I_o. Use two techniques: 1) mesh analysis and 2) loop analysis.



• In the following circuit, use mesh analysis to ginf V_o .



• Use a technique of your choice to solve for



SM

Modified Nodal Analysis

- **Recall:** The following definitions of nodes (and branches) slightly differ from traditional textbook definitions! Please note that almost all components that we deal with in this course are two-terminal components (resistors, sources, ...)
- A "**true node**" (or node for short) is the point of connection of three or more circuit elements. (The node includes the interconnection wires.)
- A "**binary node**" (or b-node for short) has only two components connected to it.
- A "**branch**" is a collection of elements that are connected between two "**true nodes**" that includes only those two true nodes (and does not include any other true nodes).

Modified Nodal Analysis

- For modified nodal analysis (MNA) we need some more definitions!
- We identify four general types for branches as follows: (we have seen these before, and here we are just formalizing them by giving them proper names!):
 - R branch
 - RV branch
 - I branch (this also include any branch that consist of a current source in series with other components)
 - V branch (also known as evil branch!)

Let's see if we can calculate the current of these branches based on the end-point node voltages!

R Branch

 A branch that consist of only a resistor (or series combination of resistors that can be represented by their equivalent resistors)



• How about the current in the other direction!



RV Branch

 A branch that consist of a resistor (or series combination of resistors that can be represented by their equivalent resistors) in series with a voltage source (or a series combination of voltage coursed that sources that can be represented by their equivalent voltage source)

- How about the current in the other direction?
- What if the polarity of the voltage source is reversed?



I Branch

• I branch: A branch that consists of only a current source!



 Another example of I branch (some times called IR branch): A branch that consists of a resistor (or equivalent resistor) in series with a current source:



V Branch (Evil Branch)

• A branch that consists of only one voltage source:



• However, the good news is:

- $V_{s} = V_{a} V_{b}$
- Note: The sources in V, RV, I, and RI branch can be either dependent (controlled) or independent sources.

Modified Nodal Analysis (MNA)

- A general technique to solve a circuit (i.e., to find voltage, current and power of every element in the circuit).
- <u>Unknowns</u>:
 - 1) controlling variables (for dependent sources)
 - 2) current in V branches (evil branches)
 - 3) voltage of each true node
- <u>MNA steps</u>:
- 1. Identify every true node of the circuit.
- 2. Choose one of them as a reference node (node whose voltage is zero).
- 3. Write one equation per controlling current or voltage of dependant sources.
- 4. Write the relationship between the two nodes of the V branch.
- 5. Write one KCL per true node.

• Use modified nodal analysis to find I_o in the following circuit:



• In the following circuit, find V_o.



Example (MNA)

• Solve the following circuit using MNA.



Notes