

## Modulo- $n$ Counters

### Introduction


Counters whose values “wrap around” back to zero when they reach the value  $n$  are called modulo- $n$  counters.

The most common example is a modulo-10 counter that counts from 0 up to 9 and then “wraps around” back to 0. We can build a multi-digit binary-coded decimal (BCD) counter using one modulo-10 counter for each digit.

In this lab you will design a single-digit modulo- $n$  counter and instantiate four instances of your module to create a four-digit counter whose digits will display on the multiplexed LED display used in previous labs. The value of  $n$  will depend on your student ID.

 
### Modulo Counter Specifications

Your counter must have single-bit **reset**, **enable** and **clock** inputs, a 4-bit **count** output and a one-bit **carry** output:



The counter is synchronous. This means **count** changes on the rising edge of the clock. It is set to zero if **reset** is asserted, otherwise it is incremented if **enable** is asserted, otherwise it does not change. If **count** is incremented when its value is  $n-1$  it becomes 0. **carry** is a combinational logic outputs that is asserted only when **enable** is asserted and **count** is  $n-1$ .

 The **carry** output allows counters to be combined into a multi-digit counter by connecting the **carry** output of one digit to the **enable** input of the next-most-significant digit:



Note that **enable** is not a clock and **count** does not necessarily change in each clock cycle.

The modulo value,  $n$ , to use in your design depends on the last digit of your student ID as shown in the table below. For example, if your ID were A00123456 you would design a modulo-7 counter.

last digit of ID	$n$
0, 1, 2	5
3, 4, 5	6
6, 7	7
8, 9	9

### Components

You will use the same four-digit 7-segment LED display, 200  $\Omega$  current-limiting resistors and keypad as in previous labs.

### Procedure

Design a modulo- $n$  counter that meets the specifications above.

Download the **lab5.qar** project archive file from the course web site. This project archive includes a complete project except for the Verilog code in the file **modncount.sv**.


Open the archive file with Quartus and restore it to a convenient folder. Add your modulo- $n$  counter code to **modncount.sv**. Do not rename the signals in the **modncount** module declaration. Change the pin assignments, if necessary, to match your circuit layout. Compile your design, program the FPGA and test it.

The project contains an **.sdc** file that defines the clock frequency (50 MHz) and the I/O signals as asynchronous. This allows Quartus to verify that your design operates at a 50 MHz clock frequency.

The test circuit instantiates four of your modulo- $n$  counters as shown above and displays the count on the 4-digit LED display. The **1** key increments the count at 5 Hz, the **2** key at 50 Hz and the **3** key at 500 Hz. Pushing the **A** key resets the counters.
 
## FPGA I/O

The connections to the FPGA are shown in the following diagram:



The keypad and LED pin assignments in the supplied project are the same as in the previous lab. The keypad inputs have internal pull-up resistors configured. The pin assignments are shown below:


To	Assignment Name	Value
out a	Location	PIN_49
out b	Location	PIN_65
out c	Location	PIN_54
out d	Location	PIN_50
out e	Location	PIN_46
out en[3]	Location	PIN_51
out en[2]	Location	PIN_69
out en[1]	Location	PIN_67
out en[0]	Location	PIN_60
out f	Location	PIN_71
out g	Location	PIN_58
out row[3]	Location	PIN_103
out row[2]	Location	PIN_100
out row[1]	Location	PIN_98
out row[0]	Location	PIN_86
in col[3]	Location	PIN_84
in col[2]	Location	PIN_80
in col[1]	Location	PIN_76
in col[0]	Location	PIN_74
in clk50	Location	PIN_23
in col	Weak Pull-Up Resistor	On

## Submission

To get credit for completing this lab, submit the following to the Assignment folder for this lab on the course website:

 1. A PDF document containing:
  - A block diagram of your modulo- $n$  counter.

- A listing of your `modncount.sv` file (but not `lab5.sv`).
- A screen capture of your compilation report.
- The schematic created by **Tools > Netlist Viewers > RTL Viewer**, clicking on the + button on the `modncount:m[0].m` block to expand it, and then **File > Export...** It may look like:



Note that this is the schematic of one of your modulo- $n$  counters, not of the complete design.

2. If you do not demonstrate your design in the lab, a video of the display and keypad showing:

- the count being reset when **A** is pushed
- holding down **1** makes the rightmost digit increase, wrap-around at the correct value and increment the next most-significant digit,
- the other digits also wrapping and carrying when **2** and **3** are pressed,
- the counts being reset when **A** is pushed.

A sample video is available on the course website.