 


Introduction to Digital Design with Verilog HDL

Exercise 1: What changes would result in a 3-input OR gate?

```
// AND gate in Verilog  
module ex1 ( input logic a, b, c,  
            output logic y ) ;  
  
] assign y = a | b | c ;  
  
endmodule
```

Exercise 2: What schematic would you expect if the statement was
assign y = (a ^ b) | c ;?




Exercise 3: If the signal *i* is declared as logic [2:0] *i*;, what is the 'width' of *i*? If *i* has the value 6 (decimal), what is the value of *i*[2]? Of *i*[0]?

2:0 is 3 bits wide (indices 2, 1, 0)

6 in binary would be $\overset{i[2]}{\uparrow} 1 \overset{i[1]}{\uparrow} 1 \overset{i[0]}{\uparrow} 0$

$\therefore i[2] = 1$
 $i[0] = 0$

Exercise 4: Use slicing and concatenation to assign y the value of the byte x with its nybbles swapped.

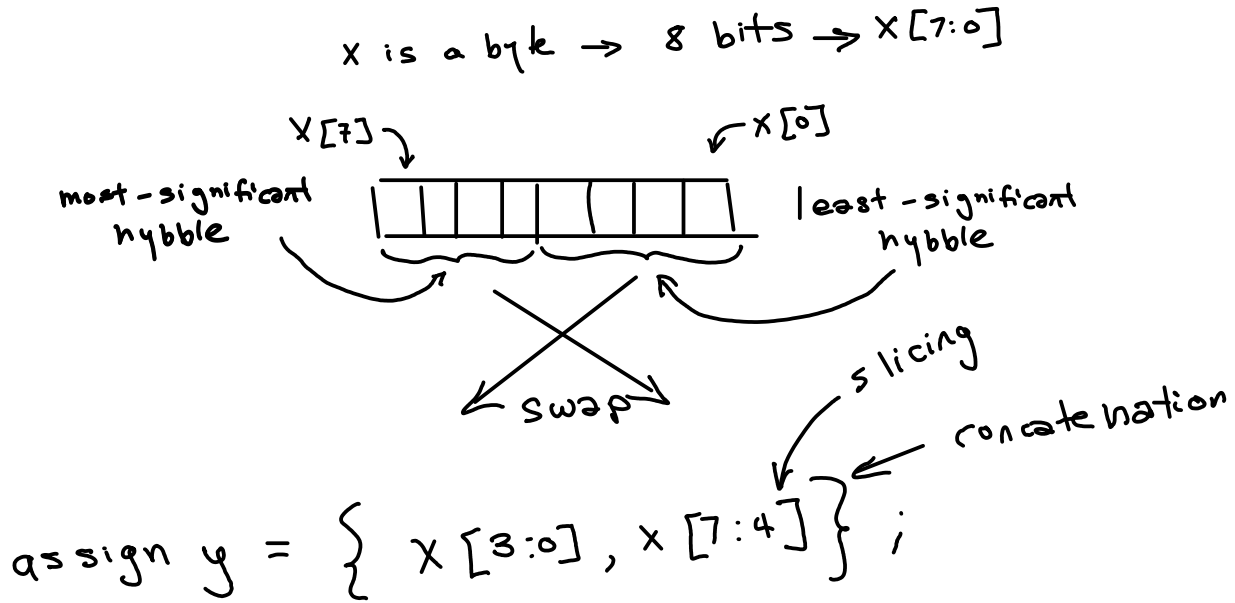


Exercise 5: What is the value of the expression 3 ? 10 : 20? Of the expression x ? 1 : 0 if x has the value 0? If x has the value -1?

3 is non-zero & therefore "true"
 3 ? 10 : 20 has value of 10

x ? 1 : 0 has value 0 if x is 0
 (0 ? 1 : 0)

x ? 1 : 0 has value 1 if x is -1
 (-1 ? 1 : 0)
 -1 is non-zero

Exercise 6: Draw the schematic corresponding to: $y = a ? (b ? s1 : s2) : (c ? s3 : s4)$

 

Exercise 7: Write a Verilog description of a 4-bit 3-to-1 multiplexer controlled by a 2-bit sel input? Label the inputs a (for sel=00) through c (for sel=10).

```

assign y = sel == 2'b00 ? a :
           sel == 2'b01 ? b :
           sel == 2'b10 ? c : ??? ;

```

output for sel == 2'b11 not defined in the question.

Exercise 8: What are the sizes and values, in decimal, of the following: 4'b1001, 5'd3, 6'h0_a, 3?

	<u>width</u>	<u>value</u>
4'b1001	4	$1001_2 = 9_{10}$
5'd3	5	$3_{10} = 3$
6'h0_a	6	$0A_{16} = 10_{10}$
3	32 ↑ default	$3_{10} = 3$