
 


## State Machines

### Exercise 1:

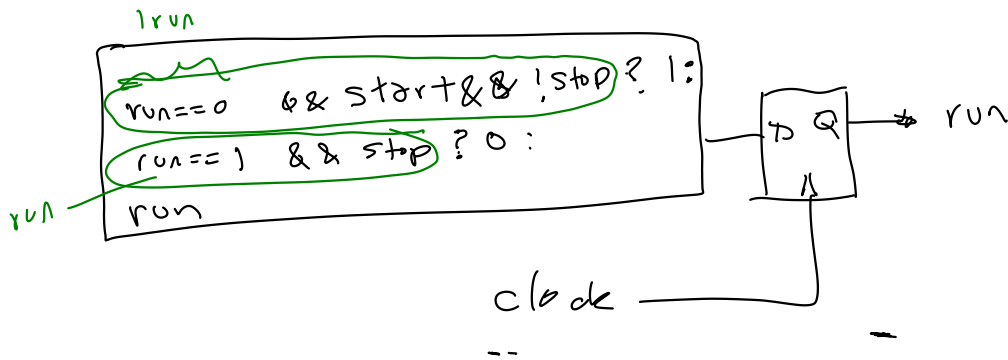

Draw the schematic for this state machine. Write an `always_ff` statement that implements this state machine.



```

always_ff @(posedge clk)
  run <= run == 0 && start && !stop ? 1 :
    (run == 1) && stop ? 0 :
    run;
  
```

**Exercise 2:** Simplify the solution using the fact that addition of 1 to 3 “wraps” a 2-bit value to 0. What would you change so the counter does not “wrap around” from 2'b11 to 2'b00?

```

module ex56
  ( output logic [1:0] count,
    input logic reset, clk );

  always_ff @(posedge clk) count
    <= reset ? 2'b00 :
      count == 2'b11 ? 2'b00 :
      count + 1'b1 ;

endmodule
  
```

remove line  
if counters "wrap around"  
use 2'b11 for count "saturating"  
at 2'b11.

**Exercise 3:** What value of  $N$  would give a 20 ms delay if the clock frequency is 50 MHz? How many bits are needed for this timer's register?

$\overbrace{\hspace{10em}}^{20\text{ms}}$

$N = \frac{20\text{ms}}{20\text{ns}} = \frac{10^{-3}}{10^{-9}} = 10^6$

$f_{\text{clock}} = 50\text{MHz}$   
 $T_{\text{clock}} = \frac{1}{f_{\text{clock}}} = \frac{1}{50 \times 10^6} = 20\text{ns}$


$999,999 \rightarrow 0$

$2^m \geq 999,999$   
 $m \geq \log_2(10^6)$   
 $19.9 \text{ (20)}$


$2^{10} \rightarrow 1024$   
 $2^{20} \rightarrow (1024)^2 \approx 10^6$   
 $2^{30} \approx 10^9$   
 $2^{40} \approx 10^{12}$

**Exercise 4:** Assume the timer above is reset to  $N - 1$  each time it reaches 0. For how long is the register value 0? What are the period and frequency of a signal that is inverted each time the count reaches 0?

it's 0 for 1 clock period


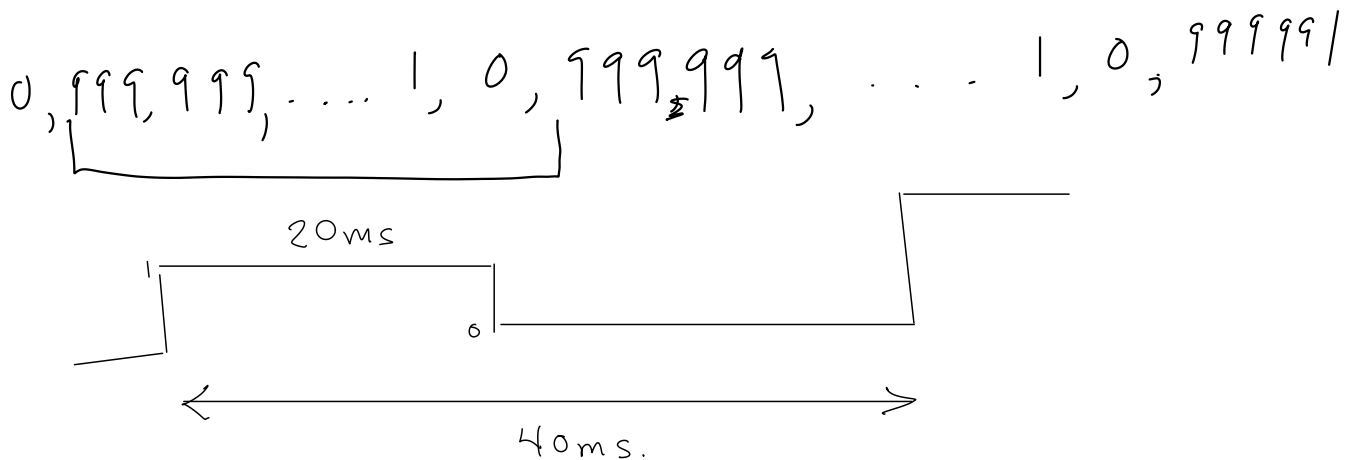


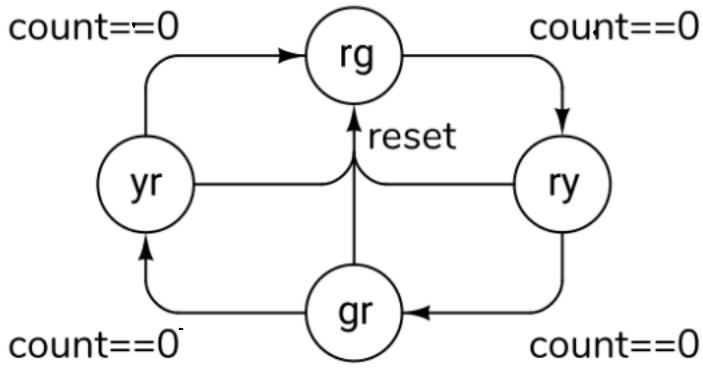**Exercise 5:** Write the state transition table for the state machine for the lights output.



current state (lights)	inputs		next state (next lights)
	reset	count	
X	1	X	rg }
rg	0	0	ry }
ry	0	0	gr }
gr	0	0	yr }
yr	0	0	rg }
S	0	≠ 0	S } no change

  **Exercise 6:** The example above is an N-bit shift register that shifts the bits right. Draw a block diagram and write the Verilog for a 6-bit shift register that shifts left.




```
module (input logic in, clk,
        output logic [5:0] q);
```

```
always_ff @(posedge clk)
    q <= {q[4:0], in};
```


```
endmodule
```

**Exercise 7:**

 

Fill in the diagram above for a 4-bit ( $N = 4$ ) right-shift shift register. Assume the initial value is zero. Which bit is the oldest (first) value in the ~~Q~~ waveform? Which bit of the shift register holds the oldest value?  $in$

 **Exercise 8:** Draw a block diagram and write the Verilog for a circuit that sets an output named **detect** high when the sequence of values 1, 1, 0, 1 has appeared on an input named **in** on successive rising edges of the clock.




```

module detector (
    input logic in, clk,
    output logic detect);
    logic [3:0] q;
    always_ff @(posedge clk)
        q <= {in, q[3:1]};
    assign detect = q == 4'b1011;
endmodule;
    
```

 **Exercise 9:** For which states would **falling** be asserted? **rising**?  
 Draw the schematic and write the Verilog for this state machine.  
 Assume an input **in** and a 2-bit register **bits** that holds the two most recent input values.

S.r. shifts left  
 falling asserted for 1 followed by 0 : state = 10  
 rising for state = 01



```
module edge-detector (
  input logic in, clk,
  output logic rising, falling);
```

```
  logic [1:0] bits;
```

```
  always_ff @(posedge clk)
    bits <= { q[0], in };
```

```
  assign rising = bits == 2'b01;
```

```
  assign falling = bits == 2'b10;
```


```
endmodule
```

**Exercise 10:** How could you modify the code so that **digits** is only updated when an **enable** input is asserted?

```
always_ff @(posedge clk) digits
```

```
← { digits[1:3], digit } ;
```

```
← enable ? { digits[1:3], digit } : digits ;
```

 


**Exercise 11:** How many states can this state machine have?

$$16 \times 16 \times 16 \times 16 = (2^4)^4 = 2^{16}$$

16 bits  $\rightarrow$   $2^{16}$  possible values (states)

(if constraint digit to 0-9 then  $10 \times 10 \times 10 \times 10 = 10^4$  possible states).

 **Exercise 12:** Draw the state transition diagram for this simpler implementation. How many states are there? Write the Verilog using a 3-bit **count** state variable.




5 states (0-4)

**Exercise 13:** Write `always_ff` statements that implement these two state machines.

count	in == out	next count
x	1	N-1
0	x	N-1
n	0	n-1


or:  $X \quad 0 \quad \text{count}-1$

 

N-1	0	N-2
N-2	0	N-3
	0	
	0	
4	0	3
3	0	2
2	0	1
1	0	0

`always_ff @(posedge clock)`
 
`count <= in == out ? N-1 :`  
`count == 0 ? N-1 :`  
`n-1;`



`always_ff @(posedge clock)`


`out <= count == 0 ? in :`  
`out;`

**Exercise 14:** What is the size of the expression `sqrt*sqrt`? Of `{8'b0, sqrt}*sqrt`?

↳ 16

↳ 8

**Exercise 15:** Draw the state transition diagram for `done`.

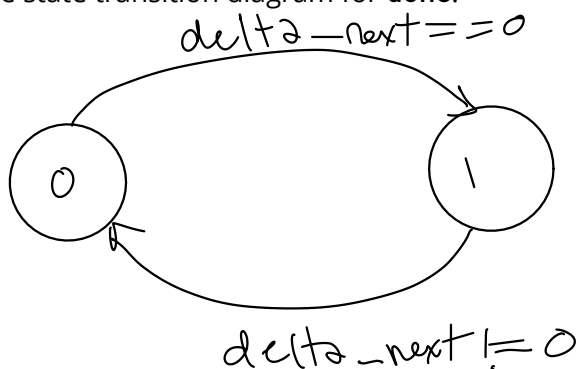

**Exercise 16:** If we used 8-bits of state information, how many states could be represented? What if we used 8 bits of state but used a "one-hot" encoding?

with 8 bits   
 ↳ binary encoding:  $2^8$    
 ↳ one-hot encoding: 8

```

0000 0000
0000 0001
0000 0010
...
1111 1111

1000 0000
0100 0000
0010 0000
...
0000 0001
  
```