


## More Verilog

**Exercise 1:** Is a signal named  $\overline{\text{overload}}$  active-high or active-low? Is there an overload if this signal is high? What if the signal was named **overload**?

**Exercise 2:** Come up with active-high and an active-low names for a signal that is at 3 V when a door is open and 0 V when the door is closed.

**Exercise 3:** If  $\bar{D}$  is a word and  $\overline{D\emptyset}$  is low, is the word an even or odd number?

**Exercise 4:**

 

Draw a diagram for this instantiation of the **bits** module. Label the module, instance, signal and port names as in the diagram above.

## Exercise 5:

```
module sr3bytes
(
  input logic [7:0] newest,
  output logic [7:0] oldest,
  input logic clock
) ;

localparam nbits = 8 ;

logic [nbits-1:0] a, b ;

// matching by order
bits #(nbits) b0 (newest,a,clock);

// matching by name (order does not matter)
bits #(.nb(nbites)) b1 (.q(b),.clock,.d(a));

// wildcards for names that match
bits #(.nb(nbites)) b2 (.d(b),.q(oldest),.*);

endmodule
```

Identify the module instantiation statements in the code above. For each one, what is the instantiated module's name? The instance name?

**Exercise 6:** What are the values of the following expressions: `|4' b0001,`  
`^4' b1001, &4' b1111, &4' b1110?`

### Exercise 7:

```
// concatenation:  
logic [3:0] x = { 2'b00, 2'b11 } ;  
// array literal:  
logic [3:0] x[2] = '{ 4'b0011, 4'b1010 } ;  
// replication within literal:  
logic [3:0] x[2] = '{2{ 2'b00, 2'b11 }} ;
```

What are the initial values of x in the examples above?