

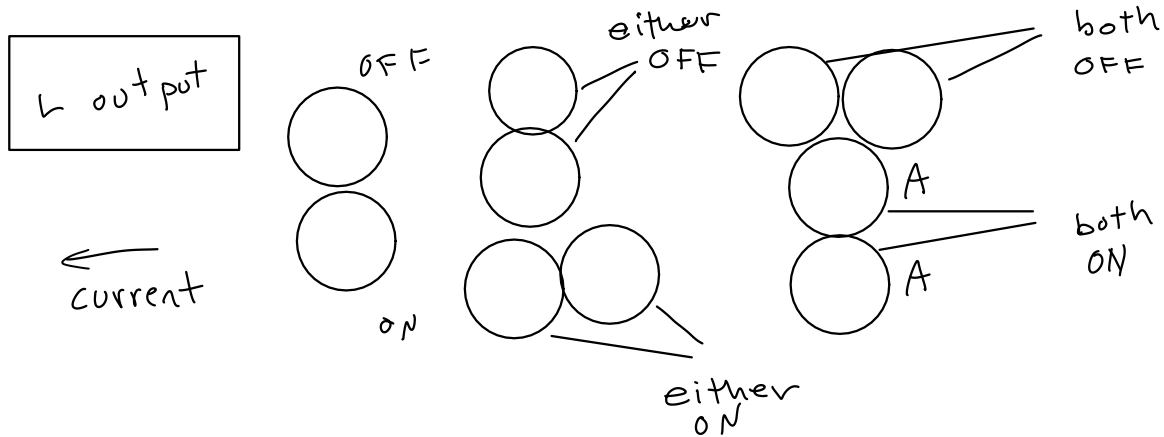


Implementation of Digital Logic Circuits


Exercise 1: Which transistors are on when the output is high? When it is low? In which direction does the output current flow in each case?

 

Exercise 2: Which of these specifications does the manufacturer guarantee? Which are requirements?

 

 Exercise 3: A logic family has $V_{OH}(\min) = 5\text{ V}$, $V_{OL}(\max) = 0.5\text{ V}$, $V_{IH}(\min) = 4\text{ V}$ and $V_{IL}(\max) = 1.5\text{ V}$. What are the noise margins?



Exercise 4: All else being equal, by how much would we expect to decrease power consumption when reducing logic levels from 5 V to 3.3 V? What would be the effect on power consumption in reducing the clock frequency from 50 MHz to 1 MHz?

$$\frac{P_2}{P_1} = \frac{f_2}{f_1} \left(\frac{V_2}{V_1} \right)^2 \quad f_2 = f_1 \quad \begin{matrix} V_2 = 3.3 \\ V_1 = 5 \end{matrix}$$


$$\frac{P_2}{P_1} = 1 \cdot \left(\frac{3.3}{5} \right)^2 = 0.44$$

$$\frac{P_2}{P_1} = \frac{1}{50} \left(\frac{V}{V} \right)^2 = 2\%$$

Exercise 5: What are the active-state current and the RC time constant for a wired-or interrupt-request line using a 10kΩ resistor pulling up a circuit with 50 pF capacitance to 3.3 V?

$$I = \frac{V}{R} = \frac{3.3}{10\text{ k}} = 0.33\text{ mA}$$

$$\begin{aligned} \tau = RC &= 10\text{ k} \cdot 50\text{ pF} \\ &= 10 \times 10^3 \cdot 50 \times 10^{-12} \\ &= 500 \times 10^{-9}\text{ s} = 0.5\text{ }\mu\text{s} \end{aligned}$$

 

Exercise 6: How many square mm of PCB area does each package require? Which packages have their pins accessible when the packages is placed on the PCB?

$$22^2 = 484 \text{ mm}^2$$

$$3.5^2 = 12.25 \text{ mm}^2$$

TFQD has accessible pins, BGA does not