

## Analog Interfaces

**Exercise 1:** Draw a sine wave and indicate two sets of sampling points at twice the frequency of the sine wave: one that demonstrates aliasing and one that does not. Is it sufficient to sample at twice the highest frequency of the analog signal?


**Exercise 2:** What minimum sampling rate would be required to digitize a 10 kHz square wave if you wanted to include frequency components up to the 7<sup>th</sup> harmonic (at 70 kHz)?

**Exercise 3:** A signal with range of  $\pm 3$  V must be quantized so that the quantization error is less than 1 mV. What minimum number of bits of resolution is required?

**Exercise 4:** A signal-to-noise power ratio of about 48 dB is considered good enough for speech communication. Approximately how many bits per sample are required to obtain this quantization SNR?

**Exercise 5:** When quantizing a full-scale sine wave, what quantization SNR would be achieved with a resolution of 12 bits? What if the signal's voltage range was only half of the full-scale range?

**Exercise 6:**

 

Assume  $V_1$  is set to  $V_{ref}$  and all other inputs are zero (grounded). Find the Thevenin resistance (resistance to ground at  $V_{out}$  with all  $V_i$  shorted) and voltage ( $V_{out}$  with  $V_1 = V_{ref}$ ).


**Exercise 7:** You are using a PWM DAC to convert a 200 VDC supply to a 48 VDC output. The switching frequency is 25 kHz. What is the duration of each PWM pulse?

**Exercise 8:** You are designing a PWM DAC and need resolution of 1 mV with a full-scale output of 12 V. How many bits of resolution are required? The pulse frequency is 10 kHz. What is the clock frequency?



**Exercise 9:** Rank the different DACs described above in terms of sampling rate relative to clock rate and complexity relative to resolution.

**Exercise 10:**

 

Draw a diagram showing the voltage ranges, the comparator outputs and the binary output for the 4-bit flash ADC above.

**Exercise 11:** A SAR ADC using a 4-bit DAC with a full-scale range of 0 to 7.5 V digitizes a 5.25 V signal. What voltages will the DAC output?

**Exercise 12:** What is the slope of an integrator, in V/s, when charging a 100 nF capacitor with 5 V through a 100 k $\Omega$  resistor?

**Exercise 13:** Rank the different ADCs described above in terms of sampling rate relative to clock rate and complexity relative to resolution.