

ELEX 2117 : Digital Techniques 2  
2022 Fall Term

**MIDTERM EXAM 2**  
**15:30 – 17:20**  
**Friday, November 4, 2022**  
**SW03-1710**

This exam has five (5) questions on two (2) pages. The marks for each question are as indicated. There are a total of seventeen (17) marks. Answer all questions. Write your answers and all rough work in this paper and nowhere else. Show your work. Draw a box around your final answer. Numerical answers must include units. Books and notes are allowed. No electronic devices other than calculators are allowed. Show your work.

This exam paper is for:

**Sample Exam 1** A00123456

Each exam is equally difficult.

Answer your own exam.

Do not start until you are told to do so.

Name: \_\_\_\_\_

BCIT ID: \_\_\_\_\_

Signature: \_\_\_\_\_

## Question 1


5 marks

A sequence detector detects input sequences consisting of a 1, followed by any number of zeros (including none), followed by a 1.

There are two inputs named **reset** and **in**. There is one output named **out**. When **reset** is asserted the output is set to 0. When the desired sequence is detected, the output is set to 1. The output remains at 1 until **reset** is asserted again.

The state transition diagram and state transition table are shown at right. The state does not change for other input conditions. A second table shows the value of **out** for each state.

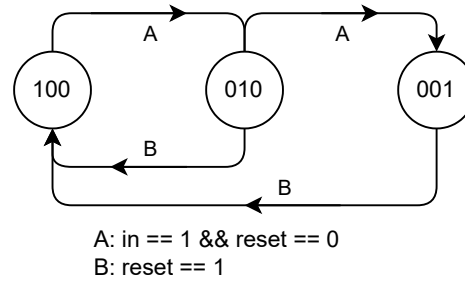Fill in the missing code in the following Verilog module so as to implement the sequence detector state machine described above.



state	reset	in	next state
X	1	X	100
100	0	1	010
010	0	1	001

state	out
100	0
010	0
001	1

```

module detector
  ( input logic reset, clk, in,
    output logic out ) ;

  logic [2:0] state ;
endmodule
  
```

## Question 2

2 marks

- Should an input named **RESET** be set high or low to cause a reset?
- Should an output named **INTERRUPT** be set high or low to cause an interrupt?

## Question 3


4 marks

The following Verilog shows the declaration of a module named **quad**. The diagram shows how two of these are connected within a module named **angles**:

```

module quad
  ( input  logic [7:0] s,
    output logic [7:0] q ) ;
  // ...
endmodule

```

 

The numbers above the lines show the signal (bus) widths. The identifiers above the boxes show the module and instance names. The identifiers below the ports show the **angles** module port names.

Write a System Verilog module named **angles** that implements the diagram above. Declare any signals required to implement the **angles** module. Do not write the **quad** module. Follow the course coding conventions

### Question 4

4 marks

Fill in the following testbench module with code that does the following:

- (a) sets the value of **n** to **0** in an **initial** block,
- (b) terminates the simulation with **\$stop()** if the value of **n** is equal to **8'd255**,
- (c) adds 1 to **n** every 5  $\mu$ s, and
- (d) uses **\$display()** to print the value of **n** every 20  $\mu$ s.

```

module midterm_tb ;


    logic [7:0] n ;
endmodule

```

### Question 5

2 marks

The following waveform shows the signals on an SPI interface. What value was transmitted from the slave to the master assuming the bits were transferred most-significant-bit first? Give your answer as a hexadecimal number. Show your work.

 

ELEX 2117 : Digital Techniques 2

2022 Fall Term

**MIDTERM EXAM 2**

**15:30 – 17:20**

**Friday, November 4, 2022**

**SW03-1710**

This exam has five (5) questions on two (2) pages. The marks for each question are as indicated. There are a total of seventeen (17) marks. Answer all questions. Write your answers and all rough work in this paper and nowhere else. Show your work. Draw a box around your final answer. Numerical answers must include units. Books and notes are allowed. No electronic devices other than calculators are allowed. Show your work.

This exam paper is for:

**Sample Exam 2** A01234567

Each exam is equally difficult.

Answer your own exam.

Do not start until you are told to do so.

Name: \_\_\_\_\_

BCIT ID: \_\_\_\_\_

Signature: \_\_\_\_\_

## Question 1


5 marks

A sequence detector detects input sequences consisting of a 1, followed by any number of zeros (including none), followed by a 1.

There are two inputs named **reset** and **in**. There is one output named **out**. When **reset** is asserted the output is set to 0. When the desired sequence is detected, the output is set to 1. The output remains at 1 until **reset** is asserted again.

The state transition diagram and state transition table are shown at right. The state does not change for other input conditions. A second table shows the value of **out** for each state.

 Fill in the missing code in the following Verilog module so as to implement the sequence detector state machine described above.



state	reset	in	next state
X	1	X	100
100	0	1	010
010	0	1	001

state	out
100	0
010	0
001	1

```
module detector
  ( input logic reset, clk, in,
    output logic out ) ;

  logic [2:0] state ;
endmodule
```

## Question 2

2 marks

- Should an input named **RESET** be set high or low to cause a reset?
- Should an output named **INTERRUPT** be set high or low to cause an interrupt?

## Question 3


4 marks

The following Verilog shows the declaration of a module named **quad**. The diagram shows how two of these are connected within a module named **angles**:

```

module quad
  ( input  logic [7:0] s,
    output logic [7:0] q ) ;
  // ...
endmodule

```

 

The numbers above the lines show the signal (bus) widths. The identifiers above the boxes show the module and instance names. The identifiers below the ports show the **angles** module port names.

Write a System Verilog module named **angles** that implements the diagram above. Declare any signals required to implement the **angles** module. Do not write the **quad** module. Follow the course coding conventions

### Question 4

4 marks

Fill in the following testbench module with code that does the following:

- (a) sets the value of **n** to **0** in an **initial** block,
- (b) terminates the simulation with **\$stop()** if the value of **n** is equal to **8'd255**,
- (c) adds 1 to **n** every 5  $\mu$ s, and
- (d) uses **\$display()** to print the value of **n** every 20  $\mu$ s.

```

module midterm_tb ;

    logic [7:0] n ;
endmodule

```

### Question 5

2 marks

The following waveform shows the signals on an SPI interface. What value was transmitted from the master to the slave assuming the bits were transferred most-significant-bit first? Give you answer as a hexadecimal number. Show your work.

