
 


## Applications of State Machines

 **Exercise 1:** The example above is an N-bit shift register that shifts the bits right. Draw a block diagram and write the Verilog for a 6-bit shift register that shifts left.




### Exercise 2:



Fill in the diagram above for a 4-bit ( $N = 4$ ) right-shift shift register. Assume the initial value is zero. Which bit is the oldest (first) value in the D waveform? Which bit of the shift register holds the oldest value?


oldest value in waveform is leftmost one.  
 oldest bit in shift register is rightmost one.

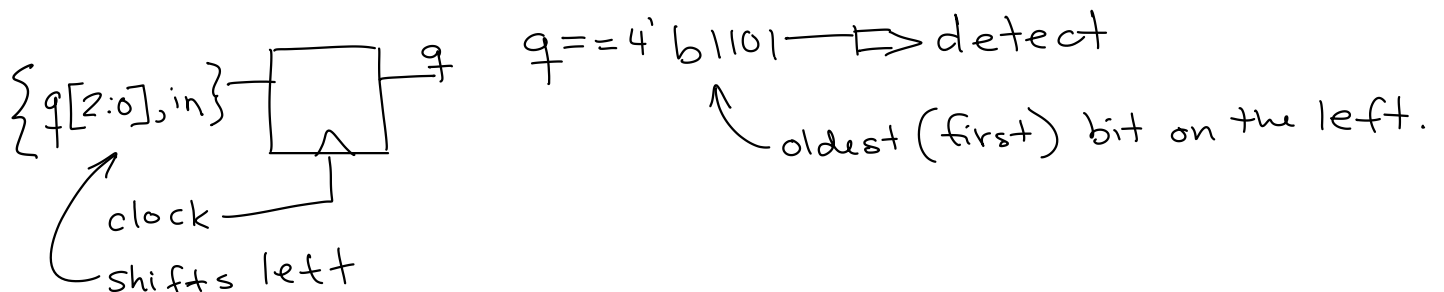**Exercise 3:** Draw a block diagram and write the Verilog for a circuit that sets an output named **detect** high when the sequence of values 1, 1, 0, 1 has appeared on an input named **in** on successive rising edges of the clock.



 **Exercise 4:** For which states would a **fell** output be asserted? A **rose** output? Draw the schematic and write the Verilog for this state machine. Assume an input **in** and a 2-bit register **bits** that holds the two most recent input values.


fell asserted when shift register is 2'b10  
 rose when 2'b01



always\_ff @(posedge clock)  
 bits <= {bits[0], in};

assign rose = bits == 2'b01;  
 assign fell = bits == 2'b10;

 **Exercise 5:** Can you design an edge detector that uses only one bit?  
 Is this a Mealy or a Moore state machine?



always\_ff @(posedge clock)

q <= in;

assign {fell, rose} = {~in & q, in & ~q};

this is a Mealy S.M. → the output is a function of the state (q) and the input (in).

**Exercise 6:** Write the state transition table for this state machine.

state	result	next state
xx	1	00
11	0	00
n	0	n+1


**Exercise 7:** Write `always_ff` statements that implement these state machines.

e.g.  $N = 20001$

`logic [15:0] count;`

count	in == out	next count
x	1	$N - 1$
0	x	$N - 1$
n	0	$n - 1$
 
`always_ff @(posedge clock)`  
`count <= in == out ? 16'd20_000 :`  
`!count ? 16'd20_000 :`  
`count - 1;`



`always_ff @(posedge clock)`  
`out <= count != 0 ? out : in;`

**Exercise 8:** How could you modify the code so that `digits` is only updated when an `enable` input is asserted?

`always_ff @(posedge clock)`  
`digits <= enable ? {digits[1:3], digit} :`  
`digits;`

**Exercise 9:** How many states can this state machine have?

$$4 \text{ digits} \times 4 \text{ bits} = 16.$$

**Exercise 10:** Draw the state transition diagram for this simpler implementation. How many states are there? Write the Verilog using a 3-bit count state variable.

