

## More Verilog

This lecture describes the relationship between numbers, logic levels and truth values. It also describes Verilog modules and parameters.

After this lecture you should be able to: convert between high/low logic levels and true/false truth values for active-high and active-low interfaces, declare modules with parameters and ports, and instantiate modules using positional, named and wildcard parameters and signals.

### Numbers, Truth Values and Logic Levels

Numbers are used for counting, logic levels are voltages, and truth values can be true or false. These are different, but related.

0 and 1 almost always mean false and true respectively. But there are two common conventions for logic levels and truth values. Active-high signals are true when they are high and active-low signals are true when they are low.

Active-low signals can be denoted by:

- a bar over the signal name ( $\overline{\text{reset}}$ )
- an asterisk after the signal name (**RESET\***)
- a suffix of N (or n) after the signal name (**reset\_n**)

Verilog uses the usual meaning of 0 and 1 as truth values in expressions. But for inputs and outputs it always uses **0** and **1** for low and high respectively. Thus the truth value of **0** or **1** in Verilog depends on the context – when used for I/O a **0** could mean either true or false.

The following table summarizes the correspondence between active-high and active-low signals, truth values, logic levels and the values used in Verilog:

signal name	logic level	truth value	Verilog expression	Verilog I/O
$\overline{s}$	L	T	1	0
$\overline{s}$	H	F	0	1
s	L	F	0	0
s	H	T	1	1

**Exercise 1:** Is a signal named  $\overline{\text{overload}}$  active-high or active-low? Is there an overload if this signal is high? What if the signal was named **overload**?

**Exercise 2:** Come up with active-high and an active-low names for a signal that is at 3 V when a door is open and 0 V when the door is closed.

In addition to the two ways to represent truth values with voltages (active-high and active-low) there are also two ways to represent binary digits (“bits”) with voltages. A high voltage may represent either a 0 or a 1. Signals where a 1 is represented by a low voltage typically, but not always, use active-low notation.


**Exercise 3:** If  $\overline{D}$  is a word and  $\overline{D[0]}$  is low, is the word an even or odd number?

### Modules

Simple things are easier to design and test than complex ones. Thus it’s good practice to divide designs into smaller parts<sup>1</sup>. These can often be re-used.

Many designs incorporate complex parts designed by others (e.g. processors, memories and interfaces), called design IP (“Intellectual Property”).

 In Verilog each part is a **module**. Modules describe logic that can be “instantiated” (duplicated and inserted into) another module:



<sup>1</sup>How small? A good rule of thumb is to make sure each part can be described on a single page.

 


Figure 1: Shift Register Synthesis

The module's interfaces are defined by a header describing ports and parameters. Ports are **in**, **out** or **inout** (bidirectional) signals while parameters are values that can customize each instance of a module. The module's body contains additional signal declarations and parallel (concurrently executing) statements between **module** and **endmodule**. These define the structure or behaviour of the module.

Here's an example of a module named **bits** that defines an **nb**-bit register:

```

module bits
  #(parameter nb=1)
  (
    input  logic [nb-1:0] d,
    output logic [nb-1:0] q,
    input  logic clock
  ) ;

  always_ff @(posedge clock) q <= d ;
endmodule

```

The parameter **nb** has a default value of **1** which is used if a value is not specified when this module is instantiated. There are two input ports (named **d** and **clock**) and one output port (named **q**).

A module instantiation starts with the name of the module followed by parameter values (if any), an instance name (to identify individual instances of the same module), and a description of how to connect signals in the instantiating module to the ports in the instantiated module. For example:


```
bits #(4) b0 (a,b,c) ;
```

Would instantiate a **bits** module with one parameter of value 4, an instance name **b0** and connect the signals **a**, **b** and **c** in the instantiating module to the corresponding ports in an instance of the **bits** module (**d**, **q** and **clock** respectively).

**Exercise 4:** Draw a diagram for this instantiation of the **bits** module. Label the module, instance, signal and port names as in the

diagram above.

 An 8-bit, 3-stage shift register could be built using three **bits** modules:



```

module sr3bytes
  (
    input  logic [7:0] newest,
    output logic [7:0] oldest,
    input  logic clock
  ) ;

  localparam nbits = 8 ;

  logic [nbits-1:0] a, b ;

  // matching by order
  bits #(nbits) b0 (newest,a,clock);

  // matching by name (order does not matter)
  bits #(.nb(nbites)) b1 (.q(b),.clock,.d(a));

  // wildcards for names that match
  bits #(.nb(nbites)) b2 (.d(b),.q(oldest),.*);
endmodule

```

**Exercise 5:** Identify the module instantiation statements in the code above. For each one, what is the instantiated module's name? The instance name?

When one module is instantiated in another, a signal can be connected to module port by:

- port order (**signal**),
- port name and explicit signal name (**.port(signal)**),
- port name only – connecting to the matching signal name (**.port**),

- a wildcard that matches all remaining matching port and signal names (. \*).

The signal name can be an expressions (e.g. `word[15:8]`) instead of a signal. Matching of values to parameters can be done by order (`value`) or explicitly, `.parameter(value)`.

The synthesis result, shown above, is as expected.