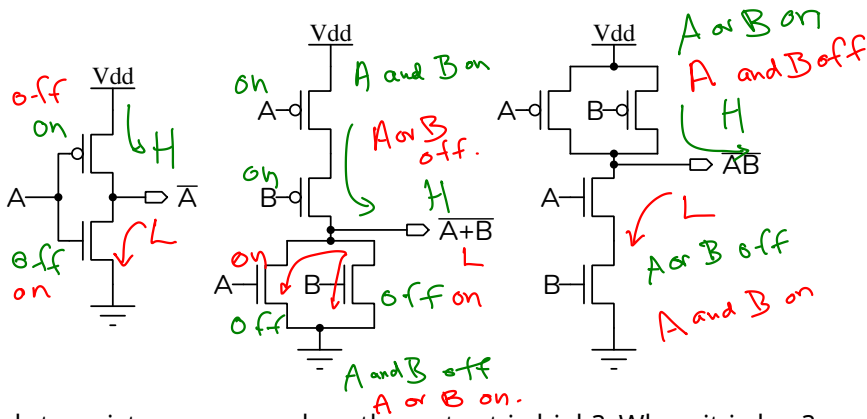



Implementation of Digital Logic Circuits

Exercise 1:



Which transistors are on when the output is high? When it is low?
In which direction does the output current flow in each case?


Exercise 2:

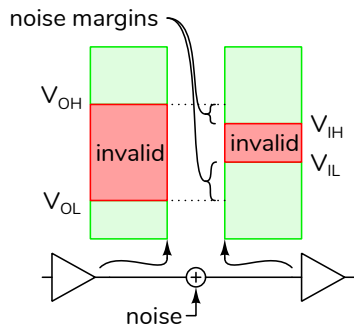

Which of these specifications does the manufacturer guarantee? → all of these specifications are guaranteed.
Which are requirements?

in a particular circuit input levels will be requirements.

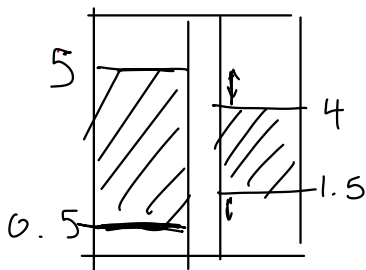Exercise 3: A logic family has $V_{OH}(\min) = 5\text{ V}$, $V_{OL}(\max) = 0.5\text{ V}$, $V_{IH}(\min) = 4\text{ V}$ and $V_{IL}(\max) = 1.5\text{ V}$. What are the noise margins?



$$\text{high noise margin} = 5 - 4 = 1\text{ V}$$



$$\text{low noisemargin} = 1.5 - 0.5 = 1\text{ V}$$

Exercise 4: All else being equal, by how much would we expect to decrease power consumption when reducing logic levels from 5 V to 3.3 V? What would be the effect on power consumption in reducing the clock frequency from 50 MHz to 1 MHz?

$$\frac{P_2}{P_1} = \frac{f_2}{f_1} \left(\frac{V_2}{V_1} \right)^2 = \left(\frac{3.3}{5} \right)^2 = 0.43$$

$$\frac{P_2}{P_1} = \frac{f_2}{f_1} = \frac{1}{50} = 2\%$$

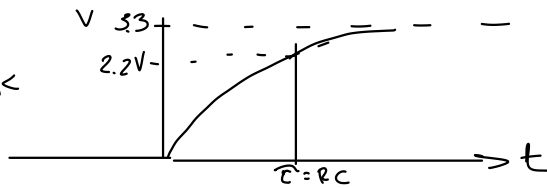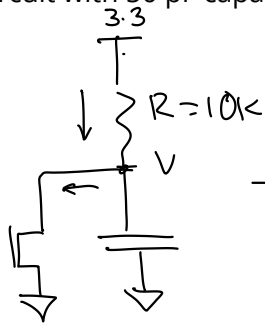Exercise 5: What are the active-state current and the RC time constant for a wired-or-interrupt-request line using a 10kΩ resistor pulling up a circuit with 50 pF capacitance to 3.3 V?




$$i = \frac{V}{R} = \frac{3.3}{10k} = 0.33 \text{ mA } (330 \mu\text{A})$$

AA
1000
3000mAh
1000mAh.

$$\tau = RC = 10 \times 10^3 \times 50 \times 10^{-12} = 500 \times 10^{-9} = 0.5 \mu\text{s}.$$

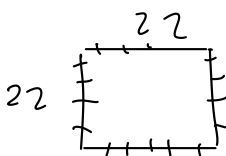Exercise 6: How many square mm of PCB area does each package require? Which packages have their pins accessible when the package is placed on the PCB?




$$22^2 \text{ mm}^2$$

$$484 \text{ mm}^2$$



$$3.5^2 \text{ mm}^2$$

$$12.25 \text{ mm}^2$$

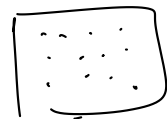

↑
TQFP - pins accessible

↑
BGA - balls not accessible