

ELEX 2117 : Digital Techniques 2  
2023 Fall Term

**MIDTERM EXAM 1**

**15:30**

**Friday, October 6, 2023**

**SW03-1750**

This exam has four (4) questions on two (2) pages. The marks for each question are as indicated. There are a total of seventeen (17) marks. Answer all questions. Write your answers and all rough work in this paper and nowhere else. Show your work. Underline or draw a box around your final answer. Numerical answers must include units. Books and notes are allowed. No electronic devices other than calculators are allowed. **Show your work.**

This exam paper is for:

**Sample Exam 1** A00123456

Each exam is equally difficult.

Answer your own exam.

Do not start until you are told to do so.

Name: \_\_\_\_\_

BCIT ID: \_\_\_\_\_

Signature: \_\_\_\_\_

### Question 1

5 marks

Fill the table below with the value of each expression as a Verilog numeric literal including the correct width and the correct value in hexadecimal base. Assume the following declarations:

```
logic [7:0] x ;
```

```
logic [3:0] y ;
```


and that **x** has the value **8'hb3** and that **y** has the value **4'b0110**. The first row has been filled in as an example.

expression	value
<code>x[3:0]</code>	<code>4'h3</code>
<code>!x[4]   x[3]</code>	
<code>{ ~y, x[7:4] }</code>	
<code>x &lt;&lt; y[3:2]</code>	
<code>x[7] ? 3'b1 : 4'd2</code>	
<code>x + 1</code>	
 
### Question 2

4 marks

Write a System Verilog module named **pwm** with three inputs (**clock**, **enable**, and **w**) and one output (**out**) that implements the schematic below. Follow the course coding conventions.



### Question 3

4 marks


A state machine has **reset** and **clock** inputs, and a **pulse** output. Whenever **reset** is asserted, the output is set to **0**. When **reset** is de-asserted, **pulse** is set to **1** for three clock cycles and then it is set to **0** and it stays at **0** until **reset** is asserted again. Write the next-state truth table and the output truth table for this state machine. Use a binary state encoding.

## Question 4

4 marks

Write a System Verilog module named **esc** that implements the state machine described by the following state transition diagram. The module has four one-bit inputs: **clear**, **even**, **odd**, and **clock** (a clock). It has a one-bit output named **done**. You may use any name(s) for signal(s) internal to the module.

Follow the course coding conventions.

 

ELEX 2117 : Digital Techniques 2  
2023 Fall Term

**MIDTERM EXAM 1**

**15:30**

**Friday, October 6, 2023**

**SW03-1750**

This exam has four (4) questions on two (2) pages. The marks for each question are as indicated. There are a total of seventeen (17) marks. Answer all questions. Write your answers and all rough work in this paper and nowhere else. Show your work. Underline or draw a box around your final answer. Numerical answers must include units. Books and notes are allowed. No electronic devices other than calculators are allowed. **Show your work.**

This exam paper is for:

**Sample Exam 2** A01234567

Each exam is equally difficult.

Answer your own exam.

Do not start until you are told to do so.

Name: \_\_\_\_\_

BCIT ID: \_\_\_\_\_

Signature: \_\_\_\_\_

### Question 1

5 marks

Fill the table below with the value of each expression as a Verilog numeric literal including the correct width and the correct value in hexadecimal base. Assume the following declarations:

```
logic [7:0] x ;
```

```
logic [3:0] y ;
```


and that  $x$  has the value  $8'h3b$  and that  $y$  has the value  $4'b0110$ . The first row has been filled in as an example.

expression	value
$x[3:0]$	$4'hb$
$!x[4]   x[3]$	
$\{ \sim y, x[7:4] \}$	
$x \ll y[3:2]$	
$x[7] ? 3'b1 : 4'd2$	
$x + 1$	
 
### Question 2

4 marks

Write a System Verilog module named `pwm` with three inputs (`clock`, `enable`, and `w`) and one output (`out`) that implements the schematic below. Follow the course coding conventions.



### Question 3

4 marks

A state machine has `reset` and `clock` inputs, and a `pulse` output. Whenever `reset` is asserted, the output is set to `0`. When `reset` is de-asserted, `pulse` is set to `1` for three clock cycles and then it is set to `0` and it stays at `0` until `reset` is asserted again. Write the next-state truth table and the output truth table for this state machine. Use a one-hot state encoding.

## Question 4

4 marks

Write a System Verilog module named **esc** that implements the state machine described by the following state transition diagram. The module has four one-bit inputs: **clear**, **even**, **odd**, and **clock** (a clock). It has a one-bit output named **done**. You may use any name(s) for signal(s) internal to the module.

Follow the course coding conventions.

