

HDL Idioms

Exercise 1: Using the schematic symbols shown below, convert each of the following System Verilog expressions into a schematic.

Exercise 2: Using the schematic symbols shown above, convert each of the following System Verilog expressions into a schematic.

Exercise 3: Write System Verilog that would generate each of the following schematics. Include any required signal declarations (using **logic**).