
 


Examples of State Machines


Exercise 1: The example above is an N-bit shift register that shifts the bits right. Draw a block diagram and write the Verilog for a 6-bit shift register that shifts left.

 

Exercise 2:




1 bit
Q [3:0]
D [3:0]

 

Fill in the diagram above for a 4-bit ($N = 4$) right-shift shift register. Assume the initial value is zero. Which bit is the oldest (first) value in the waveform? Which bit of the shift register holds the oldest value?

 Exercise 3: Draw a block diagram and write the Verilog for a circuit that sets an output named **detect** high when the sequence of values 1, 1, 0, 1 has appeared on an input named **in** on successive rising edges of the clock.



```
module ex100 (input logic in, clk,
               output logic detect);
```

```
logic [3:0] q;
always_ff @ (posedge clk)
  q <- {in, q[3:1]};
```

```
assign detect = q == 4'b1011;
```

end module

Exercise 4: How could you modify the code so that **digits** is only updated when an **enable** input is asserted?

```
always_ff @(posedge clk) digits
  <= { digits[1:3], digit } ;
```

```
<= enable ? { digits[1:3], digit } : digits ;
```


Exercise 5: How many states can this state machine have?

4	4	4	4
---	---	---	---

$$\uparrow \\ 10 \times 10 \times 10 \times 10 = 10^4$$

$$\text{or } 16 \times 16 \times 16 \times 16 = \\ 2^4 \times 2^4 \times 2^4 \times 2^4 = 2^{16}$$

 Exercise 6: Draw the state transition diagram for this simpler implementation. How many states are there? Write the Verilog using a 3-bit **count** state variable.




c: enable == 1
d: digit

assume the combination is
8936

Exercise 7: For which states would a **fell** output be asserted? A **rose** output? Draw the schematic and write the Verilog for this state machine. Assume an input **in** and a 2-bit register **bits** that holds the two most recent input values.

fell would be asserted in state 10.
rose would be asserted in state 01.

 Exercise 8: Can you design an edge detector that uses only one bit?
Is this a Mealy or a Moore state machine?




QSS'Y rose = !Q & in; ← Mealy (output is function of input)

Exercise 9: Write `always_ff` statements that implement these state machines.

```

logic [15:0] count;
always-ff @ (posedge clock)
count <= in == out ? 49-999 :
!count ? 49-999 :
in != out ? count - 1'b1 : count;
out <= count != 0 ? out : in;
    
```

count	in == out	next count
x	1	N - 1
0	x	N - 1
n	0	n - 1

 

Exercise 10: Write the state transition table for this state machine.

state	inputs	next State
-	-	-

state	reset	count == 0	next state
X	1	X	00 E
00	0	1	01 A
01	0	1	10 B
10	0	1	11 C
11		1	00 D

