 



## Implementation of Digital Logic Circuits

### Exercise 1:



In which direction does the output current flow when the output is high? When it is low? Which transistors in the NAND circuit are on (conducting) in each case?

**Exercise 2:**

 

Which of these specifications does the manufacturer guarantee?  
Which are requirements?

**Exercise 3:** A logic family has  $V_{OH}(\min) = 5\text{ V}$ ,  $V_{OL}(\max) = 0.5\text{ V}$ ,  $V_{IH}(\min) = 4\text{ V}$  and  $V_{IL}(\max) = 1.5\text{ V}$ . What are the noise margins?

**Exercise 4:** All else being equal, by how much would we expect to decrease power consumption when reducing logic levels from 5 V to 3.3 V? What would be the effect on power consumption in reducing the clock frequency from 50 MHz to 1 MHz?

**Exercise 5:** The energy stored in a battery (its “capacity”) is measured in Amp-hours. If a circuit draws 100 mA for 100  $\mu$ s per second and draws 100  $\mu$ A the rest of the time, how long will a 1000 mAh battery last?

**Exercise 6:** What are the active-state current and the RC time constant for a wired-or interrupt-request line using a  $10\text{k}\Omega$  resistor pulling up a circuit with  $50\text{ pF}$  capacitance to  $3.3\text{ V}$ ?

**Exercise 7:** How many square mm of PCB area does each package require? Which packages have their pins accessible when the package is placed on the PCB?