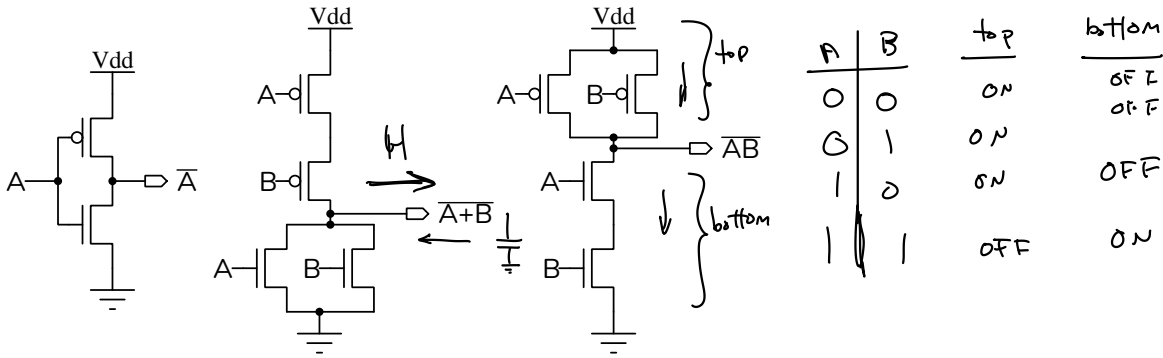



# Implementation of Digital Logic Circuits

## Exercise 1:





In which direction does the output current flow when the output is high? When it is low? Which transistors in the NAND circuit are on (conducting) in each case?

## Exercise 2:

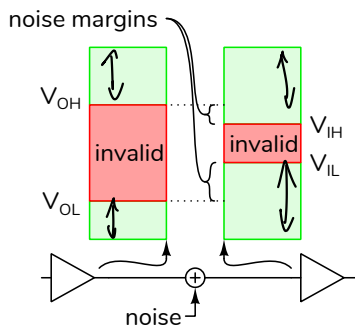

Which of these specifications does the manufacturer guarantee? all  
 Which are requirements? none

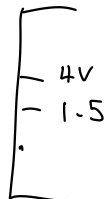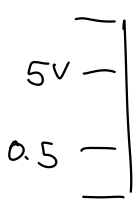**Exercise 3:** A logic family has  $V_{OH}(\min) = 5\text{ V}$ ,  $V_{OL}(\max) = 0.5\text{ V}$ ,  $V_{IH}(\min) = 4\text{ V}$  and  $V_{IL}(\max) = 1.5\text{ V}$ . What are the noise margins?



$$\text{noise margin (high)} = 5 - 4 = 1$$

$$\text{noise margin (low)} = 1.5 - 0.5 = 1$$

**Exercise 4:** All else being equal, by how much would we expect to decrease power consumption when reducing logic levels from 5 V to 3.3 V? What would be the effect on power consumption in reducing the clock frequency from 50 MHz to 1 MHz?

$$\frac{P_2}{P_1} = \frac{f_2}{f_1} \left( \frac{V_2}{V_1} \right)^2 \quad \begin{array}{l} f_2 = f_1 \\ V_2 = 3.3 \\ V_1 = 5 \end{array}$$

$$\frac{P_2}{P_1} = \left( \frac{3.3}{5} \right)^2 = 0.44 \quad P_2 = 0.44 P_1$$

power reduced by 56%


$$\frac{P_2}{P_1} = \frac{f_2}{f_1} \left( \frac{V_2}{V_1} \right)^2 \quad \begin{array}{l} V_2 = V_1 \\ f_2 = 1 \\ f_1 = 50 \end{array}$$

$$P_2 = P_1 \left( \frac{1}{50} \right) = 0.02 P_1$$

new power is 2% of original

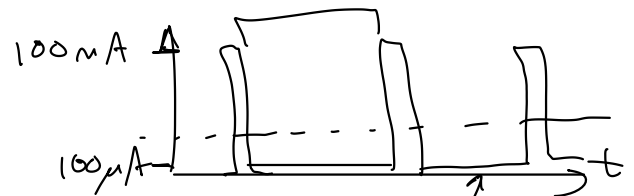**Exercise 5:** The energy stored in a battery (its "capacity") is measured in Amp-hours. If a circuit draws 100 mA for 100 μs per second and draws 100 μA the rest of the time, how long will a 1000 mAh battery last?


$$\text{capacity} = \frac{I}{\text{mA/A}} \cdot T \quad \begin{array}{l} \text{s/hour} \end{array}$$



$$\begin{aligned} \overline{I}_{\text{average}} &= \frac{100 \mu\text{s} \cdot 100 \text{ mA} + (1 - 100 \times 10^{-6}) \times 100 \times 10^{-6}}{1 \text{ s}} \text{ A} \\ &= \frac{10^{-5} + 10^{-4} - 10^{-10}}{1} \approx 1.1 \times 10^{-4} \text{ A} \end{aligned}$$

$$T = \frac{\text{capacity}}{I} = \frac{1000 \times 10^{-3} \text{ A}\cdot\text{h}}{1.1 \times 10^{-4} \text{ A}} \approx 900 \text{ hours}$$

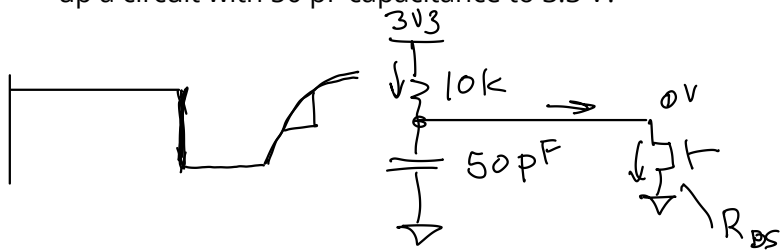**Exercise 6:** What are the active-state current and the RC time constant for a wired-or interrupt-request line using a  $10\text{k}\Omega$  resistor pulling up a circuit with  $50\text{ pF}$  capacitance to  $3.3\text{ V}$ ?



$$I = \frac{V}{R} = \frac{3.3}{10\text{k}} = 0.33\text{ mA}$$

$$P = \frac{V^2}{R} = \frac{(3.3)^2}{10\text{k}} = 1\text{ mW}$$

$$RC = 10 \times 10^3 \times 50 \times 10^{-12}$$

$$= 500 \times 10^{-9} = 0.5\text{ }\mu\text{s}$$

**Exercise 7:** How many square mm of PCB area does each package require? Which packages have their pins accessible when the package is placed on the PCB?

$$22 \times 22\text{ mm} = 484\text{ mm}^2$$

$$3.5 \times 3.5\text{ mm} = \sim 12\text{ mm}^2$$

DIP & TQFP = accessible pins.