

## State Machines

(see section 7-14 in text for related material)

**Exercise 1:** Why do I need to know this?

for Lab 5 & Lab Exam #1

**Exercise 2:** In theory, what is a SM? What isn't a SM?

- anything with memory is a SM (in theory)  
- if no memory (FF, registers) then it's not a SM.

**Exercise 3:** How large a SM is it practical to design? (how many states)

$\approx 1$  page  
 $< 20?$  states } if larger, then decompose to smaller SMs.

**Exercise 4:** What are some things we could design as SMs?

- elevator
- traffic light
- alarms

**Exercise 5:** What are some things we would not design as a SM?

Why?

counter - too many states  
CPU - too complicated.  
(but parts of the CPU would be)

**Exercise 6:** What defines the state of a SM?


the contents of registers / FFs.

**Exercise 7:** How can we describe the operation of a SM?

E = enable?


R = reset?

① as a state transition diagram

 

② as a table

state	input	state'
	E R	
00	1 X	10
10	0 1	00
	1 0	11
11	X 1	00

 

③ as a circuit

**Exercise 8:** Can a design have multiple state machines?

Yes, very common.

**Exercise 9:** How can one SM control another?

through their states or their state transitions (events).

**Exercise 10:** What are the steps in designing a SM?

**Exercise 11:** Show me some examples!

} see lecture 6.