

Solutions to Quiz 2 (second version)


This exam is for the student whose...

surname begins with	BCIT ID ends with

Question	1	2			Total
Mark					
Out of	9	9			18

Question 1: VHDL to Schematic

Using the following schematic symbols:

 


and these declarations:

```


type byte_array is array (natural range <>) of
  std_logic_vector(7 downto 0) ;
signal a, b, c, d, w, clk : std_logic ;
signal x, y, z, y_next, n : unsigned (7 downto 0) ;
signal r, s : unsigned (31 downto 0) ;
signal m : byte_array (0 to 3) ;
signal p : unsigned(1 downto 0) ;
  
```

convert each of the following VHDL expressions into a schematic:


(a) `a <= b or (not d) ;`

 

 
(b) `y <= x when not (a or b) else x"12" ;`



(c) `y <= x when rising_edge(clk) ;`

 


(d) `y_next <= y+1 when a = '1' or w = '0' else y-1 when b = '1' else y ;`
`y <= y_next when rising_edge(clk) ;`

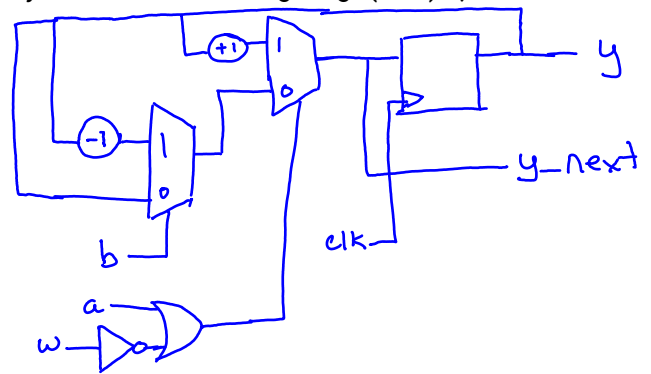

 
Question 2: Schematic to VHDL

Assuming the above signal declarations and schematic symbols, write concurrent VHDL statements that would result in the following schematics:




(a)

```
w <= not ( a and b );
```

 

(b)

```
y <= x when b = '1' else x"20" ;
```

 


(c)

```
y_next <= y + x ;
y <= y_next when rising_edge(w) ;
```


OR

```
y <= y+x when rising_edge(w) ;
```

 

(d)
 
```
y <= y_next when rising_edge(clk) ;
```



(e)

```
y_next <= y when w else
y+1 when d else
y-1 ;
```