

## Timers and Frequency Dividers

### Introduction

Timer circuits measure time by counting clock cycles. Clock dividers, also called frequency dividers, are timer circuits that generate periodic outputs.

In this lab you will use a frequency divider to generate tones by periodically switching the current flowing through a speaker.

The frequency divider's counter counts down from  $N - 1$  to 0. When the counter reaches zero the output is toggled (changes values). The clock period and  $N$  determine the speaker waveform period.

In this lab you will use a 50 MHz clock on the CPLD board. The period of this clock is  $1/50 \times 10^6 = 20$  ns. The period of the speaker waveform is thus  $2N \times 20$  ns.

### Components

You will need:

- a solderless breadboard
- your EPM240T100C5 CPLD board, Byte Blaster JTAG interface and coaxial power connector,
- a 200  $\Omega$  resistor
- two SPST N.O. pushbutton switches (two SPDT switches will also work)
- a speaker
- two cables with alligator clips from your ELEX 1117 parts kit

### Specifications


Pushing one or both buttons should result in a tone. The required tone frequencies are determined by your BCIT ID:

right button	$500 + 100d_0$
left button	$500 + 100d_1$
both buttons	$500 + 100d_2$


where  $d_n$  is the  $n$ 'th digit of your BCIT ID ( $n=7$  to 0 from left to right). For example, if your BCIT ID was A01234567 the frequencies would be 1200, 1100 and 1000 Hz for the right, left and both buttons respectively.
 
### CPLD I/O

The following diagram shows the connections to the CPLD:



 Wire two pushbutton switches and a current-limiting resistor on the breadboard and connect a CPLD I/O pin and the resistor to the speaker with alligator clip cables:



The pin assignments are similar to the previous lab. The n.o. switch inputs are configured with pull-ups and the switch inputs are active-low.

The current-limiting resistor avoids exceeding the maximum current rating of the MAX II CPLD outputs (25 mA)<sup>1</sup>

## Sample Design

If no button is being pushed the counter is set to 1. Otherwise if the counter is non-zero, the counter is decremented, otherwise it's loaded with a value equal to the appropriate number of clock cycles for a half period.

The **speaker** output is toggled (changed to the opposite value) when the count is **zero**. This results in a speaker waveform that is square wave with the required period.

## Procedure

Draw a block diagram that implements the circuit described above.

Create a project, compile it, and configure your CPLD. Assign pin 12 to the 50 MHz oscillator input (**clk50** above).

If you use the same switch pins as in the previous lab and Pin 77 for the speaker output, you should end up with the following assignments:

To	Assignment Name	Value
clk50	Location	PIN_12
x[1]	Location	PIN_99
x[0]	Location	PIN_97
x[0]	Weak Pull-Up Resistor	On
x[1]	Weak Pull-Up Resistor	On
out speaker	Location	PIN_77

It's a good idea to assign unused pins as inputs. Under **Assignments > Device... > Device and Pin Options... > Unused Pins** select "As input tri-stated with weak pull-up".

You can download the **lab3.sdc** file from the course website and add it to your project (**Project > Add/Remove Files in Project... > ...**) to allow the timing analysis to run without warnings.


Test your design.

<sup>1</sup>See page 5-1 of the MAX II datasheet available on the course web site.


## Submission

To get credit for completing this lab, submit the following to the Assignment folder for Lab 3 on the course website:

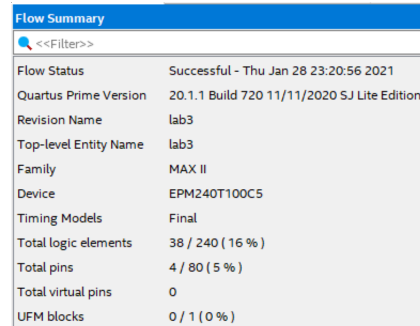1. A PDF document containing:
  - (a) A block diagram of your design.
  - (b) A listing of your Verilog code.
  - (c) A screen capture of your compilation report (**Window > Compilation Report**) similar to this:



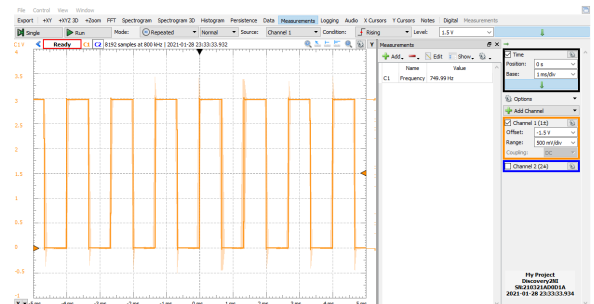- (d) The schematic created by **Tools > Netlist Viewers > RTL Viewer** and then **File > Export...**. The schematic might look like Figure 1.
- (e) A screen capture of the 'scope measurement of the **speaker** waveform when both buttons are pushed, including a frequency measurement. This might look like:



2. A short video, including audio, of the tones generated when each combination of pushbuttons is pushed. An example is on the course web site.

 


Figure 1: Example RTL Schematic for Lab 3.