

Modulo- n Counters

Introduction


Counters whose values “wrap around” back to zero when they reach the value n are called modulo- n counters.

The most common example is a modulo-10 counter that counts from 0 up to 9 and then “wraps around” back to 0. We can build a multi-digit binary-coded decimal (BCD) counter using one modulo-10 counter for each digit.

In this lab you will design a single-digit modulo- n up/down counter and instantiate four instances of your module to create a four-digit up/down counter whose digits will display on the multiplexed LED display used in the previous lab. The value of n will depend on your student ID.

Modulo Counter Specifications

 Your counter must have single-bit **clock**, **up** and **down** inputs, a 4-bit **count** output and two one-bit outputs, **carry** and **borrow**:



The counter is synchronous. This means **count** changes on the rising edge of the clock. It is:


- unchanged if neither **up** nor **down** are asserted.
- incremented if only **up** is asserted
- decremented if only **down** is asserted.
- set to zero if both **up** and **down** are asserted

If **count** is incremented when its value is $n-1$ it becomes 0. If **count** is decremented when its value is 0 it becomes $n-1$.

up and **down** are combinational logic outputs that are asserted as shown below:

count	up	down	carry	borrow
$n-1$	1	0	1	0
0	0	1	0	1
X	1	1	1	1
<i>others</i>			0	0

 The **carry** and **borrow** outputs allow modulo counters to be combined into a multi-digit counter by connecting the **carry** and **borrow** outputs of one digit to the **up** and **down** inputs of the next-most-significant digit:



Note that **up** and **down** are not clocks and **count** does not necessarily change in each clock cycle.

The modulo value, n , depends on the last digit of your student ID as shown in the table below. For example, if your ID were A00123456 you would design a modulo-7 counter.

last digit of ID	n
0, 1, 2	5
3, 4, 5	6
6, 7	7
8, 9	9

Components

You will use the same four-digit 7-segment LED display, 200 Ω current-limiting resistors and pushbutton switches as in previous labs.

Procedure

Design a modulo- n counter that meets the specifications above.

Download the **lab5.qar** project archive file from the course web site. This project archive includes a complete project except for the Verilog code in the file **modncount.sv**.

Open the archive file with Quartus and restore it to a convenient folder. Add your modulo- n counter code to `modncount.sv`. Do not rename the signals in the `modncount` module declaration. Change the pin assignments, if necessary, to match your circuit layout. Compile your design, program the CPLD and test it.

The project contains an `.sdc` file that defines the clock frequency (50 MHz) and the I/O signals as asynchronous. This allows Quartus to verify that your design operates at a 50 MHz clock frequency.

The project also includes a `.srf` file to suppress spurious error messages. These files should allow your project to compile without warnings:


● 293000 Quartus Prime Full Compilation was successful. 0 errors, 0 warnings

The archive was created using Quartus version 20.1. Opening it with Quartus II version 13.0sp1 will display errors but you can open the `.qpf` project file after restoring the archive.

The test circuit instantiates four of your modulo- n counters as shown above and displays the count on the 4-digit LED display. The `up_n` pushbutton increments the count at 1 kHz while the `down_n` button decrements it at 100 Hz. Pushing both buttons resets the counters.

CPLD I/O

 The connections to the CPLD are shown in the following diagram:



The pushbutton and LED pin assignments in the supplied project are the same as in the previous lab. The two pushbutton switch inputs have internal pull-up resistors configured. The pin assignments are shown below:

To	Assignment Name	Value
out a	Location	PIN_33
out b	Location	PIN_44
out c	Location	PIN_38
out d	Location	PIN_34
out dp	Location	PIN_36
out e	Location	PIN_30
out en[3]	Location	PIN_35
out en[2]	Location	PIN_50
out en[1]	Location	PIN_48
out en[0]	Location	PIN_42
out f	Location	PIN_52
out g	Location	PIN_40
in clock	Location	PIN_12
in up_n	Location	PIN_99
in down_n	Location	PIN_97
in up_n	Weak Pull-Up Resistor	On
in down_n	Weak Pull-Up Resistor	On

Submission

To get credit for completing this lab, submit the following to the Assignment folder for this lab on the course website:

1. A PDF document containing:
 - A block diagram of your modulo- n counter.
 - A listing of your `modncount.sv` file (but not `lab5.sv`).
 - A screen capture of your compilation report.
 - The schematic created by **Tools > Netlist Viewers > RTL Viewer**, clicking on the + button on the `modncount:m0` block to expand it, and then **File > Export...** .
Note that this is the schematic of one of your modulo- n counters, not of the complete design.
2. A video of your breadboard distinctly showing:
 - the count being reset when both buttons are pushed
 - holding down the **up** button causes the count to increase and the most-significant digit wraps around when it reaches $n-1$.
 - the count being reset again when both buttons are pushed
 - holding down the **down** button causes the count to decrease and the most-significant digit wrap around to $n-1$ when it reaches 0.