

Flip-Flops and Registers

Exercise 1: Is a signal named $\overline{\text{overload}}$ active-high or active-low? Is there an overload if this signal is high? What if the signal was named **overload**?

$\overline{\text{overload}}$: active low
H \rightarrow false : no overload. (overload is false).


overload : active high
H \rightarrow true : overload (overload is true.)

Exercise 2: Come up with an appropriate name for a signal that is at 3 V when a door is open and 0 V when the door is closed.

door_open ✓ active high 3V \rightarrow H \rightarrow open
0V \rightarrow L \rightarrow closed

$\overline{\text{door_closed}}$ active low



Exercise 3: Fill in the waveform for the Q signal in the diagram above.

 





Exercise 4: What would be another name for a 1-bit register?

FF (flip-flop).



Exercise 5: Assuming a 3-bit counter, fill in the values of D and Q in the diagram above.

  

    Exercise 6: Draw the block diagram for a counter that: (a) counts up by 3? (b) counts down by 1? (c) whose value doubles on each clock edge?




  Exercise 7: Fill in the diagram above for a 4-bit shift register. Assume the initial value of each flip-flop is zero. Which is the oldest (first) value the D waveform? Which flip-flop holds the oldest value?




oldest bit on left.

Q₃ has oldest (first) value

 

Exercise 8: Add parallel outputs to the shift register schematic. Draw a circuit whose output is high when the sequence 1, 0, 1, 1 is detected. Add the output of this circuit to the timing diagram above.

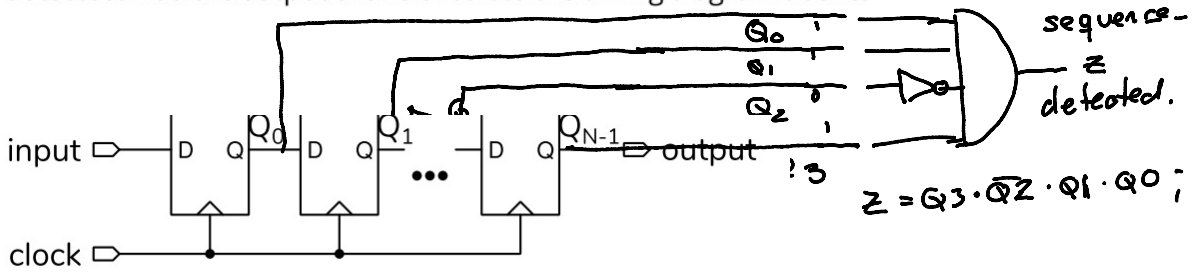

Exercise 9: What would you change to make an 8-bit register? A 4-bit counter? A 3-bit shift register? Follow the course coding conventions.


```

module test
  ( input logic [7:0] d,
    input logic clk,
    output logic [7:0] q ) ;

  always_ff @(posedge clk) q = d ;

endmodule

```

 

```

module test
  ( // input logic d,
    input logic clk,
    output logic [3:0] count ) ;


  logic [3:0] count_next ;

  assign count_next = count + 1'b1 ;

  always_ff @(posedge clk) count = count_next ;

endmodule

```

 

```

module test
  ( input logic d,
    input logic clk,
    output logic q ) ;

  logic [2:0] yeet, yeet_next ;



  assign yeet_next = { d, yeet[2:1] } ;

  always_ff @(posedge clk) yeet = yeet_next ;


  assign q = yeet[0] ;

endmodule

```

 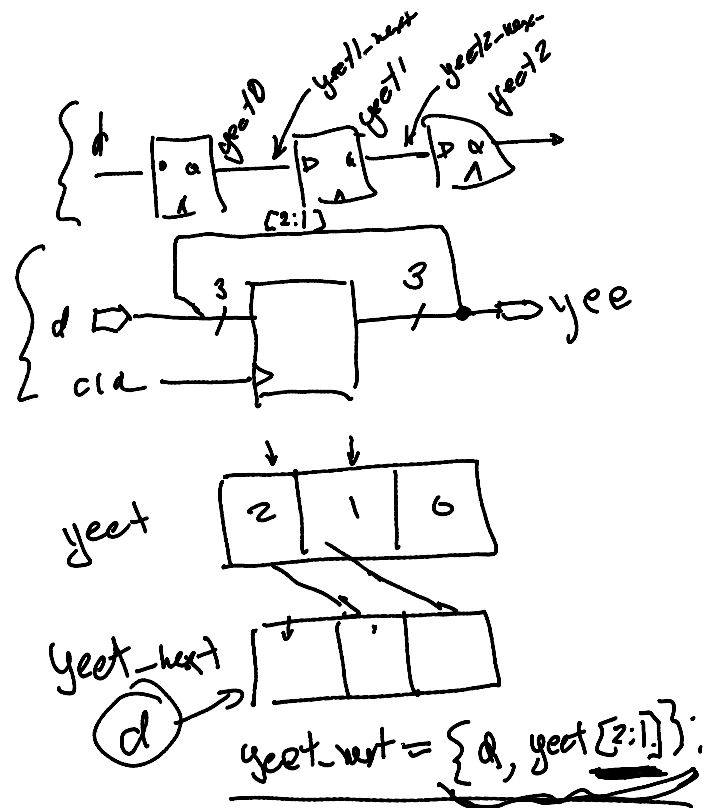

 Exercise 10: Label the specifications A through C as requirements or guaranteed responses.



input \rightarrow input : requirement

input \rightarrow output : response

output \rightarrow output : response