

## Flip-Flops and Registers

This lecture is an introduction to flip-flops and registers.

After this lecture you should be able to:

- convert between high/low logic levels and true/false truth values for active-high and active-low interfaces
- predict the relationship between the input and output waveforms of D flip-flops
- draw the output waveforms for registers, counter and shift registers
- write Verilog descriptions for these
- identify specifications on a timing diagram
- identify a specification as a requirement or guaranteed response

### Numbers, Logic Levels and Truth Values

Numbers are used for counting, logic levels are voltages, and truth values can be true or false. These are different, but related.

Almost universally, 1 and 0 are synonymous with true and false respectively. But there are two common conventions for the relationship between logic levels and truth values:

| Number | Truth | Active High | Active Low |
|--------|-------|-------------|------------|
| 0      | F     | L           | H          |
| 1      | T     | H           | L          |

Verilog uses the active-high convention: 0 and 1 are treated as low and high respectively.

Active-low signals can be denoted by:


- a bar over the signal name ( $\overline{\text{reset}}$ )
- an asterisk after the signal name (**RESET\***)
- a suffix of N (or n) after the signal name (**reset\_n**)

**Exercise 1:** Is a signal named  $\overline{\text{overload}}$  active-high or active-low? Is there an overload if this signal is high? What if the signal was named **overload**?

**Exercise 2:** Come up with an appropriate name for a signal that is at 3 V when a door is open and 0 V when the door is closed.

 
### D Flip-Flop

Consider the following circuit composed of two multiplexers:




When the clock input is 0, the output of the first multiplexer follows the input – the latch is “transparent”. When the clock input is 1, the output level is fed back to the input and held at that level<sup>1</sup>.

The symbol for the D flip-flop is:

 

The rising edge of a clock input causes the flip-flop to store the value of the input and make it available on the output. Thus the D flip-flop has a next-state input (D), a state output (Q) and a clock input. The D flip-flop’s state only changes on the rising edge of the clock.

 The D flip-flop “stores” one bit and is the memory element used in most sequential logic circuits.




<sup>1</sup>This is a “master-slave” flip-flop. The second, “slave,” latch holds the previously latched value when the clock is 0

**Exercise 3:** Fill in the waveform for the Q signal in the diagram above.

### Asynchronous Inputs


Asynchronous inputs:

 

can set (to H) or reset (clear to L) the flip-flop state independently of the clock. Ensuring reliable operation of circuits with asynchronous inputs is difficult. Asynchronous inputs are most often used to reset a circuit to a known state when it first powers up or when it fails. We will not use them in this course.


### Common Sequential Logic Circuits

Connecting multiple D flip-flops to the same clock so that all are loaded simultaneously creates a *register*. The notation on the right is for a register that is  $n$  bits wide.

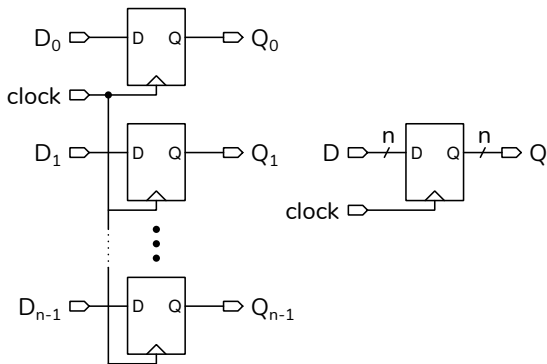


 **Exercise 4:** What would be another name for a 1-bit register?

A *counter* is a register whose value increases by 1 on each rising edge of the clock. It consists of a register whose input is the current value of the counter plus one:




On each clock edge the register loads a value that is one more than the previous value.

 


**Exercise 5:** Assuming a 3-bit counter, fill in the values of D and Q in the diagram above.

 **Exercise 6:** Draw the block diagram for a counter that: (a) counts up by 3? (b) counts down by 1? (c) whose value doubles on each clock edge?

A *shift register* is several registers with the output of each register connected to the input of the next register:



 On each rising edge of the clock the state of each register is transferred to the next one.



**Exercise 7:** Fill in the diagram above for a 4-bit shift register. Assume the initial value of each flip-flop is zero. Which is the oldest (first) value the D waveform? Which flip-flop holds the oldest value?

A shift register makes previous inputs available in parallel. This is useful for detecting sequences and for transferring data serially.

**Exercise 8:** Add parallel outputs to the shift register schematic. Draw a circuit whose output is high when the sequence 1, 0, 1, 1 is detected. Add the output of this circuit to the timing diagram above.

### Registers in Verilog


The following Verilog:

```

module ex2 (input logic d, clk,
           output logic q) ;
    always_ff @(posedge clk)
        q <= d ;
endmodule


```

synthesizes a D-flip-flop that transfers the **d** input to the **q** output on the rising (positive) edge of **clk**:

 

**Exercise 9:** What would you change to make an 8-bit register? A 4-bit counter? A 3-bit shift register? Follow the course coding conventions.

## Digital Waveforms

 

A transition from low to high is called a rising edge. The time it takes is called the rise time. A transition from high to low is called a falling edge. The time it takes is called the fall time. Two adjacent edges define a pulse, which can be negative or positive. The time between these is called the pulse width.

Rise and fall times are typically measured between 10% and 90% of the swing. Other measurements are typically made between 50% levels. But there are exceptions.

A signal consisting of periodic pulses is a clock. The inverse of the clock period is the clock frequency.

## Timing Specifications

Timing specifications can be:


**requirements:** the manufacturer requires that these specifications be met for a device to operate properly, or

**guaranteed responses:** the manufacturer guarantees that these specifications will be met.

Since the device manufacturer cannot control the timing on inputs but can guarantee the timing of outputs, a simple rule to distinguish requirements from responses is:

- requirements are measured from a transition on an input *to a transition on an input*.
- guaranteed responses are measured from a transition on an input or an output *to a transition on an output*.


Timing diagrams show the relationship between transitions on inputs and outputs. They are not drawn to scale. Both high and low levels are shown when the specification applies to both.

 

 **Exercise 10:** Label the specifications A through C as requirements or guaranteed responses.

Combinational logic circuits and D flip-flops have one important timing specification: their propagation delay. This is the delay from a change on an input to the corresponding change on an output. The usual symbols are  $t_{PD}$  for propagation delay and  $t_{CO}$  for the clock-to-output delay for a D flip-flop.

D flip-flops have two important timing requirements:



**setup time** the D input must be at a valid logic level for at least  $t_s$  before the rising edge of the clock

**hold time** the D input must remain a valid logic level for at least  $t_h$  after the rising edge of the clock

Timing analysis, be covered later, involves determining whether the timing requirements of the devices in a circuit will be met.