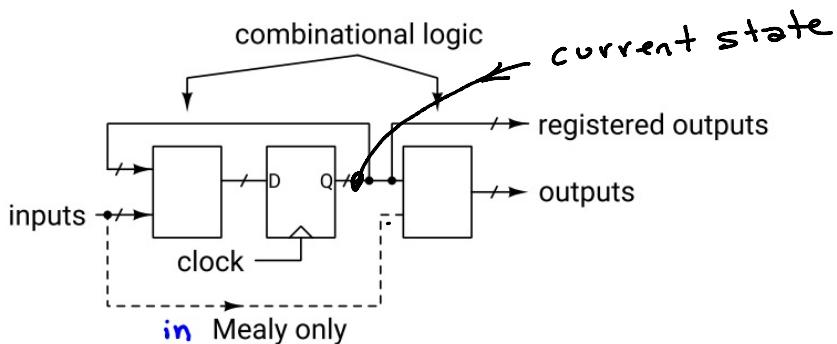


State Machines

Exercise 1: Which signal in the above diagram represents the current state?



Exercise 2: Which outputs change on the rising clock edge? Which change when the input changes?

- Q — state
- only on a Mealy SM do outputs change when i/p's change.

Exercise 3: Why?

for Moore SM each o/p is
a function of the state so
need one state per o/p value.

Exercise 4: If we used 8-bits of state information, how many states could be represented? What if we used 8 bits of state but used a "one-hot" encoding?

binary : $2^8 = 256$ possible states $00 \rightarrow FF$
 $0 - 255$

one-hot : $\begin{matrix} 0000 & 0001 \\ \vdots & \end{matrix} \} 8 \text{ possible states.}$

$\begin{matrix} 1000 & 0000 \\ \vdots & \end{matrix} \} X \rightarrow \text{not one-hot}$


$\begin{matrix} 0000 & 0000 \end{matrix}$

Exercise 5: What happens if both reset and enable are asserted?



resets to 00

Exercise 6: Draw the state transition diagram.

count		input		next count	
[1]	[0]	reset	enable	[1]	[0]
X	X	1	X	0	0
a	b	0	0	a	b
0	0	0	1	0	1
0	1	0	1	1	0
1	0	0	1	1	1
1	1	0	1	0	0

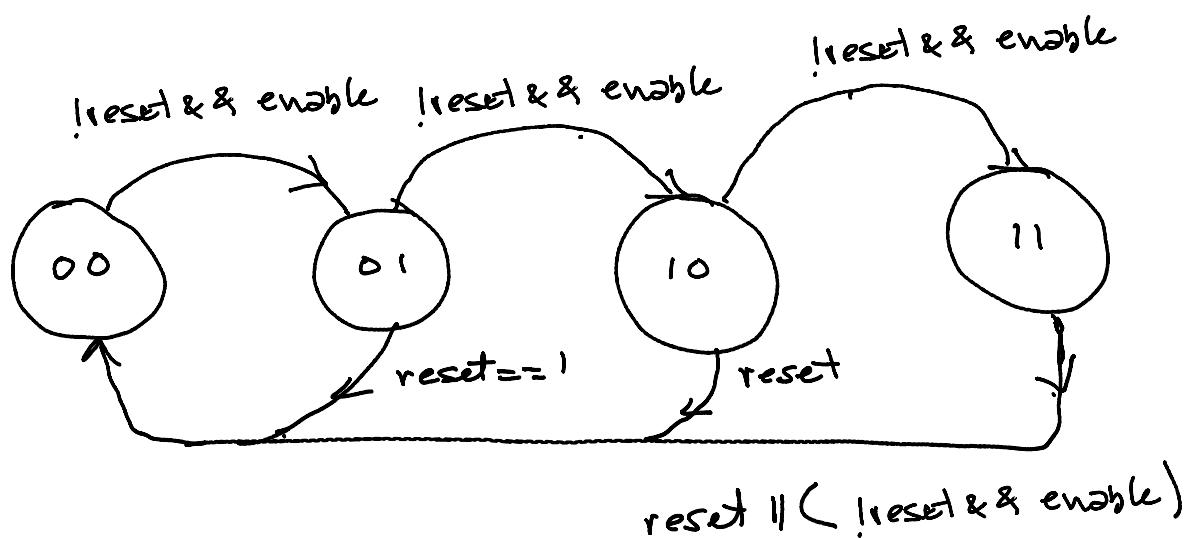

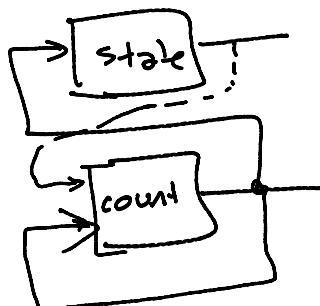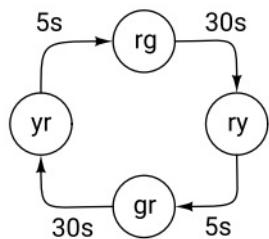Exercise 7: Write the state transition table for each state machine.



state	count +	next state
rg	0	ry
- ry	0	gr
gr	0	yr
- yr	0	rg
*	0	s

count	count, state	next count
0	0 : ry, gr	2^9
0	0 : gr, rg	4
n (#0)	x x	n-1

count	state next	count next
0	gr, rg ry, yr	2^9 4

Exercise 8: What is the size of the expression $\text{sqrt} * \text{sqrt}$? Of $\{8'b0, \text{sqrt}\} * \text{sqrt}$?

$$\begin{array}{l} \text{sqrt is } 8 \text{ bits} \\ \boxed{\text{sqrt} * \text{sqrt}} \quad 8 \text{ bits} \\ 8 * 8 = 64 \\ \text{max}(8, 8) = 8 \end{array}$$

$$\{8'b0, \text{sqrt}\} \quad 8 + 8 = 16 \text{ bits}$$

$$\underbrace{\{8'b0, \text{sqrt}\}}_{16 \text{ bits}} * \underbrace{\text{sqrt}}_{8 \text{ bits}} \Rightarrow \max(16, 8) = 16 \text{ bits.}$$

Exercise 9: Draw the state transition diagram (use $\Delta = 0$ and $\Delta \neq 0$ as the states).

