


## Introduction to Digital Design with Verilog HDL

**Exercise 1:** What changes would result in a 3-input OR gate?


```
module ex1 (input logic a, b, c,  
            output logic y);
```

```
    assign y = a | b | c;
```


```
endmodule
```

 

**Exercise 2:** What schematic would you expect if the statement was `assign y = ( a ^ b ) | c ;`?

 

**Exercise 3:** If the signal  $i$  is declared as `logic [2:0] i;`, what is the 'width' of  $i$ ? If  $i$  has the value 6 (decimal), what is the value of  $i[2]$ ? Of  $i[0]$ ?

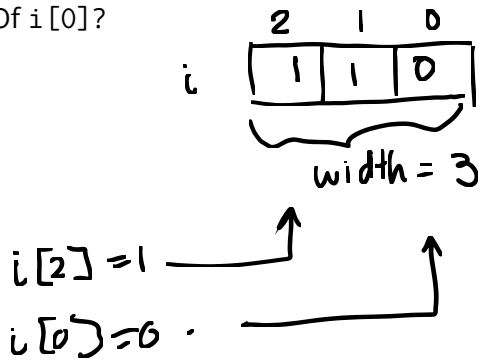

**Exercise 4:** What are the ~~sizes~~<sup>length</sup> and values, in decimal, of the following: `4'b1001`, `5'd3`, `6'h0_a`, `3?`

	length	value
<u>4'b1001</u>	4	9
5'd3	5	3
6'h0_a	6	10
3?	32	3

**Exercise 5:** An array declared as logic [15:0] n; and has the value 16'h1234.

What are the values and lengths of the following expressions?

$n[15:13] - 3'b000 \equiv 000$   
 $!n \rightarrow 0$   
 $\sim n[3:0] \rightarrow 1011$   
 $n + 1'b1$   
 $n[7:0] - n[3:0]$   
 $n \geq 16'h1234 \rightarrow 1$   
 $n \wedge \sim n$   
 $n \&\& !n$   
 $n * (n + 1'b1)$

16'h1234 = 0001 0010 0011 0100

$\sim n[3:0] \rightarrow 1011$


$$\begin{array}{r}
 n: \quad 0001 \quad 0010 \quad 0011 \quad 0100 \\
 + \quad 0000 \quad 0000 \quad 0000 \quad 0001 \\
 \hline
 0001 \quad 0010 \quad 0011 \quad 0101
 \end{array}$$

$$\begin{array}{r}
 n[7:0] = \quad 0011 \quad 0100 \quad 8'h34 \\
 n[3:0] \quad 0000 \quad 0100 \quad - 8'h04 \\
 \hline
 0011 \quad 0000 \quad 8'h30
 \end{array}$$

$n \wedge (\sim n)$   
 XOR



$$\begin{array}{r}
 \sim n \quad 1110 \quad 1101 \quad 1100 \quad 1011 \\
 n \quad 0001 \quad 0010 \quad 0011 \quad 0100 \\
 \hline
 1111 \quad 1111 \quad 1111 \quad 1111
 \end{array}$$

**Exercise 6:** What is the value of the expression  $3 ? 10 : 20$ ? Of the expression  $x ? 1 : 0$  if  $x$  has the value 0? If  $x$  has the value -1?

 

**Exercise 7:** Draw the schematics corresponding to:


$y = a ? ( b ? s1 : s2 ) : ( c ? s3 : s4 );$   
 $y = a ? s1 : b ? s2 : c ? s3 : s4;$

  

 
**Exercise 8:** Use slicing and concatenation to swap the order of the bytes in  $n$ .

What is the value and length of  $\{n[7:0], n[15:8], 4'b1111\}$ ?

Use concatenation to shift  $n$  left by two bits



swap bytes :  $\{n[7:0], n[15:8]\}$

 

value : 20'h 3912f length =  $16 + 4 = 20$  bits.

Shift left by 2 bits

$\{n, 2'b00\} \rightarrow 18$  bits

$\{n[15:0], 2'b00\} \rightarrow 16$  bits

**Exercise 9:** What would you change to make an 8-bit register? A 4-bit counter? A 3-bit shift register? Follow the course coding conventions.