


State Machines

This lecture defines state machines and describes how to document them and how to implement them using Verilog. After this lecture you should be able to: design a state machine based on an informal description of its operation, document it using state transition diagrams and tables, write a synthesizable Verilog description of it and convert between these three descriptions. Revision 3: corrections and clarifications.

Introduction

The *state* of a register is its value. A *state machine* is a description of how the state changes in response to inputs.

 The schematic of a state machine is a register whose next value is selected by a combination of inputs and the current state:



State Machine Descriptions

State machines can be described by state-transition tables or state-transition diagrams.


A state transition table has columns for the current state, the input value(s), and the corresponding next state.

The example below is for a motor controller with one bit of state and two inputs: one starts the motor and one stops it. The motor stops if both are asserted:

current state	inputs		next state
	start	stop	
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

A state machine can also be described using a state transition diagram. Each state is represented by a circle labelled with the state. Lines with arrows show

 transitions between states and the input conditions needed for that transition. The state transition diagram for this state machine would be:



State transitions, which are changes in the register value, happen at the rising edge of the clock.


State transition diagrams may omit transitions that don't result in a change of state (e.g. from 0 to 0 or from 1 to 1).

Exercise 1: Draw the schematic for this state machine. Write an `always_ff` statement that implements this state machine.

State Machine Outputs

We can generate outputs that depend on the state.

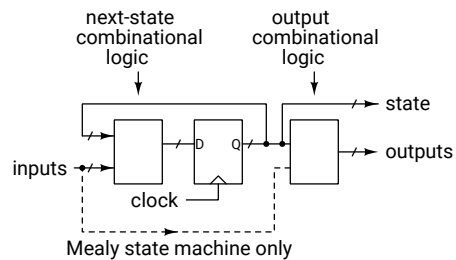For a *Moore* state machine the outputs are a function of the current state (only). For a *Mealy* state machine¹ the outputs are also a function of the current inputs:



We can often choose state encodings where the state is also the output. Otherwise, the output for each state can be documented as another column in the state transition table or added to each circle in the state transition diagram.

¹We will not cover Mealy state machines in this course.

Interacting State Machines

Circuits often contain multiple state machines. The state of one can be an input to another.

For example, a multi-digit BCD counter may contain several single-digit counters. The value of a counter would increment when the next-less-significant digit value was 9.


Another example would be the traffic light controller example below. One register represents which lights are turned on. Another register is the number of seconds remaining before the transition to the next light state.

Sequence Generators

Sequence generators are state machines that produce a desired sequence of values. Typical inputs may include those to restart the sequence (typically called reset), pause or continue the sequence (hold or enable), or change the values generated (e.g. up/down, increment, or maximum value inputs).

Counter

 The state transition state diagram and for a two-bit counter with a reset input is:



A simple way to convert a state transition diagram to Verilog is to write one conditional expression for each transition in the diagram. This expression includes the starting state and the transition condition. Only one of these logical expressions will be true and so they can be written in any order.

If an expression is true then the state is set to the ending state for that transition. If none of the conditions match then the state is set to its current value and so it doesn't change.

```
// 2-bit counter with reset
```

```
module ex53
  ( output logic [1:0] count,
    input logic reset, clk );

  always_ff @(posedge clk) count
```

```
<= count == 2'b00 && !reset ? 2'b01 :
count == 2'b01 && !reset ? 2'b10 :
count == 2'b10 && !reset ? 2'b11 :
count == 2'b11 ? 2'b00 :
count == 2'b01 && reset ? 2'b00 :
count == 2'b10 && reset ? 2'b00 : count ;
```

```
endmodule
```

Two conventions can simplify state transition tables: (1) An x (“don’t care”) can replace values that don’t affect the next state. Each x halves the number of lines needed. (2) Arithmetic expressions can replace lines where the next state can be computed from the current state or the input.

We can write the state transition table for this counter in 3 lines rather than 8 as:

count	reset	next count
xx	1	00
11	0	00
<i>n</i>	0	<i>n</i> + 1

and the Verilog would be:


```
// 2-bit counter with reset
```

```
module ex56
  ( output logic [1:0] count,
    input logic reset, clk );

  always_ff @(posedge clk) count
    <= reset ? 2'b00 :
    count == 2'b11 ? 2'b00 :
    count + 1'b1 ;
```

```
endmodule
```

 Exercise 2: Simplify the solution using the fact that addition of 1 to 3 “wraps” a 2-bit value to 0. What would you change so the counter does not “wrap around” from 2'b11 to 2'b00?



Timers and Clock Dividers

We can create delays by counting clock cycles. It takes N clock periods for a counter to count down² from $N - 1$ to 0. If the clock period is T then the delay is NT .

Exercise 3: What value of N would give a 20 ms delay if the clock frequency is 50 MHz? How many bits are needed for this timer's register?

²Timers usually count down from $N - 1$ to 0 rather than up from 0 to $N - 1$ because it's simpler to determine when the count has reached 0.

 



Figure 1: Simulation of traffic light controller.

If the counter is reset to $N - 1$ when it reaches 0 then the count values will be periodic with a period NT .

 
Exercise 4: Assume the timer above is reset to $N - 1$ each time it reaches 0. For how long is the register value 0? What are the period and frequency of a signal that is inverted each time the count reaches 0?

Traffic Light Controller

This is a controller for a traffic light at an intersection:




 It combines two state machines: one to sequence the traffic lights and one as a timer. The states are encoded as 6-bit values with the on/off values of the (Red, Green, Yellow) lights in each direction:




Delays are implemented by decrementing a counter on each clock edge. When the counter reaches zero the state register is loaded with the next state and the counter register is loaded with the duration of the next state.

 The state transition diagram for the light state machine is:



and for the timer:

 

A Verilog module implementing this state machine is:

```
// traffic light controller
module ex54
  ( output logic [5:0] lights,
    input logic reset, clk );

  typedef enum logic [5:0] // RYG RYG
    { rg=6'b100_001, ry=6'b100_010,
      gr=6'b001_100, yr=6'b010_100 }
    lightstate ;

  logic [4:0] count ;

  // next traffic light lights
  always @(posedge clk) lights
    <= reset ? rg :
      count ? lights :
      lights == rg ? ry :
      lights == ry ? gr :
      lights == gr ? yr : rg ;

  // state durations
  always @(posedge clk) count
    <= reset ? 29 :
      count ? count-1 :
      lights == rg || lights == gr ? 4 : 29 ;

endmodule
```

An enumerated type, **lightstate**, allows us to use more meaningful symbolic names (**rg**, **ry**, **gr**, and **yr**) for the four possible values of the **state** register.

The simulation results are shown in Figure 1.

Exercise 5: Write the state transition table for the state machine for the **lights** output.


Sequence Detectors

This type of state machine detects particular sequences of input values. Examples include detecting a change in an input, a specific sequence of input values or the duration of an input.

The most general implementation of a sequence detector is a shift register that stores previous inputs. Outputs are generated based on previous inputs – the values in the shift register. However, a simpler implementation is often possible as shown in the examples below.

Detecting Changes

 An edge detector detects the change of an input between clock edges. The state is the input at the two most recent clock edges. For example, **10** means the two most recent inputs were **1** followed by **0**. The **rising** output is true when the input changed from low to high. The **falling** output is true for the opposite change. store the




Exercise 6: For which states would **falling** be asserted? **rising**? Draw the schematic and write the Verilog for this state machine. Assume an input **in** and a 2-bit register **bits** that holds the two most recent input values.

Detecting Sequences of Values

In this example, a combination lock, the state is the most recent four input digits. Combinational logic asserts an **unlock** output when the most recent four inputs match the passcode (1,2,3,4 in this example).

```
// digit-sequence detector
module ex24 ( output logic unlock,
             input logic [3:0] digit,
             input logic clk );
    logic [15:0] digits ;
    // next-state logic
    always_ff @(posedge clk) digits
```

```
<= { digits[11:0], digit } ;
// sequence detector output
assign unlock
    = digits == { 4'd1, 4'd2, 4'd3, 4'd4 } ?
      '1 : '0 ;
endmodule
```

 

Exercise 7: How could you modify the code so that **digits** is only updated when an **enable** input is asserted?

Exercise 8: How many states can this state machine have?



A simpler implementation would count the number of digits that had been entered in the correct order.

Exercise 9: Draw the state transition diagram for this simpler implementation. How many states are there? Write the Verilog using a 3-bit count state variable.

Detecting Durations

Most mechanical switches briefly interrupt the connection when they switch. A switch debouncer eliminates the extra edges on a switch input.

The debouncer below uses two state machines: a timer to delay changing the output until the input has been stable for *N* clock cycles and one to hold the current output value until the timer expires. The timer uses a register named **count** and the input and output are named **in** and **out** respectively.

  

Exercise 10: Write **always_ff** statements that implement these two state machines.

 


Figure 2: Simulation of the calculation of square root of 1234.

RTL Controller

“Algorithmic state machines” control the computation of numerical results. A state machine, called the “controller,” controls the values loaded into registers, called the “datapath,” which hold numerical values. This is called Register Transfer Level (RTL) design.

This example computes the square root of an input number by [bisection](#).

The datapath contains two registers: one holds the current best estimate of the square root, `sqrt`, and the other the search interval, `delta`. On reset, `sqrt` is loaded with the number whose square root it to be computed and `delta` is set to half of the maximum value. The controller state machine consists of a one-bit register, `done`, which is reset to 0 and set to 1 when `delta` reaches 0.

Note that `delta_next`, the input to the `delta` register, is a separate signal. This allows `done` to be set to 1 at the same clock edge as `delta` is set to zero.

```

module ex41
(
  input logic [15:0] n,
  input logic reset, clk,
  output logic [7:0] sqrt,
  output logic done
) ;

  logic [7:0] delta, delta_next ;

  always_ff @(posedge clk) sqrt
    <= reset ? 8'd128 :
      {8'b0, sqrt} * sqrt < n ?
        sqrt + delta : sqrt - delta ;

  assign delta_next
    = reset ? 8'd128 : delta/2 ;

  always_ff @(posedge clk) delta
    <= delta_next ;

  always_ff @(posedge clk) done
    <= delta_next == 0 ;
endmodule

```

Figure 2 shows the calculation of the square root

of 1234.

Exercise 11: What is the size of the expression `sqrt*sqrt`? Of `{8'b0, sqrt}*sqrt`?

Exercise 12: Draw the state transition diagram for `done`.

One-Hot State Encodings

“One-hot” state encodings use one flip-flop per state and only one flip-flop at a time may be set to 1. This requires more flip-flops but may require less combinational logic. For the first example (the motor controller) the two states could be encoded in two different ways:

state	binary encoding	one-hot encoding
off	0	10
on	1	01

Exercise 13: If we used 8-bits of state information, how many states could be represented? What if we used 8 bits of state but used a “one-hot” encoding?