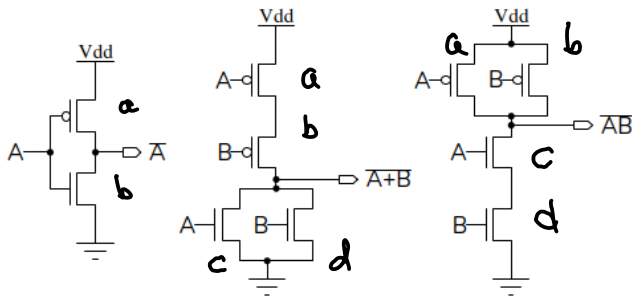


Implementation of Digital Logic Circuits

Exercise 1: Which transistors are on when the output is high? When it is low? In which direction does the output current flow in each case?



	NOT	NOR	NAND	current
low	b	c or d	c and d	in
high	a	a and b	a or b	out

Exercise 2: Which of these specifications does the manufacturer guarantee? Which are requirements?

V_{OH} , V_{OL} - guaranteed (outputs)
 V_{IH} , V_{IL} - requirements (inputs)

Exercise 3: A logic family has $V_{OH}(\min) = 5\text{ V}$, $V_{OL}(\max) = 0.5\text{ V}$, $V_{IH}(\min) = 4\text{ V}$ and $V_{IL}(\max) = 1.5\text{ V}$. What are the noise margins?


$$\begin{array}{c}
 5\text{ V} \\
 \hline
 0.5\text{ V}
 \end{array}
 \left|
 \begin{array}{c}
 \overline{\underline{\underline{4}}} \\
 \underline{\underline{1.5}}
 \end{array}
 \right.
 \begin{array}{l}
 5 - 4 = \rightarrow 1\text{ V} \\
 1.5 - 0.5 = \rightarrow 1\text{ V}
 \end{array}$$

Exercise 4: All else being equal, by how much would we expect to decrease power consumption when reducing logic levels from 5 V to 3.3 V? What would be the effect on power consumption in reducing the clock frequency from 50 MHz to 1 MHz?

$$\frac{P_2}{P_1} = \left(\frac{3.3}{5}\right)^2 = 0.4 \quad (\text{reduced by } 60\%)$$

$$\frac{P_2}{P_1} = \left(\frac{1}{50}\right) = 0.02 \quad (\text{reduced by } 98\%)$$

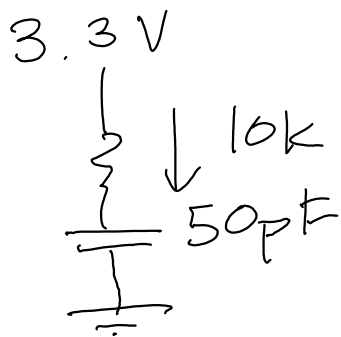Exercise 5: What are the active-state current and the RC time constant for a wired-or interrupt-request line using a 10kΩ resistor pulling up a circuit with 50 pF capacitance to 3.3 V?



$$I = \frac{V}{R} = \frac{3.3}{10k} = 0.33 \text{ mA}$$


$$P = 1 \text{ mW}$$

$$V(t) = 3.3 \left(1 - e^{-t/RC}\right)$$

$$\tau = RC = 10 \times 10^3 \cdot 50 \times 10^{-12}$$

$$= 500 \times 10^{-9} \text{ s.}$$

$$= 0.5 \mu\text{s}$$

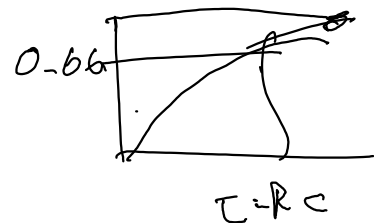

Exercise 6: How many square mm of PCB area does each package require? Which packages have their pins accessible when the packages is placed on the PCB?

$$22 \times 22 = 484 \text{ mm}^2 \quad \leftarrow \text{accessible pins}$$

$$3.5 \times 3.5 = 12.25 \text{ mm}^2 \quad \leftarrow \text{PCB pads covered by package}$$