

## Solutions to Quiz 1

### Question 1

There were four versions of this question with two different bit widths, and two different output signal names and behaviour.

Write a Verilog module named `check` with two 15 (or 7)-bit inputs named `s1` and `s2` and a 1-bit output named `both` (or `either`). `both` (or `either`) should be set to 1 if both `s1` and `s2` (or either `s1` or `s2`) are non-zero. `both` (or `either`) should be set to zero otherwise. Declare arrays with decreasing bit order.

### Answer

Some correct and incorrect solutions are shown below. Incorrect solutions include examples that the give incorrect results.

```

module check
(
  input logic [6:0] s1, s2,
  // input logic [14:0] s1, s2,
  // output logic both ) ;
  output logic either ) ;

  /* correct: */

  // assign both = s1 && s2 ;
  // assign both = s1 && s2 ? '1 : '0 ;
  // assign both = s1 ? ( s2 ? '1 : '0 ) : '0 ;

  assign either = s1 || s2 ;
  // assign either = s1 || s2 ? '1 : '0 ;
  // assign either = s1 ? '1 : ( s2 ? '1 : '0 ) ;

  /* incorrect: */

  // incorrect: 2&1 = 0
  // assign both = s1 & s2 ;

  // incorrect: 7'd64*7'd02 = 0
  // assign both = s1 * s2 ? '1 : '0 ;

  // incorrect: 2|2 = 0 (truncated to 1 bit)
  // assign either = s1 | s2 ;

  // incorrect: b7'd64+7'd64 = 0 (overflow)
  // assign either = s1 + s2 ? '1 : '0 ;

```

endmodule

A “testbench” module that tests the solution is shown in Appendix A.

### Question 2

Given the following Verilog declarations:

```

logic [11:0] x = 12'd32 ;
logic [7:0] y = 8'b101 ;

```

or

```

logic [11:0] x = 12'd64 ;
logic [7:0] y = 8'b111 ;

```

fill in in the table below with the value of the each expression as a hexadecimal (base 16) number (Verilog format not necessary) and the length (number of bits) as a decimal (base 10) number:

expression	value (in hexadecimal)	length (in bits, decimal)
<code>{y,y}</code>		
<code>x[7:4]</code>		
<code>x &amp;&amp; y</code>		
<code>x + y</code>		

### Answer

For the first version of the question these are:

```

{y,y}: value: 505 bits: 16
x[7:4]: value: 2 bits: 4
x && y: value: 1 bits: 1
x + y: value: 25 bits: 12

```

and for the second:

```


{y,y}: value: 707 bits: 16
x[7:4]: value: 4 bits: 4
x && y: value: 1 bits: 1
x + y: value: 47 bits: 12

```


A Verilog module in Appendix A displays the values and lengths of each expression.
 
### Question 3

Write a Verilog statement that would implement the schematic on the right. You can assume it would replace the “missing statement” comment in the `quiz1` module:



or

 

```

module quiz1
  ( input logic [5:0] x, y,
    input logic a,
    output logic [5:0] r );
  // missing statement
endmodule

```

### Answer

The statements for the two schematics are:

```
assign r = a ? x+y : x-y ;
```

and

```
assign r = a ? x-y : x+y ;
```

respectively.

The synthesis results are shown in Appendix A.

## Appendix A

### Question 1 Testbench

```

module test ;
  logic a, b, c, d ;
  check c0 (0,0,a) ;
  check c1 (0,2,b) ;
  check c2 (64,0,c) ;
  check c3 (64,2,d) ;
  initial begin
    #1 ;
    $display(a,b,c,d) ;
  end
endmodule

```

The result for **both** should be 0001 (only the last test case outputs a 1) and the result for **either** should be 0111 (only the first test case outputs a 0).

### Question 2 Testbench

```

`define ans(expr) \
  $display("%16s: value: %0h bits: %2d", \
    `expr`, expr, $bits(expr)) ;
module test ;
  logic [11:0] x = 12'd32 ;

```

```

logic [7:0] y = 8'b101 ;
// logic [11:0] x = 12'd64 ;
// logic [7:0] y = 8'b111 ;
initial begin
  `ans({y,y})
  `ans(x[7:4])
  `ans(x && y)
  `ans(x + y)
end
endmodule

```

### Question 3 Synthesis Results

In the schematics below subtraction is implemented by adding the two's complement (inverting the bits and adding 1).

