

Introduction to Digital Design with Verilog HDL

Exercise 1: What changes would result in a 3-input OR gate?

Exercise 2: What schematic would you expect if the statement was
`assign y = (a ^ b) | c ;?`

Exercise 3: What are the lengths and values, in decimal, of the following:

4' b1001?

5' d3?

6' h0_a?

3?

Exercise 4: If the signal `i` is declared as `logic [2:0] i;`, what is the 'width' of `i`?

If `i` has the value 6 (decimal), what is the value of `i[2]`?

Of `i[0]`?

Exercise 5: Use slicing and concatenation to compute the byte-swapped value of an array `n` declared as `logic [15:0] n`.

Exercise 6: If n has the value $16'h1234$, what is the value and length of:

$\{n[7:0], n[15:8], 4'b1111\}$?

Exercise 7: Use concatenation to shift n left by two bits.

Exercise 8: Use concatenation to assign the high-order byte of **n** to **a** and the low-order byte to **b**.

Exercise 9: An array declared as `logic [15:0] n;` and has the value `16'h1234`. What are the values and lengths of the following expressions?

`n[15:13]`

`!n`

`~n[3:0]`

`n>>4`

`n + 1'b1`

`n[7:0] - n[3:0]`

`n >= 16'h1234`

`n ^ '1`

`n && !n`

`n * (!n + 1'b1)`

Exercise 10: What are the length and value of the expression: $3 \cdot 16 \cdot d10 : 8 \cdot h20$?

If x has the value 0, what is the value of the expression: $x \cdot 1 \cdot b1 : 1 \cdot b0$?

If x has the value -1?

Exercise 11: Draw the schematics corresponding to:

$$y = a ? (b ? s1 : s2) : (c ? s3 : s4);$$

$$y = a ? s1 : b ? s2 : c ? s3 : s4;$$


Exercise 12:

```
assign y = a + 1 ;
```

Some software warns about truncation. How could you re-write the **assign** statement to avoid such a warning?

Exercise 13: Write an `always_ff` statement that toggles (inverts) its output on each rising edge of the clock.


Exercise 14:

 

Identify the following in the diagram above: component names, component "instance names," component port names, module port names. Label the signal `t` in the schematic.

Exercise 15: Rewrite the `ex60` module using operators. Which version – “structural” or “behavioural” – is easier to understand?

Exercise 16:

 

How would you specify the bit marked A in the diagram above?

The bits marked B?

The least-significant byte?

Exercise 17: Define a Verilog lookup table named **isprime** that can be used to determine if a value between 0 and 7 is a prime number or not. The result should be 1 if the value is a prime or else 2. *Hint: The primes are 2, 3, 5 and 7.*

Exercise 18: Write an expression giving the same result. Draw the corresponding block diagram.