

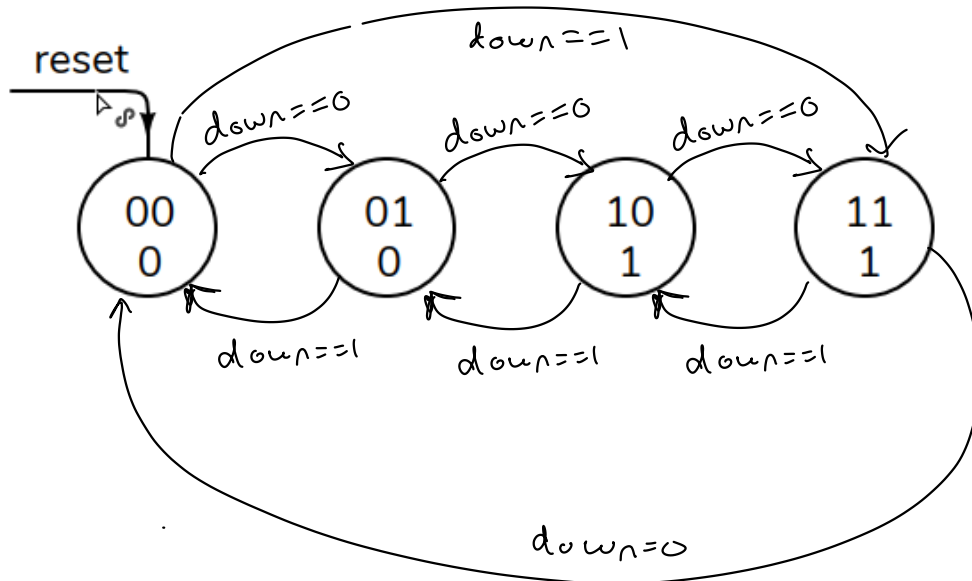


State Machines

Exercise 1: Modify the diagram so the state machine counts to 11 and stops. Add a down input that cause the values to count down.

 

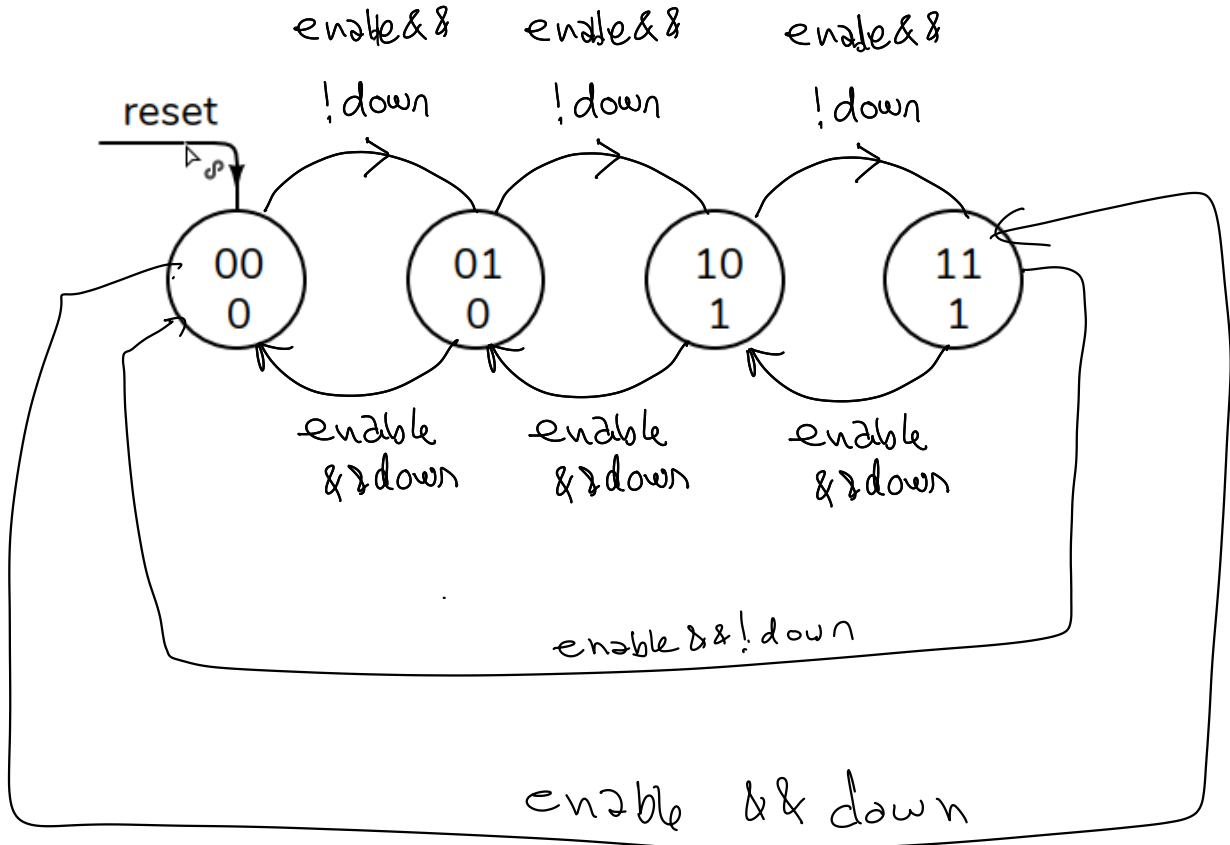Exercise 2: Show the state transition diagram and table for a 2-bit counter with reset, enable, and down inputs. Reset should have priority. Write the Verilog.



count	reset	enable	down	count
x x	1	x	x	0 0
n	0	0	x	n
t 1	0	1	0	0 0
0 0	0	1	1	1 1
n	0	1	0	n+1
n	0	1	1	n-1

Exercise 2: Show the state transition diagram and table for a 2-bit counter with reset, enable, and down inputs. Reset should have priority. Write the Verilog.

count	reset	enable	down	count ←
xx	1	x	x	00
n-	0	0	x	n
11	0	1	0	00
00	0	1	1	11
n	0	1	0	n+1
n	0	1	1	n-1

always_ff @(posedge clk) count <=

reset ? 2'b00 :

!enable ? count :

count == 2'b11 && !down : 2'b00;

Exercise 3: What value of N would result in a 20 ms delay if the clock frequency is 50 MHz? How many bits are needed for this timer's register?


clock frequency = $f = 50 \times 10^6 \text{ Hz}$
 clock period = $T = 20 \times 10^{-9} \text{ s}$
 delay = $t = NT = 20 \times 10^{-3}$
 clock cycles = $N = \frac{t}{T} = \frac{20 \times 10^{-3}}{20 \times 10^{-9}} = 10^6$

Exercise 4: Assume the timer above is reset to $N - 1$ each time it reaches 0. For how long is the register value 0? What are the period and frequency of a signal that is inverted each time the count reaches 0?

the register is 0 for one clock period.





 Exercise 5: Write the state transition table for the state machine for the lights output.



lights	reset	count	next lights
X	1	X	rg
rg	0	0	ry
ry	0	0	gr
gr	0	0	yr
yr	0	0	rg
n	0	≠ 0	n

  
Exercise 6: The example above is an N-bit shift register that shifts the bits right. Draw a block diagram and write the Verilog for a 6-bit shift register that shifts left.




always_ff @(posedge clock)

q <= { q[4:0], in } ;


Exercise 7:

 

 Fill in the diagram above for a 4-bit ($N = 4$) right-shift shift register. Assume the initial value is zero. Which bit is the oldest (first) value in the D waveform? Which bit of the shift register holds the oldest value? in



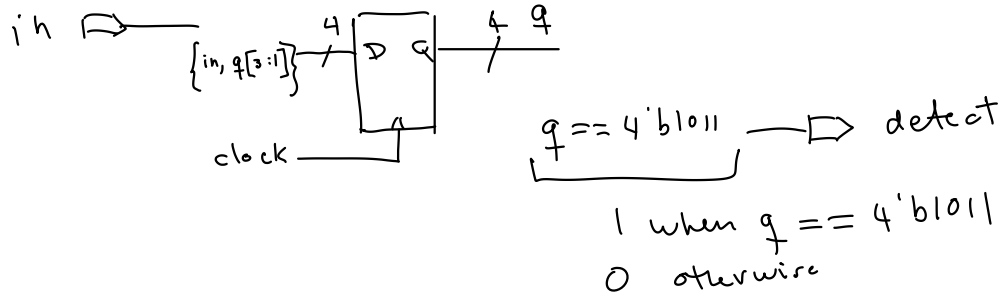Exercise 8: Draw a block diagram and write the Verilog for a circuit that sets an output named **detect** high when the sequence of values 1, 1, 0, 1 has appeared on an input named **in** on successive rising edges of the clock.



always_ff @(posedge clock)




q <= {in, q [3:1]};

assign detect = q == 4'b1011;

Exercise 9: For which states would **falling** be asserted? **rising**? Draw the schematic and write the Verilog for this state machine. Assume an input **in** and a 2-bit register **bits** that holds the two most recent input values.

10 → falling

01 → rising

 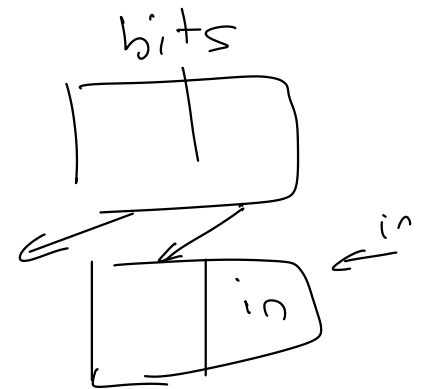 

bits == 2'b01 → rising
bits == 2'b10 → falling

```
module ex9 (
    input logic in, clock,
    output logic rising, falling);
```


```
logic [1:0] bits;
```

```
always_ff @(posedge clock)
    bits <= {bits[0], in};
```

```
assign rising = bits == 2'b01;
assign falling = bits == 2'b10;
```

```
endmodule
```

 Exercise 10: Write `always_ff` statements that implement these state machines.



`always_ff @ (posedge clock)`

`out <= count != 0 ? out : in;`

count	in == out	next count
x	1	N - 1
0	x	N - 1
n	0	n - 1

`always_ff @ (posedge clock)`

`count <= in == out || count == 0 ? N - 1 : count - 1;`