

Exercise 11: How could you modify the code so that **digits** is only updated when an **enable** input is asserted?


```
always_ff @(posedge clk) digits
  <= { digits[1:3], digit } ; -
```

```
always_ff @(posedge clk) digits
  <= enable ? { digits[1:3], digit } : digits,
```

Exercise 12: How many states can this state machine have?

There are 10 possible values for each digit
 so there are $10 \times 10 \times 10 \times 10 = 10^4 = 10,000$
 possible states.


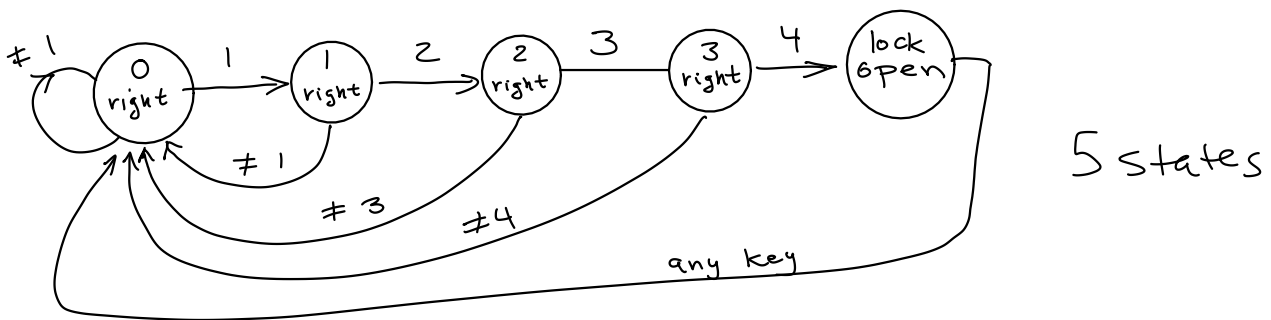
Exercise 13: Draw the state transition diagram for this simpler implementation. How many states are there? Write the Verilog using a 3-bit **count** state variable.



5 states


```
logic [2:0] count;
always_ff @(posedge clk)
  count <= count == 0 && digit == 1 ? 1 :
           count == 1 && digit == 2 ? 2 :
           count == 2 && digit == 3 ? 3 :
           count == 3 && digit == 4 ? 4 : 0;
assign unlock = count == 4;
```

  Exercise 14: How much logic is required to detect a state when a binary encoding is used? With a one-hot encoding?



need
n-bit
AND to
detect a
state
for 2^n states

binary encoding

 

no logic
needed.

+ encoding

w/ binary encoding.

Exercise 15: If we used 8 bits of state information, how many states could be represented? What if we used 8 bits of state but used a "one-hot" encoding?

binary: $2^8 = 256$ {

0	0	0	0	0	0	0	0
0	0	0	0	0	0	0	1
⋮							
1	1	1	1	1	1	1	1

}

one-hot: 8 {

1	0	0	0	0	0	0	0
⋮							
0	0	0	0	0	0	0	1

}