
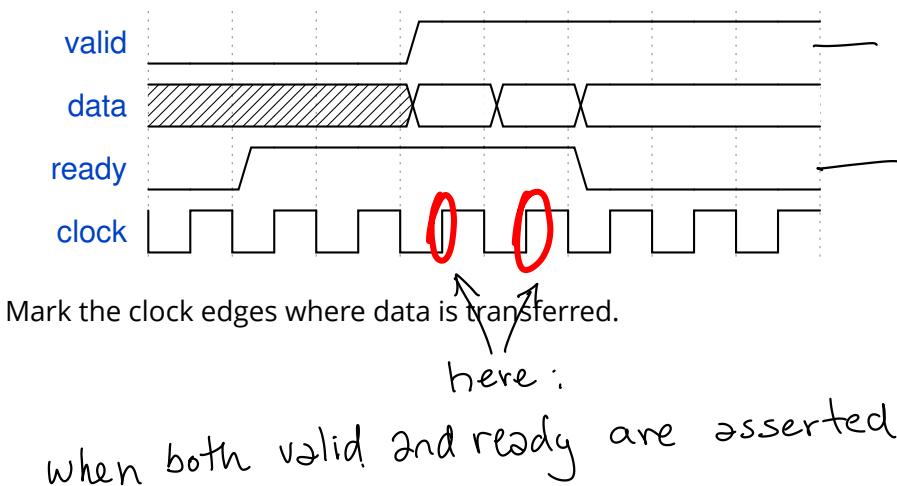


## Interfaces

### Exercise 1:

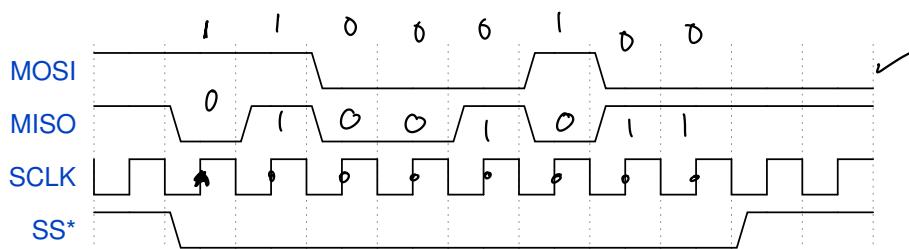

### Exercise 2:



The diagram above shows a transfer over an SPI bus. How many bits of data are transferred? What is the value, in decimal, of the data transferred from the master to the slave? From the slave to the master?


- 8 bits (rising clock edges while  $\overline{SS}$  is asserted).
- from master to slave (MOSI):

$$\underbrace{1 \quad 1 \quad 0 \quad 0}_{8'h C} \quad \underbrace{6 \quad 1 \quad 0 \quad 0}_{8'h 4} = 196_{10}$$

- from slave to master (MISO)

$$\underbrace{0 \quad 1 \quad 0 \quad 0}_{8'h 4b} \quad \underbrace{1 \quad 0 \quad 1 \quad 1}_{8'd 75}$$

### Exercise 3:

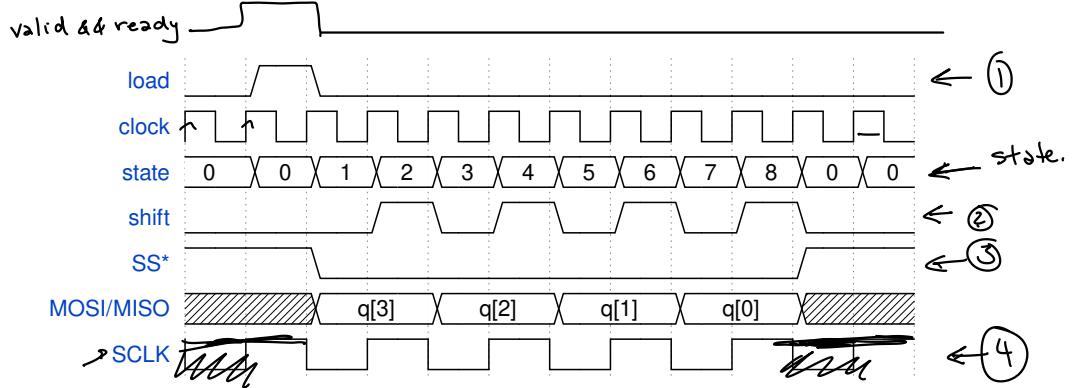

valid &  
ready


state	state_next

Based on the diagram above, write a state transition table for an SPI interface controller that transfers four bits at a time. Include an idle state. In which states are SCLK and SS asserted?

SCLK is asserted in states 0, 2, 4 ... 8

assign       $sclk = !state[0];$   
 assign       $ss_n = state == 0;$   
 assign       $shift = state == 2 \text{ || } state == 4 \text{ || } state == 6 \text{ || } state == 8;$   
 assign       $load = valid \& \& ready;$

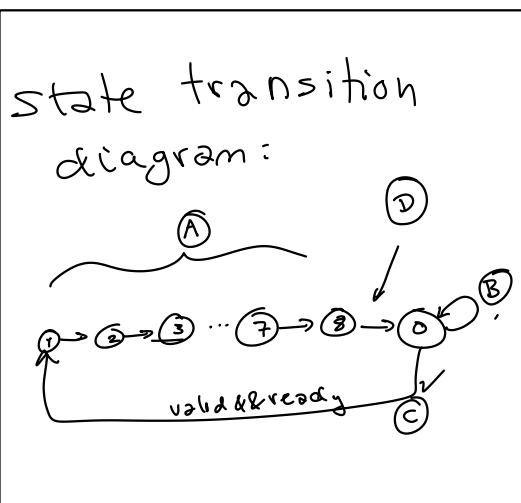assign       $state\_next =$   
 $!state \& \& valid \& \& ready ? 1 : c$



$!state ? 0 : B$

$state == 8 ? 0 : D$

$\frac{state ? state + 1 : state}{1 \dots 7} A$