 



Timing Analysis

Exercise 1:



The diagram above shows an oscilloscope screen capture that includes one period of an active-low digital waveform. The scale on the horizontal axis is 20 ns per division. What are: the rise time, period, positive pulse width and duty cycle?

Exercise 2:

 

Label the specifications A through D as requirements or guaranteed responses. Which specifications are measured to a signal being in a high-impedance state? Which are measured from a rising edge only? From either?

Exercise 3: Is t_{PD} a requirement or a guaranteed response?

Exercise 4: Is t_{SU} a requirement or a guaranteed response? How about t_{H} ?

Exercise 5:

$$t_{\text{SU}} (\text{avail}) = T_{\text{clock}} - t_{\text{CO}} (\text{max}) - t_{\text{PD}} (\text{max})$$

Which of the specifications in the formula above decrease the available setup time as they increase? Which increase it?

Exercise 6: For a particular circuit f_{clock} is 50 MHz, t_{CO} is 2 ns (maximum), the worst-case (maximum) t_{PD} in a circuit is 15 ns and the minimum setup time requirement is 5 ns. What is the setup time slack? Will this circuit operate reliably? If not, what is the maximum clock frequency at which it will?

Exercise 7: What is the maximum clock frequency for a counter using flip-flops with 200 ps setup times, 50 ps hold times and adder logic that has a 250 ps propagation delay?