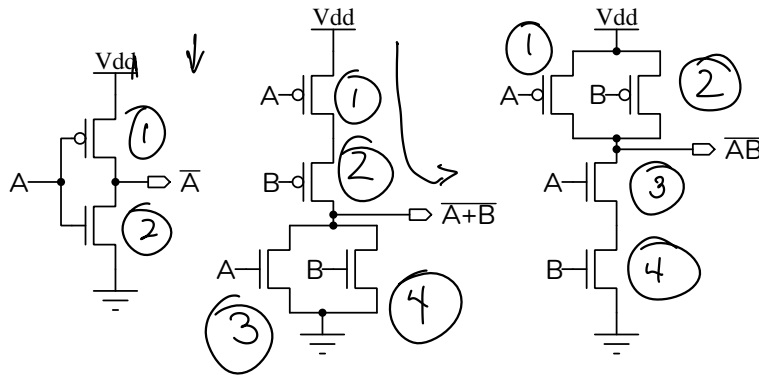


Implementation of Digital Logic Circuits

Exercise 1:




Which transistors are on when the output is high? When it is low?
In which direction does the output current flow in each case?

	NOT		NOR		NAND	
output:	H	L	H	L	H	L
ON:	1	2	1 and 2	3 or 4	1 or 2	3 and 4
OFF:	2	1	3 and 4	1 or 2	3 or 4	1 and 2

current flows in when output is low,
flows out when output is high.

Exercise 2:

 


V_{IH}
 V_{IL} } requirements

V_{OH}
 V_{OL} } guaranteed.

Which of these specifications does the manufacturer guarantee?
Which are requirements?

 Exercise 3: A logic family has $V_{OH}(\min) = 5\text{ V}$, $V_{OL}(\max) = 0.5\text{ V}$, $V_{IH}(\min) = 4\text{ V}$ and $V_{IL}(\max) = 1.5\text{ V}$. What are the noise margins?



Exercise 4: All else being equal, by how much would we expect to decrease power consumption when reducing logic levels from 5 V to 3.3 V? What would be the effect on power consumption in reducing the clock frequency from 50 MHz to 1 MHz?


$$\frac{P_2}{P_1} = \left(\frac{V_2}{V_1}\right)^2 = \left(\frac{3.3}{5}\right)^2 \approx 0.44$$

$$\text{reduction} = 1 - 0.44 = 56\%$$

$$\frac{P_2}{P_1} = \left(\frac{1}{50}\right) = 0.02$$

$$\text{reduction} = 1 - 0.02 = 98\%$$

 Exercise 5: What are the active-state current and the RC time constant for a wired-or interrupt-request line using a 10kΩ resistor pulling up a circuit with 50 pF capacitance to 3.3 V?




$$i = \frac{V}{R} = \frac{3.3\text{ V}}{10\text{ k}\Omega} = 0.3\text{ mA}$$



$$RC = 10 \times 10^3 \cdot 50 \times 10^{-12} \text{ s}$$

$$= 500 \times 10^{-9} \text{ s}$$

$$= 0.5\text{ }\mu\text{s}$$

 

  Exercise 6: How many square mm of PCB area does each package require? Which packages have their pins accessible when the package is placed on the PCB?



TQFP has accessible pins
(BGAs are under the package).