 



Analog Interfaces

Exercise 1: Draw a sine wave and indicate two sets of sampling points at twice the frequency of the sine wave: one that demonstrates aliasing and one that does not. Is it sufficient to sample at twice the highest frequency of the analog signal?



No. $f_s > 2f_{max}$

 Exercise 2: What minimum sampling rate would be required to digitize a 10 kHz square wave if you wanted to include frequency components up to the 7th harmonic (at 70 kHz)?



$$f_s > 2f_{max} = 2 \cdot 70 \text{ kHz} = 140 \text{ kHz}$$

most sample at > 140 kHz

Exercise 3: A signal with range of $\pm 3 \text{ V}$ must be quantized so that the quantization error is less than 1 mV. What minimum number of bits of resolution is required?

$$V = 6 \text{ V} = 3 - (-3)$$

$$\frac{V}{2^n} = 1 \text{ mV}$$

$$2^n = \frac{6 \text{ V}}{1 \text{ mV}}$$


$$n = \log_2 \left(\frac{6}{.001} \right) = \log_2 (6000) = 12.5$$

use 13 bit resolution ADC.

Exercise 4: A signal-to-noise power ratio of about 48 dB is considered good enough for speech communication. Approximately how many bits per sample are required to obtain this quantization SNR?

$$48 = 6B \quad B = \frac{48}{6} = 8 \text{ bits are needed}$$

 
Exercise 5: When quantizing a full-scale sine wave, what quantization SNR would be achieved with a resolution of 12 bits? What if the signal's voltage range was only half of the full-scale range?



$n = 12$ bits


$$\begin{aligned} \text{quantization SNR} &= 1.76 + 6n \text{ dB} \\ &= 1.76 + 6 \cdot 12 \\ &\approx 74 \text{ dB} \end{aligned}$$
 
$$\begin{aligned} 74 \text{ dB} &= 10 \log_{10} \left(\frac{P_{\text{signal}}}{P_{\text{noise}}} \right) = 10 \log_{10} \left(\frac{V_{\text{sig}}}{V_{\text{noise}}} \right)^2 \\ &= 20 \log_{10} \left(\frac{V_{\text{sig}}}{V_{\text{noise}}} \right) \end{aligned}$$



equivalent to using
 $n = 11$ bits of resolution

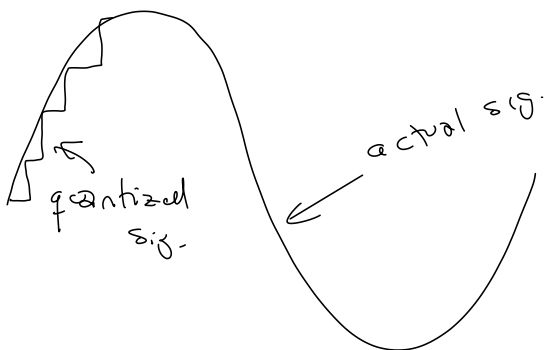
$$\text{Quant. SNR} \approx 2 + 6 \cdot 11 = 68 \text{ dB}$$




$$\text{SNR} = \frac{\text{signal power}}{\text{quant. noise power}}$$

△△△△ ← quantization noise


Exercise 6:

 

 
Assume V_1 is set to V_{ref} and all other inputs are zero (grounded). Find the Thevenin resistance (resistance to ground at V_{out} with all V_i shorted) and voltage (V_{out} with $V_1 = V_{ref}$).




Some.

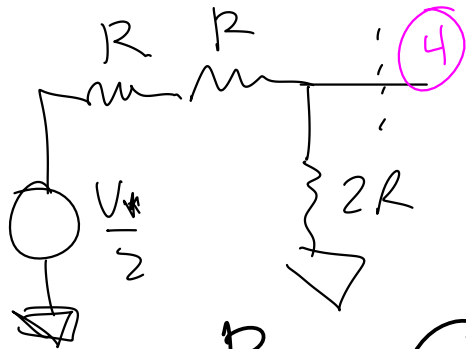

$$\frac{V_1}{4}$$

 

 Exercise 7: You are using a PWM DAC to convert a 200 VDC supply to a 48 VDC output. The switching frequency is 25 kHz. What is the duration of each PWM pulse?




$$V_{out} = \frac{t}{T} V_{ref}$$

$$t = \frac{V_{out}}{V_{ref}} \cdot T$$

$$= \frac{48}{200} \cdot \frac{1}{25 \times 10^3}$$

$$= 9.6 \mu s.$$

 Exercise 8: You are designing a PWM DAC and need resolution of 1 mV with a full-scale output of 12 V. How many bits of resolution are required? The pulse frequency is 10 kHz. What is the clock frequency?



$$t = \frac{1mV}{12V} \cdot T$$

$$1mV \Rightarrow 1$$

$$12V \Rightarrow N-1$$

$$N \approx \frac{12}{1mV} \approx 12000$$

$$N = \log_2(12000) \text{ so we can count from } 0 \text{ to } 12000.$$

$$= \underline{\underline{14 \text{ bits}}}$$

t for minimum pulse duration

$$= \frac{1}{12000} \cdot \frac{1}{10 \text{ kHz}}$$

$$2^{10} = 1024$$

$$2^4 = 16$$

$$2^{14} = 16K$$



$$2^{13} = 8K$$

$$f_{req} = 12 \times 10^3 \cdot 10 \times 10^3 = \underline{\underline{120 \text{ MHz}}}$$

Exercise 9: Rank the different DACs described above in terms of sampling rate relative to clock rate and complexity relative to resolution.

| | f_s / f_{clock} or bandwidth | complexity |
|-----------------------------------|--------------------------------|--|
| - binary weighted DAC (e.g. R-2R) | 1 | 2 resistors/bit need accurate resistors |
| - PWM | $\frac{1}{2^n - 1}$ | grows as n |
| - $\Sigma-\Delta$ | $> \frac{1}{2^n - 1}$ | grows as n |



Exercise 10:

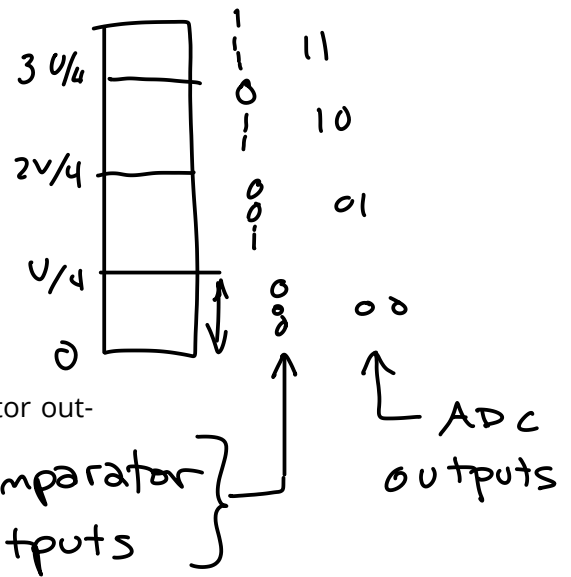 

Draw a diagram showing the voltage ranges, the comparator outputs and the binary output for the 4-bit flash ADC above.

comparator outputs } ADC outputs

 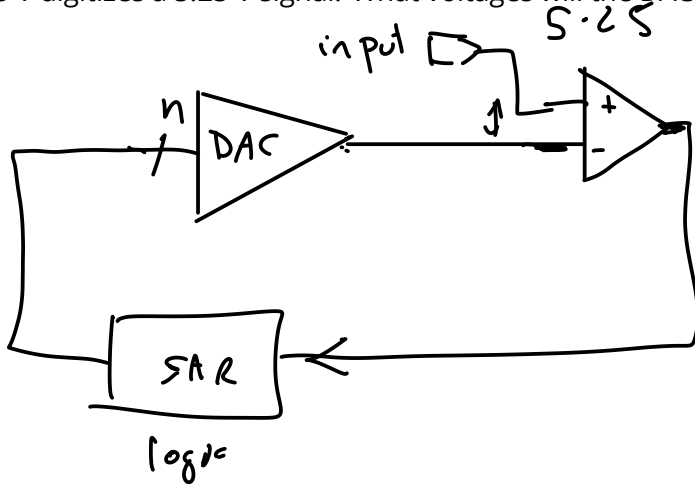Exercise 11: A SAR ADC using a 4-bit DAC with a full-scale range of 0 to 7.5 V digitizes a 5.25 V signal. What voltages will the DAC output?





| Value | 4-bit DAC Output |
|-------|------------------|
| 0 | 0000 |
| 0.5 | 0001 |
| 1.0 | 0010 |
| 1.5 | 0011 |
| 2.0 | 0100 |
| 2.5 | 0101 |
| 3.0 | 0110 |
| 3.5 | 0111 |
| 4.0 | 1000 |
| 4.5 | 1001 |
| 5.0 | 1010 |
| 5.5 | 1011 |
| 6.0 | 1100 |
| 6.5 | 1101 |
| 7.0 | 1110 |
| 7.5 | 1111 |

| 0 - 7.5 | ref. v | comp. off |
|---------|---------|-----------|
| 1000 | → 4.0V | H |
| 1100 | → 6.0V | L |
| 1010 | → 5.0V | H |
| 1011 | → 5.5V | L |
| 1010 | ← final | |



  Exercise 12: What is the slope of an integrator, in V/s, when charging a 100 nF capacitor with 5 V through a 100 kΩ resistor?



$$i = C \frac{dV}{dt}$$

$$i(t=0) = \frac{5V}{100k} = 50 \mu A = C \frac{dV}{dt}$$

$$\frac{dV}{dt} = \frac{i}{C} = \frac{50 \times 10^{-6}}{100 \times 10^{-9}} = 0.5 \times 10^3 \text{ (500 V/s.)}$$

DAcs binary

Exercise 13: Rank the different ADCs described above in terms of sampling rate relative to clock rate and complexity relative to resolution.

| | f_s / f_{clock} | complexity / resolution | $\Sigma \Delta$ | PWM |
|-----------------|-------------------|-------------------------|-----------------|----------|
| flash | 1 | $O(2^n)$ | | |
| SAR | f_s / n | $O(n)$ | +1 comp | |
| $\Sigma \Delta$ | 100 - 1000 | $O(1)$ | +1 comp | medium |
| dual-slope | " | " | " | |
| ramp. | " | " | " | high low |

↑ f_s slower
↓ cheaper

accuracy ↑

$O(n)$ means increases proportional to n .