

ELEX 2117 : Digital Techniques 2
2023 Winter Term

Quiz 3
1:30 – 2:20 PM
Friday, March 24, 2023
SW03-1710

This exam has three (3) questions on two (2) pages. The marks for each question are as indicated. There are a total of seven (7) marks. Answer all questions. Write your answers and all rough work in this paper and nowhere else. Show your work. Draw a box around your final answer. Numerical answers must include units. Books and notes are allowed. No electronic devices other than calculators are allowed. **Show your work.**

This exam paper is for:

Paper, Test 1 A00123456

Each exam is equally difficult.

Answer your own exam.

Do not start until you are told to do so.

Name: _____

BCIT ID: _____

Signature: _____

Question 1

3 marks

The table below shows part of the datasheet for a 74LS-series IC. What are the high- and low-level noise margins?

DC CHARACTERISTICS OVER OPERATING TEMPERATURE RANGE

		Min	Max	
V _{IH}	Input HIGH Voltage	2.2		V
V _{IL}	Input LOW Voltage		0.8	V
V _{OH}	Output HIGH Voltage	2.7		V
V _{OL}	Output LOW Voltage		0.4	V

Question 3


2 marks

You are designing a circuit with an open-collector output. The rise-time time constant must be less than $100\ \mu\text{s}$. The total capacitance to ground on this output is $60\ \text{pF}$. What is the highest resistance that you can use for the pull-up resistor?

Question 2

2 marks

What logic function is implemented by the circuit on the right? Give your answer as a Boolean logic expression for Y involving A, B and C.

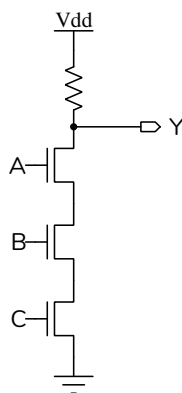

ELEX 2117 : Digital Techniques 2

2023 Winter Term

Quiz 3

1:30 – 2:20 PM

Friday, March 24, 2023

SW03-1710

This exam has three (3) questions on two (2) pages. The marks for each question are as indicated. There are a total of seven (7) marks. Answer all questions. Write your answers and all rough work in this paper and nowhere else. Show your work. Draw a box around your final answer. Numerical answers must include units. Books and notes are allowed. No electronic devices other than calculators are allowed. **Show your work.**

This exam paper is for:

Paper, Test 2 A00123456

Each exam is equally difficult.

Answer your own exam.

Do not start until you are told to do so.

Name: _____

BCIT ID: _____

Signature: _____

Question 1

3 marks

The table below shows part of the datasheet for a 74LS-series IC. What are the high- and low-level noise margins?

DC CHARACTERISTICS OVER OPERATING TEMPERATURE RANGE

		Min	Max	
V _{IH}	Input HIGH Voltage	2.0		V
V _{IL}	Input LOW Voltage		0.8	V
V _{OH}	Output HIGH Voltage	2.7		V
V _{OL}	Output LOW Voltage		0.5	V

Question 3

2 marks

You are designing a circuit with an open-collector output. The rise-time time constant must be less than $100\ \mu\text{s}$. The total capacitance to ground on this output is $35\ \text{pF}$. What is the highest resistance that you can use for the pull-up resistor?

Question 2

2 marks

What logic function is implemented by the circuit on the right? Give your answer as a Boolean logic expression for Y involving A, B and C.

