

## **Introduction to Digital Design with Verilog HDL**

**Exercise 1:** What changes would result in a 3-input OR gate?

**Exercise 2:** What schematic would you expect if the statement was  
`assign y = ( a ^ b ) | c ;?`

**Exercise 3:** If the signal **i** is declared as **logic [2:0] i;**, what is the 'width' of **i**?

If **i** has the value 6 (decimal), what is the value of **i[2]**?

Of **i[0]**?

**Exercise 4:** What are the widths and values, in decimal, of the following:

4' b1001?

5' d3?

6' h0\_a?

3?

**Exercise 5:** What are the values of the following expressions:

`!4'b010?`

`~4'b010?`

`|4'b0001?`

`^4'b1001?`

`&4'b1111?`

`&4'b1110?`

**Exercise 6:** Use slicing and concatenation to compute the byte-swapped value of an array `n` declared as `logic [15:0] n`.

**Exercise 7:** If  $n$  has the value `16'h1234`, what is the value and width of:

$\{n[7:0], n[15:8], 4'b1111\}$ ?

**Exercise 8:** Use concatenation to shift  $n$  left by two bits.



**Exercise 9:** Use concatenation to assign the high-order byte of **n** to **a** and the low-order byte to **b**.

**Exercise 10:** What are the width and value of  $\{ \{3\{2'b10\}\}, 2'b11 \}$ ?

**Exercise 11:** An array declared as `logic [15:0] n;` and has the value `16'h1234`. What are the values and widths of the following expressions?

`n[15:13]`

`!n`

`~n[3:0]`

`n>>4`

`n + 1'b1`

`n[7:0] - n[3:0]`

`n >= 16'h1234`

`n ^ '1`

`n && !n`

`n * ( !n + 1'b1 )`

**Exercise 12:** What are the width and value of the expression:  $3 \cdot 16'd10 : 8'h20$ ?

If  $x$  has the value 0, what is the value of the expression:  $1'b1 : 1'b0$ ?

If  $x$  has the value -1?

**Exercise 13:** Draw the schematics corresponding to:

$y = a ? ( b ? s1 : s2 ) : ( c ? s3 : s4 );$

$y = a ? s1 : b ? s2 : c ? s3 : s4;$

**Exercise 14:**


```
assign y = a + 1 ;
```

Some software warns about truncation. How could you re-write the **assign** statement to avoid such a warning?

**Exercise 15:** Write an `always_ff` statement that toggles (inverts) its output on each rising edge of the clock.




**Exercise 16:**

 

Identify the following in the diagram above: component names, component "instance names," component port names, module port names. Label the signal `t` in the schematic.

**Exercise 17:** Rewrite the **ex60** module using operators. Which version – “structural” or “behavioural” – is easier to understand?

**Exercise 18:**

 

How would you specify the bit marked A in the diagram above?

The bits marked B?

The least-significant byte?

**Exercise 19:**

```
// concatenation:
logic [3:0] x = { 2'b00, 2'b11 } ;

// replication (z=8'b1010_1010):
logic [7:0] y = { 4{2'b10} } ;

// array literal
logic [0:1] [3:0] z = '{ 4'b0011, 4'b1010 } ;
```

What are the dimensions and initial values of **x**, **y**, and **z** in the examples above?