

## Introduction to Digital Design with Verilog HDL

*This is a brief introduction to digital circuit design using the System Verilog Hardware Description Language (Verilog HDL). After this lecture you should be able to: define a module with single- and multi-bit **logic** inputs and outputs; write Verilog numeric literals in binary, decimal and hexadecimal bases; declare arrays and arrays of arrays; evaluate the value and length of expressions containing **logic** signals, arrays, numeric literals and the operators described below; use **assign**, **always\_ff**, and component instantiation statements to create combinational logic, registers, and to instantiate one module in another.*

### Introduction

Hardware Description Languages (HDLs) are used to design digital circuits. In this course we will use System Verilog, the modern version of the Verilog HDL, rather than the other popular HDL, VHDL.

Let's start with a simple example – a circuit called an **ex1** that has one output (**y**) that is the logical AND of two input signals (**a** and **b**). The file **ex1.v** contains the following Verilog description:

```
// AND gate in Verilog

module ex1 ( input logic a, b,
             output logic y );

    assign y = a & b ;

endmodule
```

Some observations on Verilog syntax:

- Everything following `//` on a line is a comment and is ignored.
- Module and signal names can contain letters, digits, underscores (`_`), and dollar signs (`$`). The first character of an identifier must be a letter or an underscore. They cannot be the same as certain reserved words (e.g. **module**).
- Verilog is case-sensitive: **a** and **A** would be different signals.
- Statements can be divided into any number of lines. Any number of spaces can be used. A semicolon ends each statement.


Capitalisation and indentation styles vary. In this course you will need to follow the coding style guide available on the course website.

The module definition begins by defining the input and output signals for the device being designed.

The body of the module contains one or more statements, each of which operates at the same time – *concurrently*. This is the key difference between HDLs and programming languages – HDLs allows us to define concurrent behaviour.

The single statement in this example is a signal assignment that assigns the value of an expression to the output signal **y**. Expressions involving **logic** signals can use the logical operators described below including **&** (AND), **|** (OR), and **^** (XOR). Parentheses can be used to order the operations.

 From this Verilog description a program called a logic synthesizer (e.g. Intel's Quartus) can generate a circuit that has the required functionality. In this case it's not too surprising that the result is the following circuit:



If you're familiar with the C programming language you'll note that Verilog uses similar syntax.

**Exercise 1:** What changes would result in a 3-input OR gate?

**Exercise 2:** What schematic would you expect if the statement was `assign y = ( a ^ b ) | c ;`?

### Syntax

#### Reserved Words

System Verilog has about 250 reserved words (including many common ones such as **time**, **wait**, **disable**, **reg**, **table**, **input**, ...) that may not be used as module or signal names. Doing so will give a syntax error when you try to compile ("synthesize") the description. An editor with syntax highlighting will help you identify and avoid using reserved words.

## logic values

Verilog's **logic** signals can have four values: **0** (false or low), **1** (true or high), **z** (high impedance) and **x** (undefined).

## Arrays

An array is a collection of **logic** signals whose elements can be selected by a value called the index. Arrays often represent numerical values in binary form.

For example, the declaration **logic [3:0] a;** specifies an array named **a** with a 'width' of four bits.

In this example the bit indices are declared as going from 3 down to 0. If the bit values are written out and represent a binary number then **a[3]**, the left-most bit, is the most significant bit. **a[0]** is the right-most (least significant) bit.

**Exercise 3:** If the signal **i** is declared as **logic [2:0] i;**, what is the 'width' of **i**? If **i** has the value 6 (decimal), what is the value of **i[2]**? Of **i[0]**?

## Numeric Literals

Numeric literals, often called "constants," are written as a sequence of up to three parts: the number of bits; the letters '**b**' for binary, '**h**' for hex, or '**d**' for decimal; and the value in the specified base. The default width is 32 and the default base is decimal. Underscores (**\_**) may be used within the value to improve readability.

**Exercise 4:** What are the widths and values, in decimal, of the following: **4'b1001**? **5'd3**? **6'h0\_a**? **3**?

The notations '**0**' and '**1**' are convenient abbreviations for a literal that is all-zeros or all-ones.

## Expressions

Logic circuits in HDLs are defined using expressions as in the example above. These include operators that operate on "operands" – numeric literals ("constants"), **logic** signals and arrays of these. Operators with higher "precedence" are applied before those of lower precedence. If two operators are of equal precedence they are applied from left to right. Operators can change the number of bits in an expression (the "width") as they're applied. Values are padded with zeros on the left when necessary.

To evaluate an expression:

1. find the width and value of each operand (signals or literals)
2. group the operators with operands according to precedence (or left to right when the precedence is the same)
3. apply the operators, obeying rules for padding and truncation as appropriate for the operands

## Operators

The following describe some useful Verilog operators in order of decreasing precedence.

**Slices** A range of bits in an array (a "slice") can be extracted using a range of indices in brackets (**[first:last]**) after the array name. The bit order cannot be reversed. The width is the number of bits in the slice.

**Negation and Reduction** Logical negation (**!**) is zero (0) when applied to a non-zero operand and one (1) otherwise. The width is 1 bit.

Bitwise negation (**~**) inverts the value of each bit. The width is the width of the operand.

Logical reduction operators apply AND (**&**), OR (**|**) and XOR (**^**) operations to the bits of an array. The result has a width of 1 bit.

**Exercise 5:** What are the values of the following expressions: **!4'b010**? **~4'b010**? **|4'b0001**? **^4'b1001**? **&4'b1111**? **&4'b1110**?

**Concatenation** The concatenation operator (**{,}**) combines expressions into a wider value. The width is the sum of the widths.

**Exercise 6:** Use slicing and concatenation to compute the byte-swapped value of an array **n** declared as **logic [15:0] n**.

**Exercise 7:** If **n** has the value **16'h1234**, what is the value and width of: **{n[7:0], n[15:8], 4'b1111}**?

**Exercise 8:** Use concatenation to shift **n** left by two bits.

Concatenations of variables can also be used on the left hand side of an assignment.

**Exercise 9:** Use concatenation to assign the high-order byte of **n** to **a** and the low-order byte to **b**.

**Replication** The replication operator (**{n,{...}}**) repeats the operand(s) **n** times. The width is **n** times the width of the operand(s).

**Exercise 10:** What are the width and value of { {3{2'b10}}, 2'b11 }?

**Arithmetic** Multiplication (\*), division (/), addition (+) and subtraction (-) can be applied to arrays. The first two have higher precedence. The width is the largest of the two operands' widths.

**Shift** Right- (>>) and left-shift (<<) operators shift the bits in the array operand on the left by the amount on the right. The width is the width of the left operand.


**Comparison** When arithmetic comparison operators (<, >, <=, >=, ==, !=) are applied to arrays the result is 1 if the comparison is true and 0 otherwise. The width is 1 bit.

**Bitwise Logical** Bitwise logical operators (&, |, ^) are applied to the corresponding bits in two operands. The width is the largest of the two operands' widths.

**Logical** The logical AND operator (&&) has value 1 if both operands are non-zero. The logical OR operator (||) has value 1 if either operand is non-zero. The width is 1 bit.

 **Exercise 11:** An array declared as `logic [15:0] n;` and has the value `16'h1234`. What are the values and widths of the following expressions? `n[15:13] !n~n[3:0] n>>4 n + 1'b1 n[7:0] - n[3:0] n >= 16'h1234 n ^ '1 n && !n n * ( !n + 1'b1 )`

**Conditional Operator** Verilog's conditional operator is a concise syntax for describing a two-way multiplexer. The operator consists of three parts: the condition, the true value and false value. The result of the operator is the true value if the condition is non-zero, or the false value otherwise. The width is the largest of the true and false value widths. For example:



sets **y** to **a** when **sel** is non-zero and sets **y** to **b** when **sel** is zero.

**Exercise 12:** What are the width and value of the expression: `3 ? 16'd10 : 8'h20`? If **x** has the value 0, what is the value of the expression: `x ? 1'b1 : 1'b0`? If **x** has the value -1?


The following example implements a multiplexer that selects from one of two 4-bit inputs:

```
module ex36 (input logic outhi,
             input logic [3:0] hi, lo,
             output logic [3:0] y) ;

    assign y = outhi ? hi : lo ;

endmodule
```

which results in:

 

Conditional operators can be used to concisely describe trees of multiplexers. In the absence of parentheses a sequence of conditional operators is evaluated from left to right.

**Exercise 13:** Draw the schematics corresponding to:

`y = a ? ( b ? s1 : s2 ) : ( c ? s3 : s4 ) ;`

`y = a ? s1 : b ? s2 : c ? s3 : s4 ;`

## Statements

The **assign**, **always\_ff**, and component instantiation statements create logic. Statement order does not matter since the hardware created by each statement operates simultaneously (*concurrently*).

### assign

The **assign** statement continuously assigns the value of the expression on the right-hand side (RHS) to the signal on the left-hand side (LHS). The most significant bits are dropped if the RHS is wider than the LHS. For example, this module:

```
module ex62 ( input logic [15:0] a,
              output logic [15:0] y ) ;
    assign y = a + 1 ;
endmodule
```

results in this logic:

**Exercise 15:** Write an `always_ff` statement that toggles (inverts) its output on each rising edge of the clock.

## Component Instantiation

Module instantiation inserts a copy of (“instantiates”) one module into another and connects signals to the instantiated module’s input and output ports. For example, the module:


```
module ex60 ( input logic x, y, z,
              output logic c );

    logic t ;

    ex1 ex1_1 ( x, y, t );
    ex1 ex1_2 ( z, t, c );

endmodule
```

creates a 3-input AND gate by instantiating two instances of the `ex1` module defined earlier:

 

**Exercise 14:** Some software warns about truncation. How could you re-write the `assign` statement to avoid such a warning?

## always\_ff


The `always_ff` statement creates flip-flops and registers. For example, the following Verilog:

```
module ex2 (input logic [3:0] d,
            input logic clk,
            output logic [3:0] q) ;

    always_ff @(posedge clk)
        q <= d ;

endmodule
```

 synthesizes a 4-bit D flip-flop that transfers the `d` input to the `q` output on the rising (positive) edge of `clk`:




Note the use of “non-blocking assignment” (`<=`) in `always_ff` statements. As with the blocking assignment (`=`), the leftmost bits are dropped if the RHS is wider than the LHS.

**Exercise 16:** Identify the following in the diagram above: component names, component “instance names,” component port names, module port names. Label the signal `t` in the schematic.

**Exercise 17:** Rewrite the `ex60` module using operators. Which version – “structural” or “behavioural” – is easier to understand?

## Arrays of Arrays

We can also declare arrays of arrays. For example, `logic[3:0][7:0] w;` declares `w` as an array of four arrays of eight bits. A single index selects one of the bytes, two indices selects a byte as well as a bit from that byte:

 

**Exercise 18:** How would you specify the bit marked A in the diagram above? The bits marked B? The least-significant byte?

## Array Literals

Literals (constants) of arrays can be defined by grouping with '{...}'. The quote distinguishes an array literal from concatenation.

```
// concatenation:
logic [3:0] x = { 2'b00, 2'b11 } ;

// replication (z=8'b1010_1010):
logic [7:0] y = { 4{2'b10} } ;

// array literal
logic [0:1] [3:0] z = '{ 4'b0011, 4'b1010 } ;
```

**Exercise 19:** What are the dimensions and initial values of x, y, and z in the examples above?