 


Applications of State Machines

Exercise 1: The example above is an N-bit shift register that shifts the bits right. Draw a block diagram and write the Verilog for a 6-bit shift register that shifts left.



module shift ;

logic [5:0] q;
logic in;
always_ff @(

q <= {q[4:0], in};

q <= {q << 1, in};

left shift

7 bit

~~q <= {in, q >> 1};~~

right shift


end module

wrong - this would always shift in a zero!



q <= {in, q[5:1]};

right shift


Exercise 2:

 

  Fill in the diagram above for a 4-bit ($N = 4$) right-shift shift register. Assume the initial value is zero. Which bit is the oldest (first) value in the waveform? Which bit of the shift register holds the oldest value?



 Exercise 3: Draw a block diagram and write the Verilog for a circuit that sets an output named **detect** high when the sequence of values 1, 1, 0, 1 has appeared on an input named **in** on successive rising edges of the clock.



always_ff @(posedge clock)

q <= {in, q[3:1]};

assign detect = q == 4'b1011;

OR
= q[3] && !q[2] && q[1] && q[0];

Exercise 4: How could you modify the code so that **digits** is only updated when an **enable** input is asserted?

```
always_ff @(posedge clk) digits
    <= { digits[1:3], digit } ;
```

<= enable ? { digits[1:3], digit } :
digits;


Exercise 5: How many states can this state machine have?

$$16 \times 16 \times 16 \times 16 = (2^4)^4 = 2^{16}$$

$$= 65536$$

1, 2, 3, 4

 Exercise 6: Draw the state transition diagram for this simpler implementation. How many states are there? Write the Verilog using a 3-bit **count** state variable.



always for @ (posedge clk)

state <= // <start state> && <condition> ? <end state>:

state == 0 && digit == 1 ? 1 :

state == 1 && digit == 2 ? 2 :

state == 2 && digit == 3 ? 3 :

state == 3 && digit == 4 ? 4 :

state == 1 && digit != 2 ? 0 :

state == 2 && digit != 3 ? 0 :




state == 3 && digit != 4 ? 0 :

state ;

template

   Exercise 7: For which states would a **fell** output be asserted? A **rose** output? Draw the schematic and write the Verilog for this state machine. Assume an input **in** and a 2-bit register **bits** that holds the two most recent input values.

fell is asserted for state 10
 rose is asserted for state 01



```
module edge-detect (
  input logic in, clk,
  output logic rose, fell);
```

```
  logic [1:0] bits;
```



```
  always_ff @(posedge clk) bits <= {bits[0], in};
```

```
  assign rose = bits == 2'b01;
```

```
  assign fell = bits == 2'b10;
```

```
end module
```


Exercise 8: Can you design an edge detector that uses only one bit?
 Is this a Mealy or a Moore state machine?

  

Exercise 9: Write `always_ff` statements that implement these state machines.

count	in == out	next count
x	1	$N - 1$
0	x	$N - 1$
n	0	$n - 1$

se

 

logic [:] count ;

always_ff @(posedge clk)

count <=

in == out ? N-1 :

!count ? N-1 :

in != out ? count-1 :


count ;

always_ff @(posedge clk)

out <=

count != 0 ? out : in ;

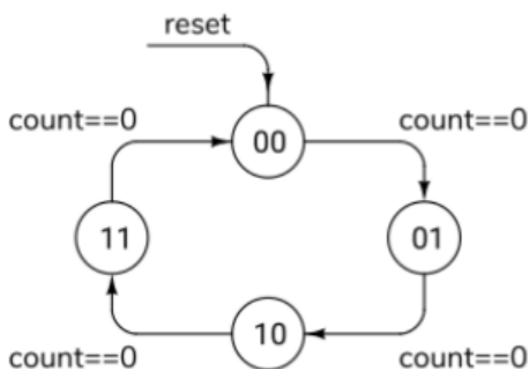Exercise 10: Write the state transition table for this state machine.



count	reset	next count
x	1	00
00	0	01
01	0	10
10	0	11
11	0	00